



Answer all the questions

Question ①

(15 marks)

- (a) For the circuit shown in Fig.1 (a), assume ideal diodes, find I_{D1} , I_{D2} , I and voltage V .
- (b) For the circuit shown in Fig. 1(b), sketch V_{out} against time for the given input signal.

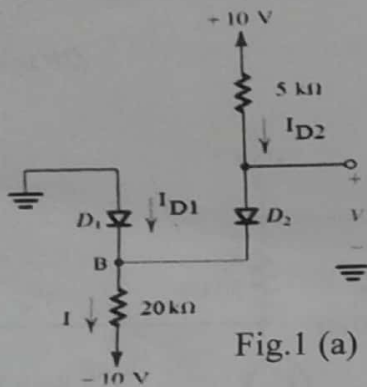


Fig.1 (a)

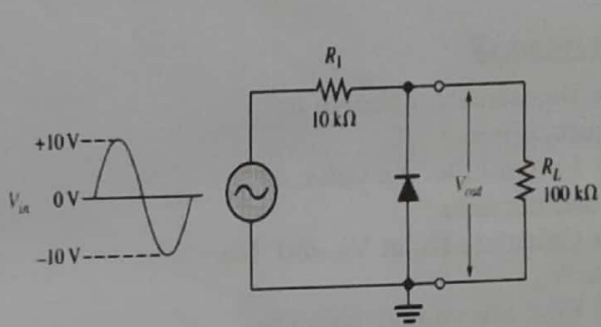



Fig.1 (b)

Question ②

(15 marks)

For the circuit shown, if the voltage drops on each diode when conduct is 0.7 V, sketch the voltage against time

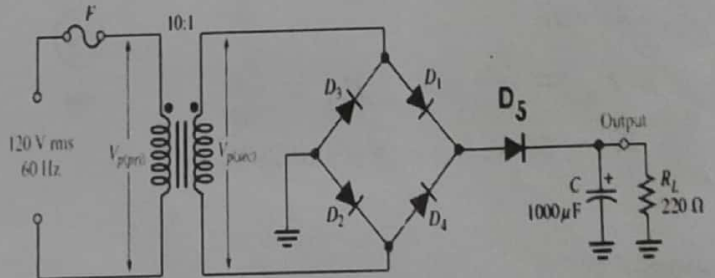- (a) Before the diode D_5
- (b) At the output load R_L .
- (c) Calculate the ripple voltage (V_r) and the value of the DC output voltage.



Given $V_{r(PP)} = \left(\frac{1}{fR_L C}\right)V_{P(Rec)}$

$V_{DC} = \left(1 - \frac{V_r(PP)}{2}\right)V_{P(Rec)}$

$V_{rms} = V_p / \sqrt{2}$


Question ③

(15 marks)

For the circuit shown in figure

- (a) Determine V_Z at each of the currents I_{ZK} and I_{ZM}
- (b) What is the value of R that should be used?
- (c) Determine the minimum and maximum value of R_L .

Given $V_{Z0} = 15 V$, $I_{Z0} = 17 mA$, $I_{ZK} = 0.25 mA$, and $r_Z = 14 \Omega$, $P_{Zmax} = 1 W$.

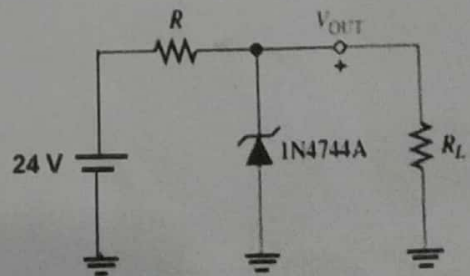


Question 4

(10 marks)

For the BJT circuit shown, Given $\beta = 100$

- (a) Calculate all the DC voltages and currents
- (b) What is the transistor region of operation
- (c) What is the value of I_C to make transistor in deep saturation

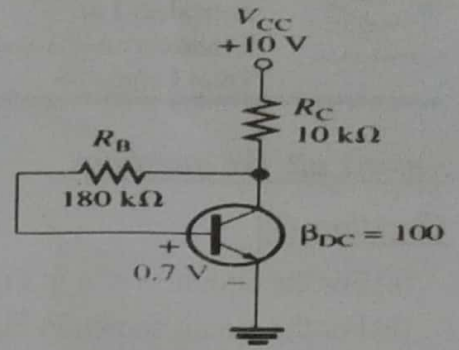


Question 5

(20 marks)

For the transistor shown in figure, given $\beta = 75$

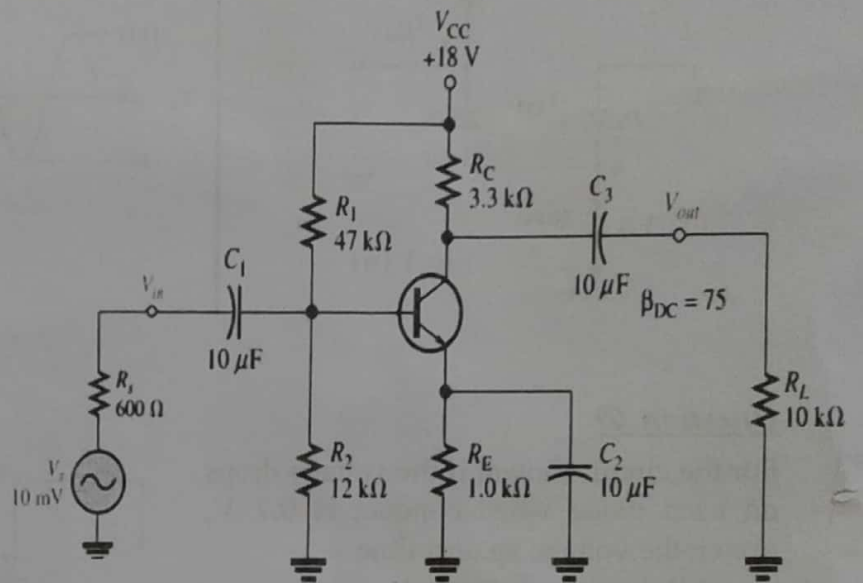
- (a) Find all Dc the voltages and currents
- (b) Calculate R_{in} , at V_{in} and R_o at V_{out}
- (c) Find the voltage gain G_{V_o}
- (d) For the given ac input, calculate the corresponding value of V_{out} .



Given

$$r_{\pi} = \frac{V_T}{I_B}, \quad r_o = \frac{V_A}{I_C}$$
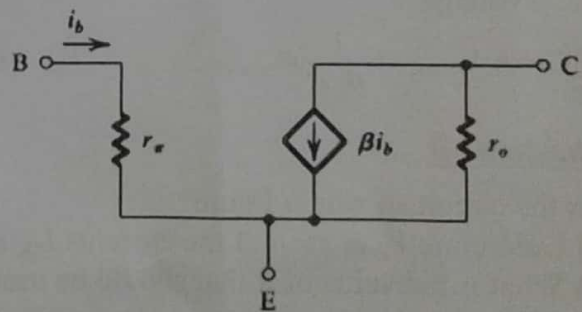
$$V_A = 50 \text{ V}, \quad V_T = 0.025 \text{ V}$$



Good Luck

Q(11)

assume ideal diode

assume D1 on

$V_x = 0$

$I = \frac{0 - 10}{20} = 0.5 \text{ mA}$

at node x

$I_{D2} = \frac{10 - 0}{5} = 2 \text{ mA}$


at x $I_{D1} + I_{D2} = I$
 $I_{D1} + 2 = 0.5$

So $I_{D1} = -1.5$, so D1 off

$I_{D1} = 0$

$I_{D2} = I = \frac{10 - (-10)}{25} = \frac{20}{25} \text{ mA}$

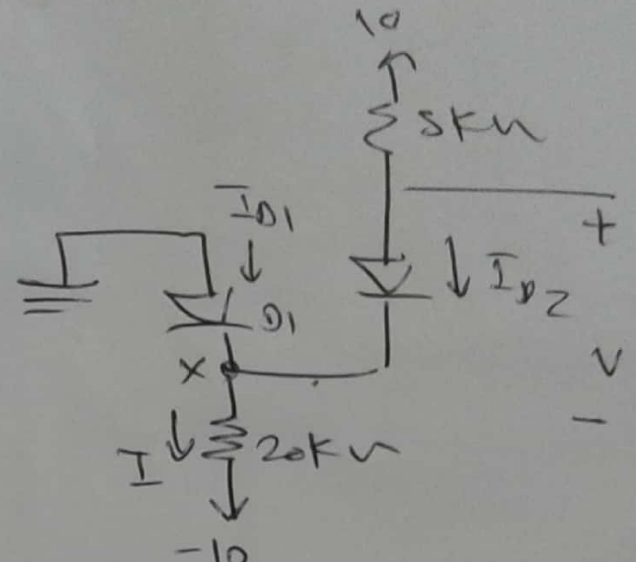$V = 10 - \frac{20}{25} \times 5 = 6 \text{ V}$




1 1/2



3

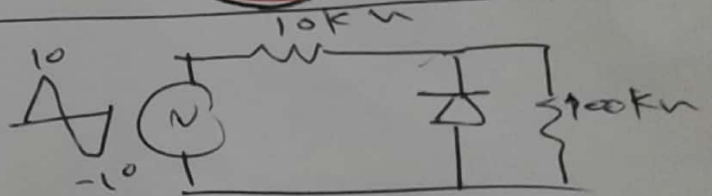(b) diode will conduct when $v_i < -0.7$

$V_o = 10 + \frac{10 \times 100}{110} = 9.09$




7 1/2

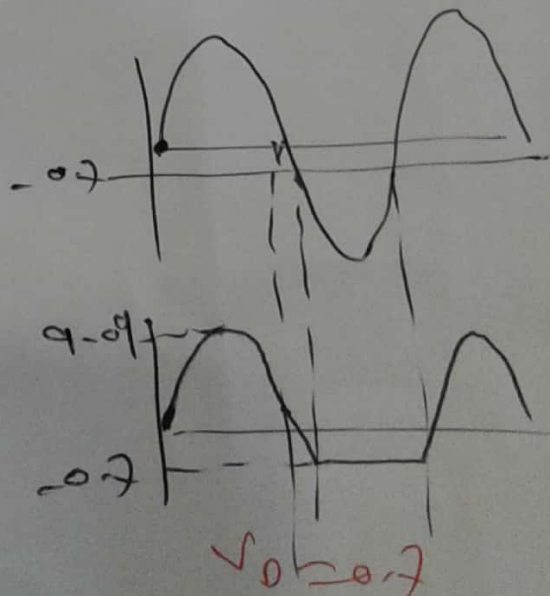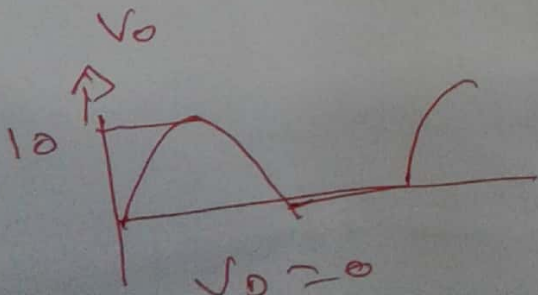


$$\frac{Q(2)}{V_{inpp}} = 120\sqrt{2} = 169.7 \text{ V} \quad (2)$$
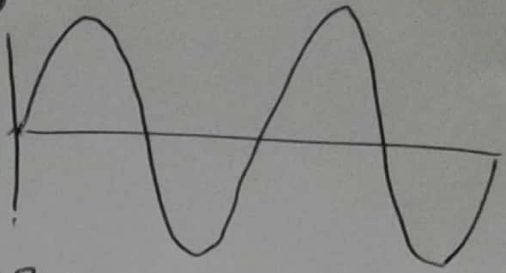
$$V_{sec} = 16.97 \text{ V} \quad \checkmark$$



$$V_{refr} = 16.97 - 1.4 = 15.57 \text{ V}$$

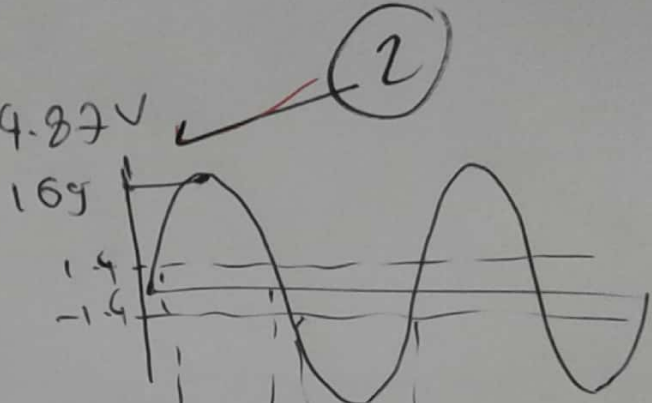
$$\frac{\text{after DS}}{V_{pDS}} = 15.57 - 0.7 = 14.87 \text{ V} \quad (2)$$



$$V_{rpp} = \frac{V_P}{f_{RLC}}$$

$$= \frac{14.87}{120 \times 220 \times 100 \times 10^6}$$


$$= 0.56325 \quad \checkmark \quad (2)$$

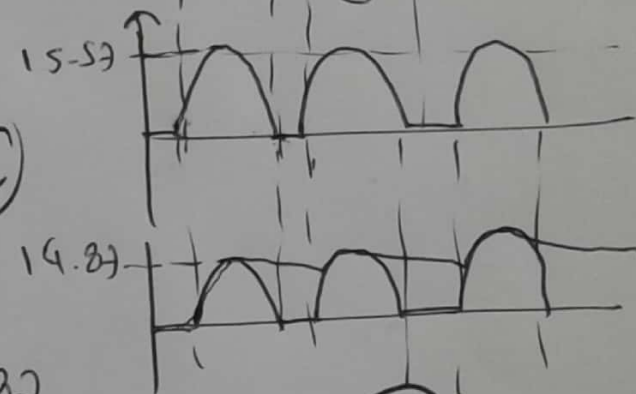

$$V_{DC} = \left(1 - \frac{V_{rpp}}{2}\right) V_{p_{rect}}$$

$$= \left(1 - \frac{0.56325}{2}\right) \times 14.87$$
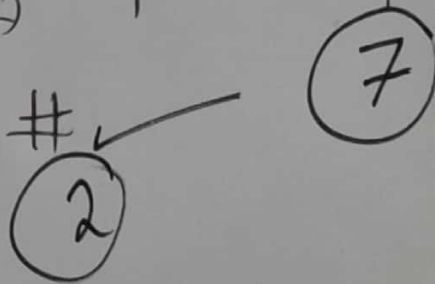
$$= 10.682 \text{ V} \quad \# \quad (2)$$



Q(3)

$$V_{zk} = V_{z0} - (I_{z0} - I_{zk}) R_z$$

$$= 15 - (17 - 0.25) \times 14$$

$$= 14.7655 \text{ V} \quad \#$$

$$I_{z\text{max}} = \frac{P_{D\text{max}}}{V_{z0}} = \frac{1 \text{ W}}{15}$$

$$= 66.66 \text{ mA}$$

$$V_{z\text{max}} = 15 + (66.66 - 17) \times 14$$

$$= 15.6953 \text{ V} \quad \#$$

$$R = \frac{V_1 - V_{z0}}{I_{z\text{max}}} = \frac{24 - 15}{66.66}$$



$$= 135 \Omega \quad \#$$

minimum value of R_L when
 I_L is max or I_z min

$$I_{z\text{max}} = I_T - I_{z\text{min}}$$

$$= \frac{24 - 15}{0.135} - 0.25 = 66.4166 \text{ mA} \quad \#$$
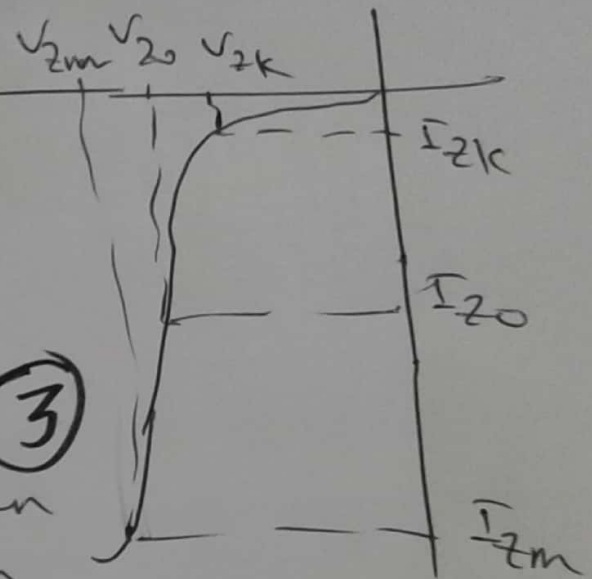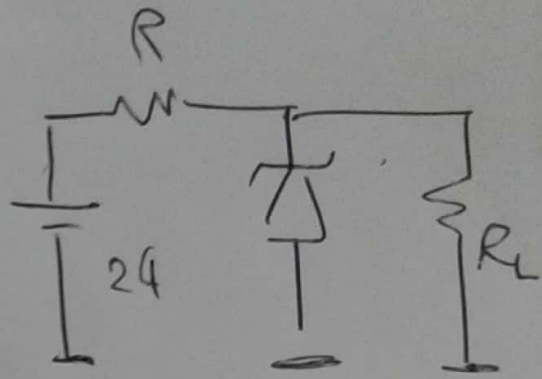
$$R_{L\text{min}} = \frac{V_z}{I_{z\text{max}}} = \frac{15}{66.4166} = 225.8 \Omega \quad \#$$



Q(4)

assume operate in active region

$V_E = 0$ (#) (1)

$V_B = 0.7$ (#) (1)

$10 = 10 I_E + 180 I_B + 0.7$



$10 - 0.7 = 10 I_E + \frac{180}{101} I_E$

$I_E = 0.78932 \text{ mA}$ (#) (1)

$I_C = \alpha I_E = \frac{100}{101} \times 0.78932 = 0.7815 \text{ mA}$ (#) (1)

$I_B = \frac{I_C}{\beta} = 0.007815 \text{ mA}$ (#) (1)

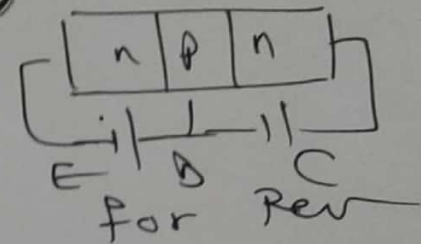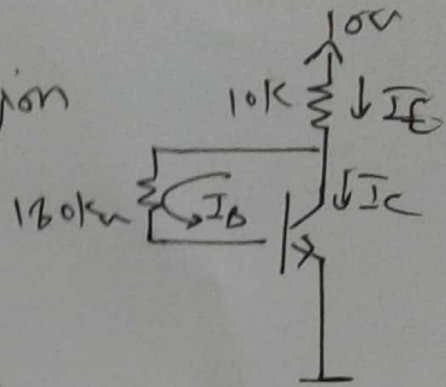$V_C = 10 - 10 I_E = 2.10068 \text{ V}$ (#) (1)



(b) active ✓ (2)

(c) for deep saturation



$V_{CE} = 0.2$

$\therefore I_C = \frac{10 - 0.2}{10} = 0.98 \text{ mA}$ (2)

Q(5) DC analysis, $\beta = 75$

$47 \parallel 12 = 9.5593$

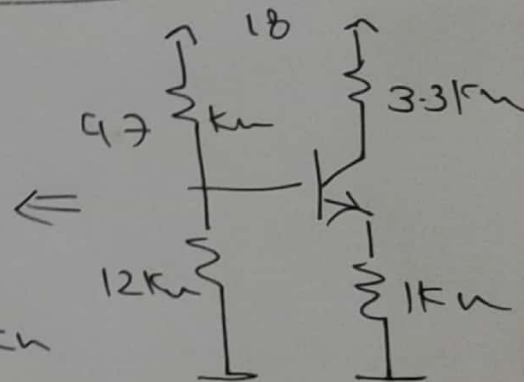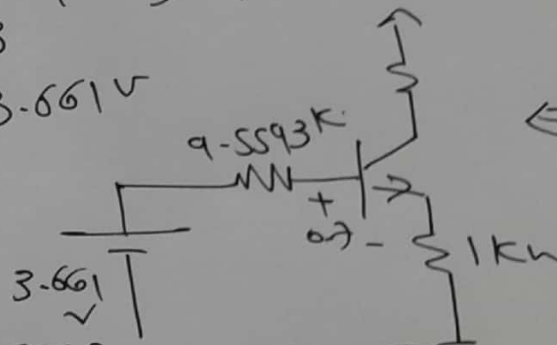$V_{BB} = \frac{18 \times 12}{12 + 47} = 3.661 \text{ V}$



$3.661 = \frac{9.5593}{76} I_E + 0.7 + I_E$

$I_E = 2.63 \text{ mA}$ (#)

$I_C = \alpha I_E = 2.59556 \text{ mA}$ (#)

$I_B = 0.0346 \text{ mA}$ (#)

$V_E = I_E \times 1 = 2.63 \text{ V}$ (#)


$V_B = V_E + 0.7 = 3.33 \text{ V}$ (#)

$V_C = 18 - 33 \times 2.5955 = 9.43 \text{ V}$ (#)

(5)

(a)

check active ✓

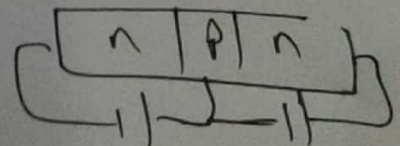



AC analysis

all AC are sic
all DC are sic

$$r_{\pi} = \frac{V_T}{I_B} = \frac{0.025}{0.0346} = 0.723 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = 19.26 \text{ k}\Omega$$

(2)

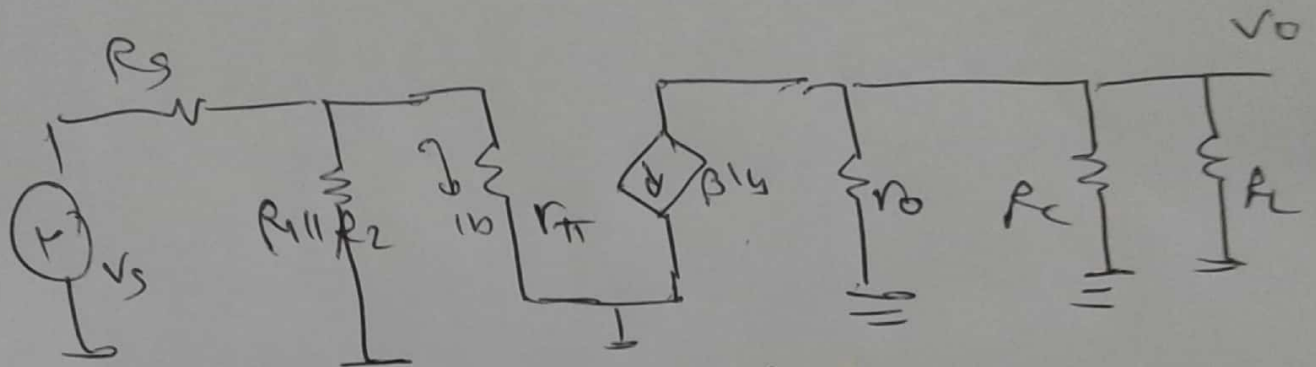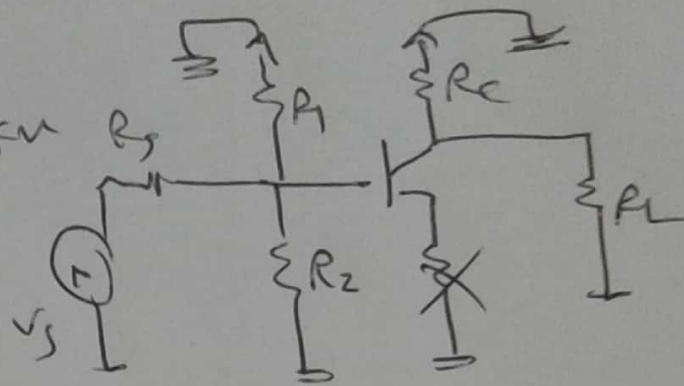

$$\therefore v_{o \downarrow \text{without}} = -\beta i_b (r_o \parallel R_C)$$

$$v_{o \downarrow \text{with}} = -\beta i_b (r_o \parallel R_L \parallel R_C)$$

$$v_i = \beta r_{\pi} i_b$$

$$\therefore R_i = R_1 \parallel R_2 \parallel r_{\pi} = 0.6722 \text{ k}\Omega \quad \#$$

$$R_o = r_o \parallel R_C = 2.817 \text{ k}\Omega \quad \#$$

$$A_v = \frac{v_o}{v_i} = -\beta \frac{(r_o \parallel R_L \parallel R_C)}{r_{\pi}}$$

$$A_{v_o} = \frac{v_o}{v_i} = -\beta \frac{(r_o \parallel R_C)}{r_{\pi}}$$

$$v_i = \frac{v_{s_{sig}} \times R_1 \parallel R_2 \parallel r_{\pi}}{R_s + R_1 \parallel R_2 \parallel r_{\pi}}$$

$$\therefore \frac{v_i}{v_{s_{sig}}} = \frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_s + R_1 \parallel R_2 \parallel r_{\pi}}$$

$$A_{v_o} = \frac{v_o}{v_i} \cdot \frac{v_i}{v_{s_{sig}}} = -\beta \frac{(r_o \parallel R_C)}{r_{\pi}} \cdot \frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_s + R_1 \parallel R_2 \parallel r_{\pi}} \quad \#$$

$$= \frac{-75 \times 19.26 \parallel 3.3}{0.5 + 0.6722} \times \frac{0.6722}{0.5 + 0.6722}$$

$$v_{o_{ac}} = -1.544177 \text{ V} \quad \#$$