



Model Answer

Question 1: (1X2→20 Points)

- 1) c → $v_6 = -16.7V$
- 2) d
- 3) b → $0.05 J$
- 4) b → $v_a = 3.03V$
- 5) d → $1.28 J$
- 6) d
- 7) a → 2Ω
- 8) c
- 9) c → $V_{out} = 3 V_{in}$
- 10) b

Question 2: (12 Points)

Open circuit case to get V_{th} :

a)

$$\frac{v_x - 100}{4} + \frac{v_x - 20}{4} + \frac{v_x - v_a}{4} = 0 \text{ (1 point)}$$

$$v_\phi = v_x - 20 \text{ (1 point)}$$

$$\frac{v_a - v_\phi - 100}{4} = \frac{v_x - v_a}{4} \text{ (1 point)}$$


$$v_x = 80 V, \quad v_a = V_{th} = 120 V \text{ (1 point)}$$

Short circuit case to get I_{sc} :

$$\frac{v_x - 100}{4} + \frac{v_x - 20}{4} + \frac{v_x - v_a}{4} = 0 \text{ (1 point)}$$

$$\frac{v_a - v_x}{4} + \frac{v_a - v_\phi - 100}{4} = I_{sc} \text{ (1 point)}$$
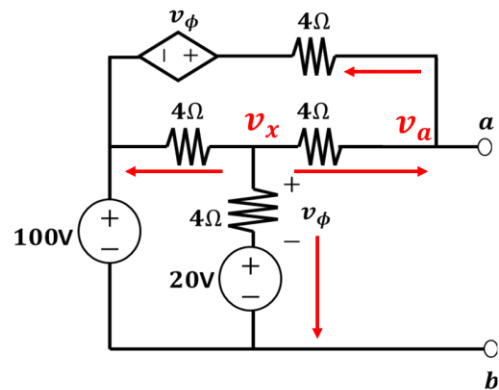
$$v_a = zero \rightarrow S.C, \quad v_x = 40V, \quad v_\phi = 20V$$



$$\frac{dv(t)}{dt} = -12 \sin(3t) \quad (1 \text{ point})$$


$$i(t) = -4.57 \sin(3t) [\mu A] \quad (2 \text{ point})$$

Question 3)-b: (4 Points)

KVL at loop:

$$-v_c + v_L + v_o = 0 \quad (1 \text{ point})$$

$$v_o = v_c - v_L$$

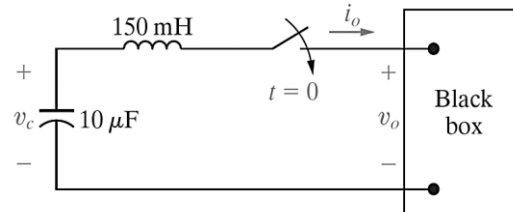

$$v_c = -\frac{1}{10 \times 10^{-6}} \left(\int_0^t 0.2e^{-800x} dx - \int_0^t 0.04e^{-200x} dx \right) + 5 \quad (1.5 \text{ points})$$

$$= 25(e^{-800t} - 1) - 20(e^{-200t} - 1) + 5$$

$$= 25e^{-800t} - 20e^{-200t} \text{ V}$$

$$v_L = 150 \times 10^{-3} \frac{di_o}{dt} \quad (1 \text{ points})$$

$$= 150 \times 10^{-3} (-160e^{-800t} + 8e^{-200t})$$

$$= -24e^{-800t} + 1.2e^{-200t} \text{ V}$$


$$v_o = v_c - v_L$$

$$= (25e^{-800t} - 20e^{-200t}) - (-24e^{-800t} + 1.2e^{-200t})$$

$$= 49e^{-800t} - 21.2e^{-200t} \text{ V}, t > 0 \quad (0.5 \text{ points})$$

Question 4: (12 Points)

Step 1:

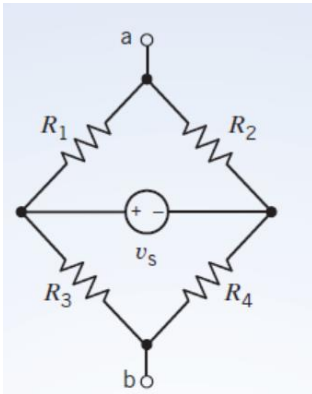


$$V_{o.c} = V_{ab} = V_a - V_b$$

$$V_{o.c} = \left[\frac{R_2}{R_2 + R_1} v_s - \frac{R_4}{R_4 + R_3} v_s \right] \quad (2 \text{ points})$$

$$R_t = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4} \quad (2 \text{ points})$$

Thévenin equivalent:

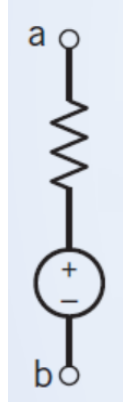

Apply KVL at node a:



$$v_a = i_1 R_t + v_{oc} + v_1 \quad (2 \text{ points})$$


$$v_1 = 0, \quad i_1 R_t = 0$$

$$v_a = v_{oc}$$

Apply KCL at node a:
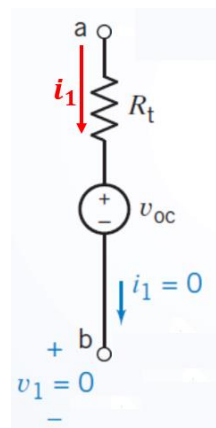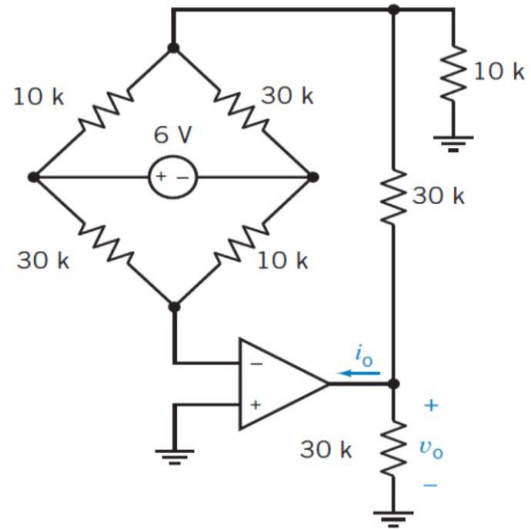
$$\frac{v_a - v_{oc}}{R_t} + \frac{v_a - v_o}{R_5} + \frac{v_a}{R_6} = 0 \quad (2 \text{ points})$$



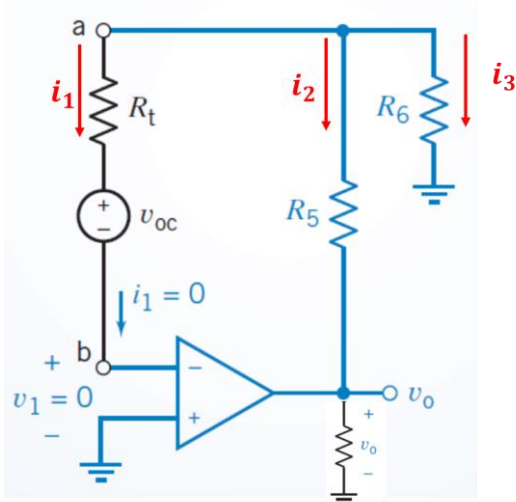


$$\frac{v_{oc} - v_o}{R_5} + \frac{v_{oc}}{R_6} = 0$$

$$v_o = \left[\frac{R_2}{R_2 + R_1} - \frac{R_4}{R_4 + R_3} \right] \left[1 + \frac{R_5}{R_6} \right] v_s$$

Apply values to the above equation:

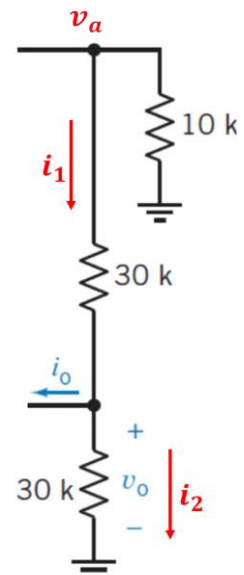- $v_o = 12 V$
- $v_{th} = v_a = 3V$ (1 point)
- $i_1 = \frac{v_a - v_o}{30K} = -0.3 mA$, (1 point)
- $i_2 = \frac{v_o}{30K} = 0.4 mA$, (1 point)
- $i_1 = i_o + i_2$,
- $i_o = -0.7mA$. (1 point)



Best wishes