



Digital Logic Circuits Analysis (E321)


Model Answer

No. of Questions: 5


Question (1)

(12 Marks)

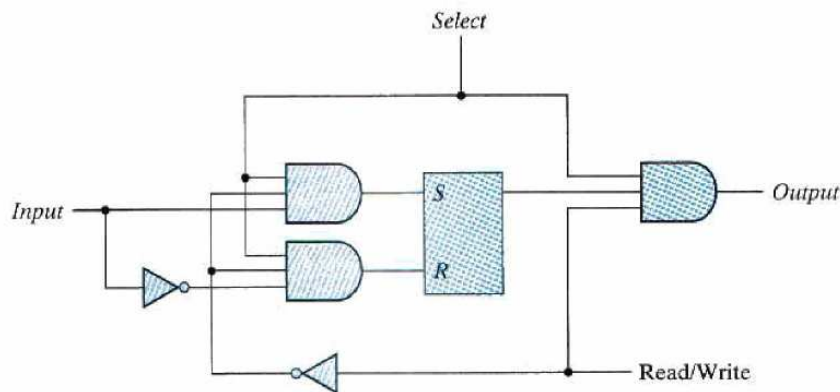- a. Draw the equivalent logic diagram of a binary cell “basic building block of a RAM” that stores one bit of information. (3 Marks)



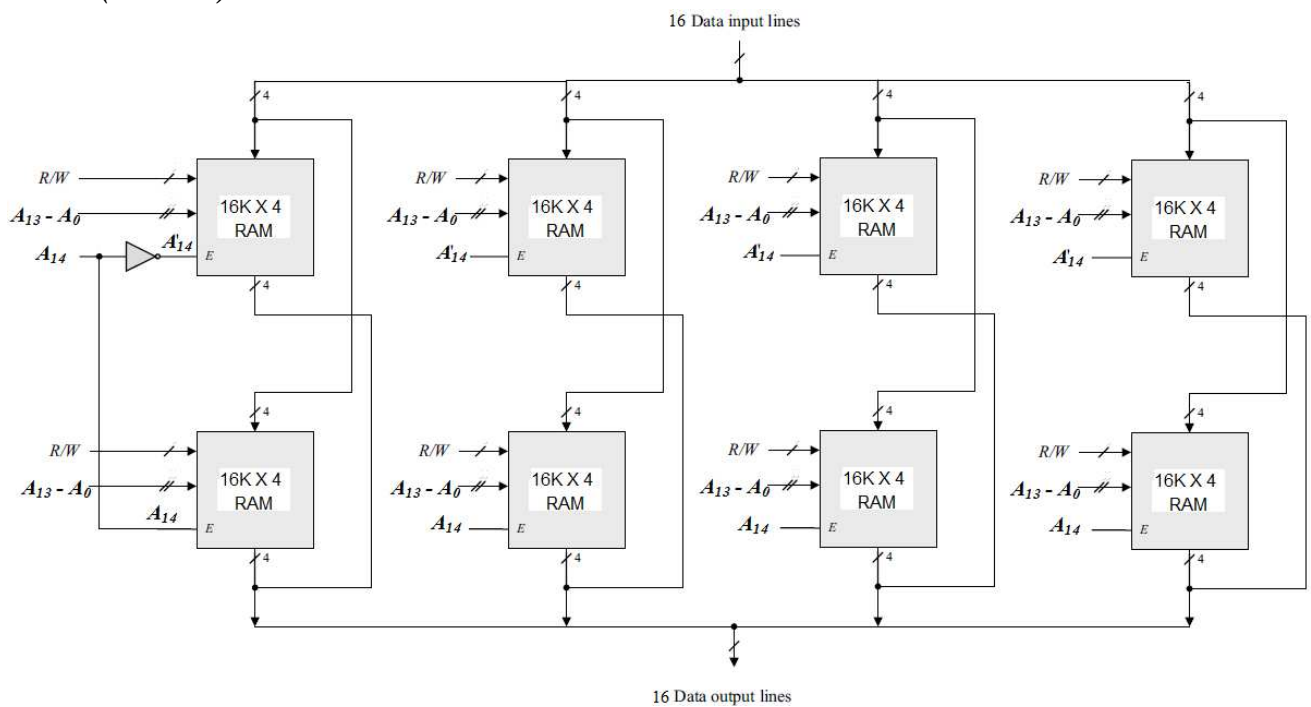- b. Given a 16K X 4 RAM chip with an enable input, show the external connections necessary to construct a 32K X 16 RAM with the 16K X 4 RAM chips and a decoder. (5 Marks)



- c. Given the 8-bit data word 01011011, generate the 13-bit composite word for the Hamming code that corrects single errors and detect double errors. (4 Marks)

01011011 = 1 2 3 4 5 6 7 8 9 10 11 12 13
 $P_1 P_2 0 P_4 1 0 1 P_8 1 0 1 1 P_{13}$

$P_1 = \text{Xor of bits (3, 5, 7, 9, 11)} = 0, 1, 1, 1, 1 = 0$ (Note: even # of 0s)

$P_2 = \text{Xor of bits (3, 6, 7, 10, 11)} = 0, 0, 1, 0, 1 = 0$

$P_4 = \text{Xor of bits (5, 6, 7, 12)} = 1, 0, 1, 1 = 1$ (Note: odd # of 0s)

$P_8 = \text{Xor of bits (9, 10, 11, 12)} = 1, 0, 1, 1 = 1$

Composite 13-bit code word: 0001 1011 1011 1

Question (2)

(11 Marks)


- a. A 4K X 8 memory uses coincident decoding by splitting the internal decoder into X-selection and Y-selection.
1. What is the size of each decoder, and how many AND gates are required for decoding the address? What's the number of inputs per each AND gate? (3 Marks)

$$4 \text{ K} = 2^{12} = 2^6 \times 2^6 = 64 \times 64$$

Each decoder is 6 X 64

Decoders require 128 AND gates, each with 6 inputs

 2. Draw the structure of such two dimensional decoding? Determine the X and Y selection lines that are enabled when the input address is the binary equivalent 3000. (3 Marks)




$$3,000 = 101110_111000$$

$x = 46$ and $y = 56$

- b. Design a combinational circuit using a ROM. The circuit accepts a three-bit number and outputs a binary number equal to the square of the input number. Showing the ROM implementation (i.e. its size and connections with external inputs and outputs) and tabulate its truth table. (5 Marks)

Truth Table for Circuit

Inputs			Outputs						
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	Decimal
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

 

A_2	A_1	A_0	B_5	B_4	B_3	B_2
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table


Question (3)

(10 Marks)

- a. Draw a PLA circuit to implement the functions (4 Marks)

$$F_1 = A'B + AC' + A'BC'$$

$$F_2 = (AC + AB + BC)'$$

 

b. The following is a truth table of a three-input, four-output combinational circuit:

$$A(x, y, z) = \sum (1, 2, 4, 6)$$

$$B(x, y, z) = \sum (0, 1, 3, 6, 7)$$

$$C(x, y, z) = \sum (1, 2, 4, 6, 7)$$

$$D(x, y, z) = \sum (1, 2, 3, 5, 7)$$

Tabulate the PAL programming table for the circuit, and mark its fuse map diagram.

(6 Marks)

		y			
		00	01	11	10
x	0	m_0 0	m_1 1	m_3 0	m_2 1
	1	m_4 1	m_5 0	m_7 0	m_6 1
		z			

$$A = yz' + xz' + x'y'z$$

		y			
		00	01	11	10
x	0	m_0 1	m_1 1	m_3 1	m_2 0
	1	m_4 0	m_5 0	m_7 1	m_6 1
		z			

$$B = x'y' + xy + yz$$

		y			
		00	01	11	10
x	0	m_0 0	m_1 1	m_3 0	m_2 1
	1	m_4 1	m_5 0	m_7 1	m_6 1
		z			


$$C = A + xyz$$

		y			
		00	01	11	10
x	0	m_0 0	m_1 1	m_3 1	m_2 1
	1	m_4 0	m_5 1	m_7 1	m_6 0
		z			

$$D = z + x'y$$

AND				
Product term	x	y	z	A
1	-	1	0	-
2	1	-	0	-
3	0	0	1	-
<hr/>				
4	0	0	-	-
5	1	1	-	-
6	-	1	1	-
<hr/>				
7	-	-	-	1
8	1	1	1	-
<hr/>				
9	-	-	-	-
10	-	-	1	-
11	0	1	-	-
12	-	-	-	-

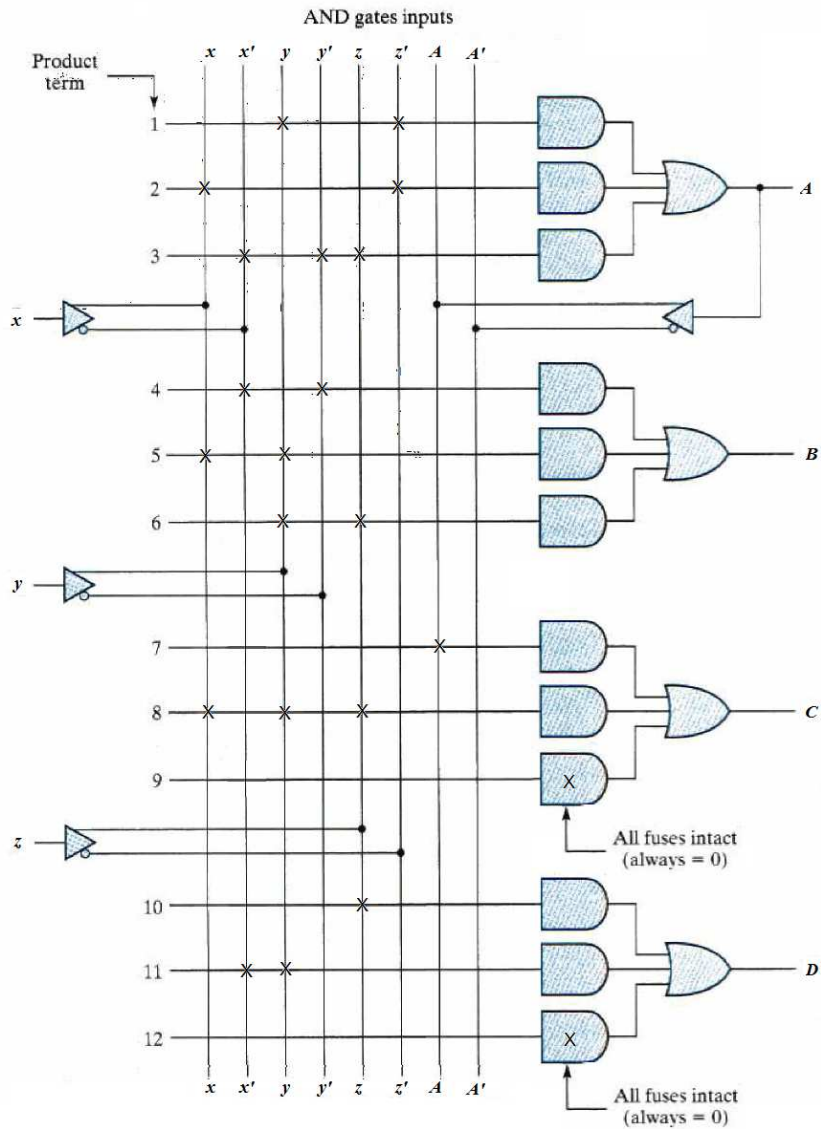
$A = yz' + xz' + x'y'z$
$B = x'y' + xy + yz$
$C = A + xyz$
$D = z + x'y$



Question (4)


(12 Marks)

 - a. Draw the ASMD charts for the following state transition:
 - If $x = 1$, control goes from state S1 to state S2; if $x = 0$, generate a conditional operation to increment R by 2 and go from S1 to S2. **(6 Marks)**




 - b. The state diagram and the register transfer level description of a control unit are shown below. It has 3 states and 3 inputs (Start, A2 and A3)

$S_idle \longrightarrow S_1, clr_A_F:$
 $S_1 \longrightarrow S_1, incr_A:$
 if ($A_2 = 1$) then set_E
 if ($A_2 = 0$) then clr_E
 $S_2 \longrightarrow S_idle, set_F:$



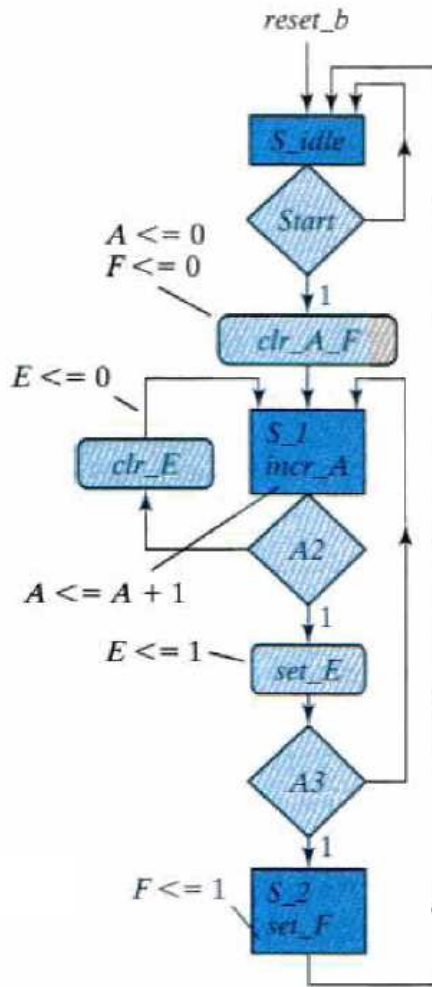1. Draw the equivalent ASMD chart. **(3 Marks)**




2. Design the control circuit with one *D* flip flop per state. (2 Marks)

Design equations:

$$D_{S_idle} = S_2 + S_idle \text{ Start}'$$

$$D_{S_1} = S_idle \text{ Start} + S_1 (A_2 A_3)'$$

$$D_{S_2} = A_2 A_3 S_1$$

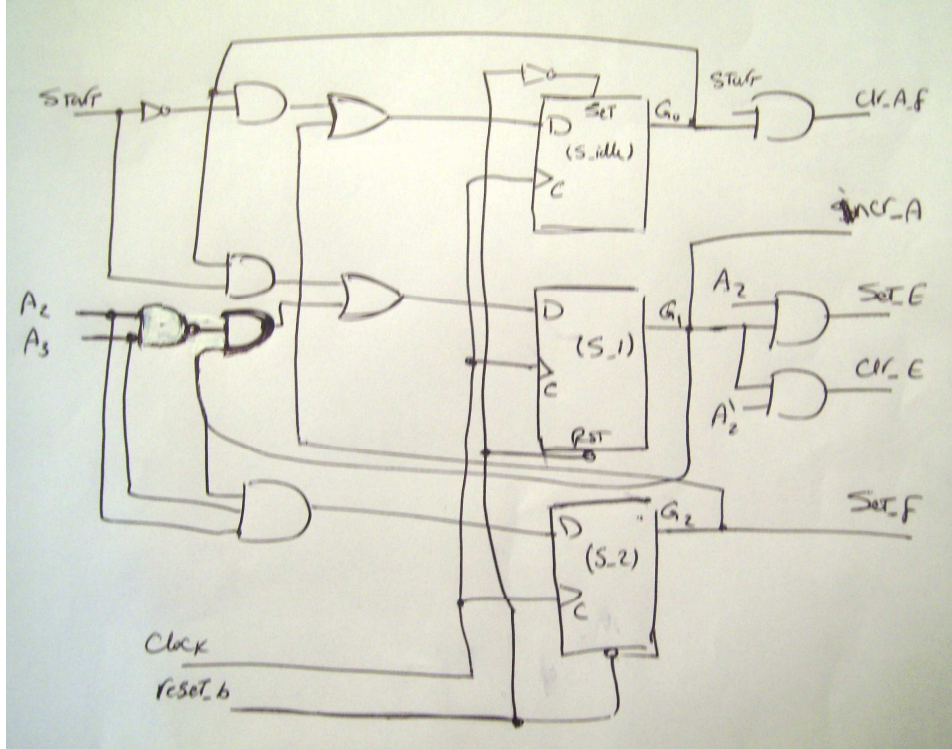

3. Design the control unit with *D* flip flops, a decoder, and gates. (2 Marks)

State Table for the Controller


Present-State Symbol	Present State		Inputs			Next State		Outputs				
	G ₁	G ₀	Start	A ₂	A ₃	G ₁	G ₀	set_E	clr_E	set_F	clr_A_F	incr_A
S_idle	0	0	0	X	X	0	0	0	0	0	0	0
S_idle	0	0	1	X	X	0	1	0	0	0	1	0
S_1	0	1	X	0	X	0	1	0	1	0	0	1
S_1	0	1	X	1	0	0	1	1	0	0	0	1
S_1	0	1	X	1	1	1	1	1	0	0	0	1
S_2	1	1	X	X	X	0	0	0	0	1	0	0

$$DG_0 = Start S_idle + S_1$$

$$DG_1 = S_1 A_2 A_3$$

$$set_E = S_1 A_2 \quad clr_E = S_1 A_2'$$

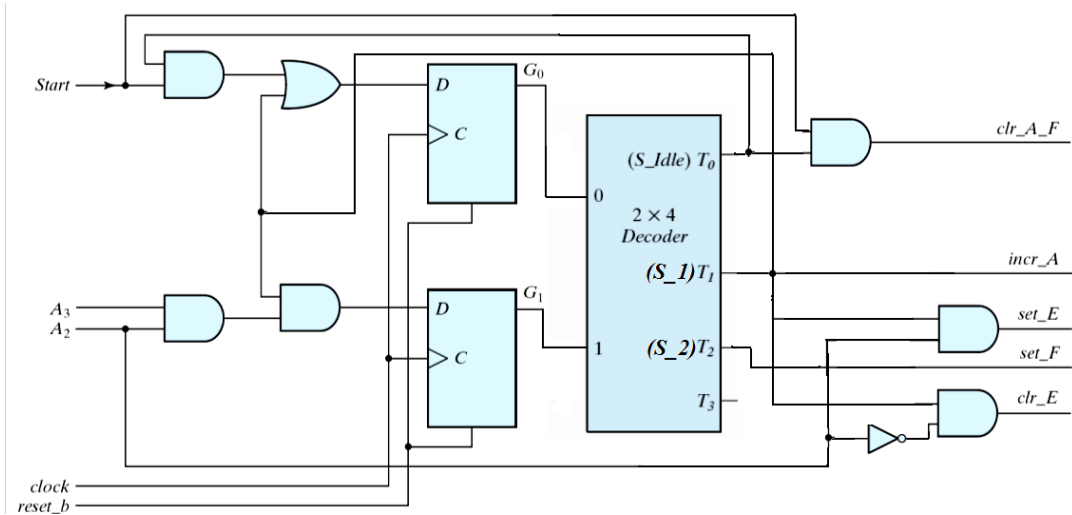
$$set_F = S_2 \quad clr_A_F = Start S_idle \quad incr_A = S_1$$



4. Design the control unit with multiplexers, a register, and a decoder. (2 Marks)

Multiplexer Input Conditions

Present State		Next State		Input Condition	Inputs	
G_1	G_0	G_1	G_0	s	MUX1	MUX2
0	0	0	0	$start'$		
0	0	0	1	$start$	0	$start$
0	1	0	1	A_2'		
0	1	0	1	$A_2 A_3'$	$A_2 A_3$	$(A_2 A_3)'$
0	1	1	0	$A_2 A_3$		
1	0	0	0	None	0	0

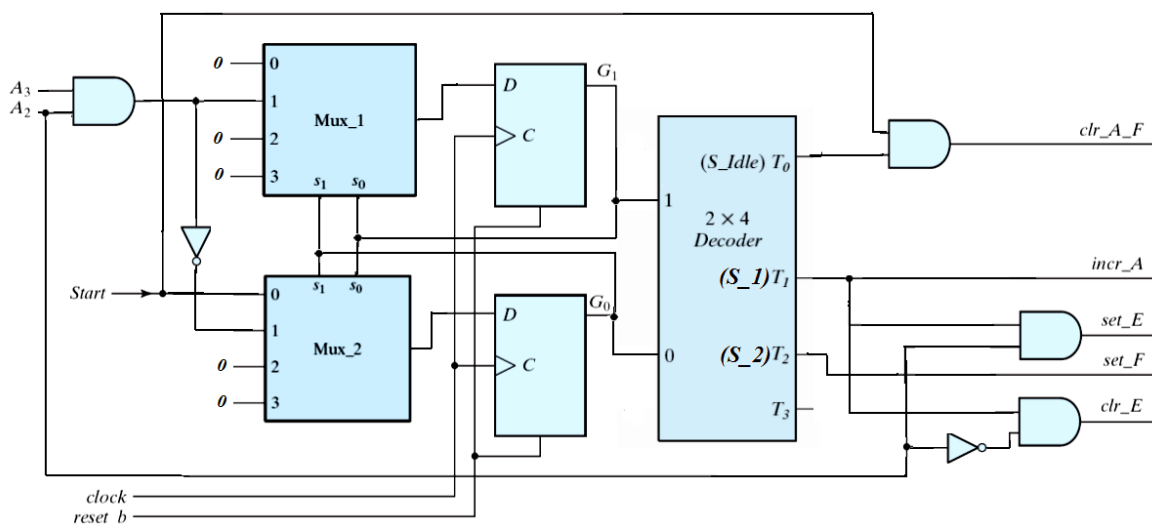

Question (5)

(12 Marks)

- a. Explain the difference between asynchronous and synchronous sequential circuits. **(2 Marks)**

Asynchronous circuits do not use clock pulses and change state in response to input changes.

Synchronous circuits use clock pulses and a change of state occurs in response to the clock transition.

- b. Define the fundamental-mode operation. **(1 Marks)**

The input signals change one at a time when the circuit is stable


- c. An asynchronous sequential circuit has two internal states and one output The two excitation functions and one output function describing the circuit are, respectively,

$$Y_1 = x_1y_2 + x_1y_1 + x_2y_1$$

$$Y_2 = x_1x_2 + x_2y_2 + y_1'y_2$$

$$z = x_2 + y_1$$

 1. Draw the logic diagram of the circuit. **(1 Marks)**



2. Derive the transition table and output map. **(2 Marks)**

$y_1y_2 \backslash x_1x_2$	00	01	11	10
00	00	00	01	00
01	01	01	11	11
11	00	11	11	10
10	00	10	11	10

Transition Table

$y_1y_2 \backslash x_1x_2$	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	1	1	1
10	1	1	1	1

Output Map

3. Determine all race conditions and whether they are critical or noncritical.
(2 Marks)

Investigating the transition table, we deduce that the circuit is stable. There is a critical race condition when the circuit is initially in total state $y_1y_2x_1x_2 = 1101$ ($Y_1Y_2 = 11$) and x_2 changes from 1 to 0 ($Y_1Y_2 = 00$). If Y_1 changes to 0 before Y_2 , the circuit goes to total state 0100 instead of 0000.

4. Implement the circuit with NOR SR latches. (4 Marks)


$$S_1 = x_1y_2 \quad S_2 = x_1x_2$$

$$R_1 = x_1'x_2' \quad R_2 = x_2'y_1$$

We then check whether the condition $SR = 0$ is satisfied to ensure proper operation of the circuit:

$$S_1R_1 = x_1y_2x_1'x_2' = 0$$

$$S_2R_2 = x_1x_2x_2'y_1 = 0$$

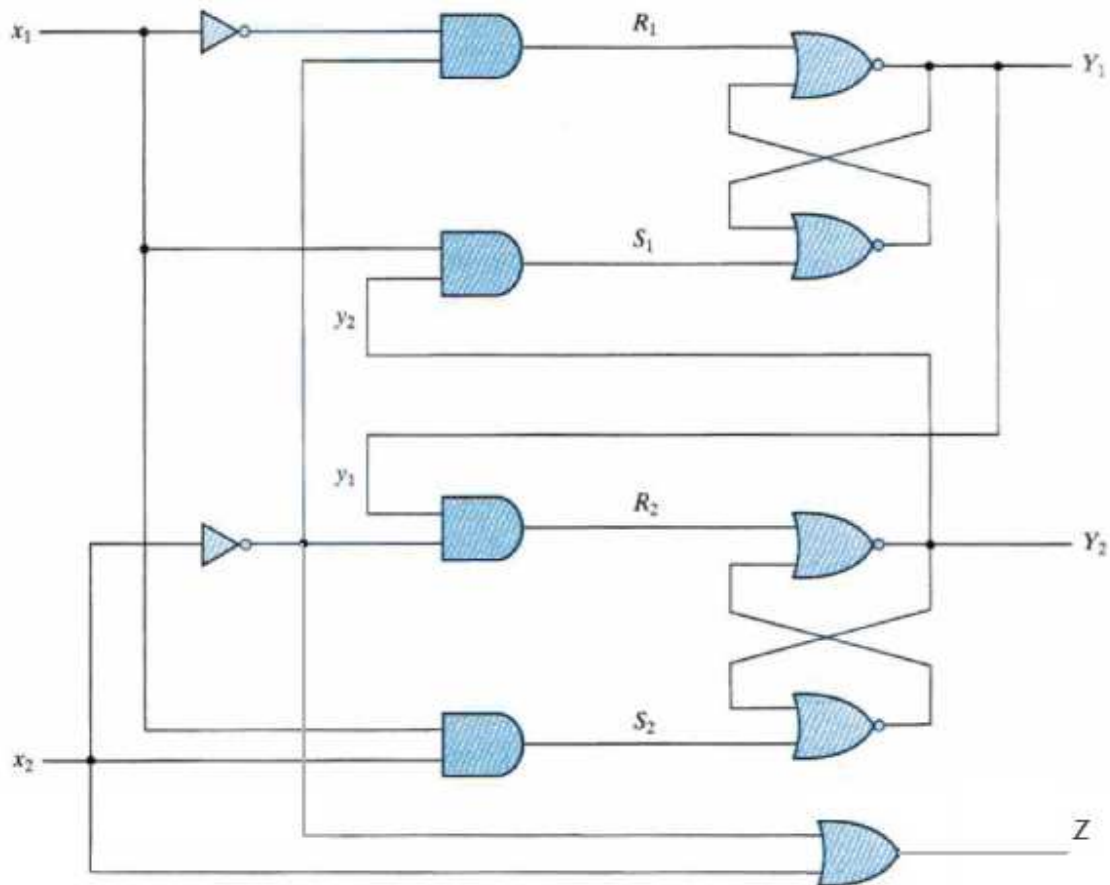

(Good Luck)