

Answer the following questions:

Q1: (a) In the circuit of Fig(1), if V_s is a $20V_p$ square wave of period T , $R_L = R_1 = 10\Omega$, and the diode is ideal, find the average value of V_L .

(b) Analyze the circuit of Fig. (2), to determine the voltages at all nodes and the currents through all branches. Assume that the transistor β is specified to be at least 50.

Q2: (a) Determine and sketch the output waveform for the network of Fig. (3).

(b) The Si Darlington transistor pair of Fig.(4) has $\beta_1 = \beta_2 = 50$. Let $R_2 \rightarrow \infty$ Find the values of R_1 , and V_{CE1} needed to bias the circuit so that $V_{CE2} = 6V$.

Q3: The 6.8V zener diode in the circuit of Fig. (5) is specified to have $V_z = 6.8V$ at $I_z = 5mA$, $r_z = 20\Omega$, and $I_{zk} = 0.2 mA$. The supply voltage V^+ is nominally 10V but can vary by $\pm 1 V$.

- (a) Find V_0 with no load and with V^+ at its nominal value.
- (b) Find the change in V_0 resulting from the $\pm 1 V$ change in V^+ .
- (c) Find the change in V_0 when $R_L = 2 k\Omega$.

(d) What is the minimum value of R_L for which the diode still operates in the breakdown region?

Q4: In the circuit of Fig. (6), v_{sig} is a small sine-wave signal with zero average value. For $V_{CC} = 15V$, $R_1 = R_2 = 100K\Omega$, $R_E = 200 \Omega$, $R_C = R_L = 20 K\Omega$, and $\beta = 100$. Find using hybrid- π model the values of R_{in} , R_o , the voltage gain (v_o/v_{sig}), and the current gain (i_o/i_i).

Q5: The transistor in the circuit shown in fig. (7) is biased to operate in the active mode. Replace the transistor with small-signal equivalent circuit T –model and then find R_{in} , the voltage gain (v_o/v_{sig}), the current gain (i_o/i_i), and the output resistance R_{out} . Assuming that $\beta = 100$.

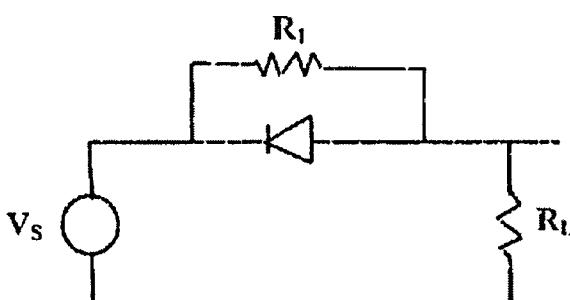


Fig.(1)

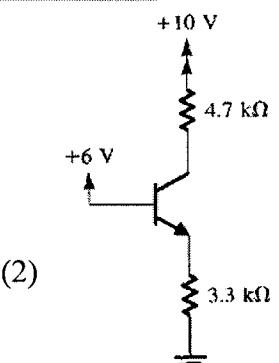


Fig.(2)

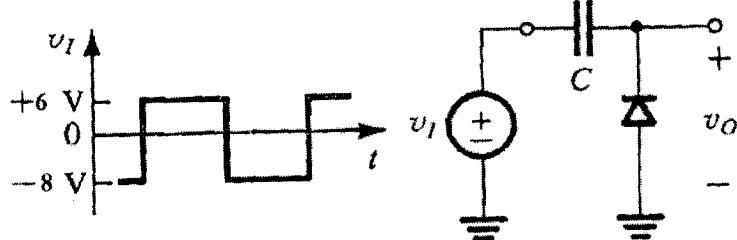


Fig.(3)

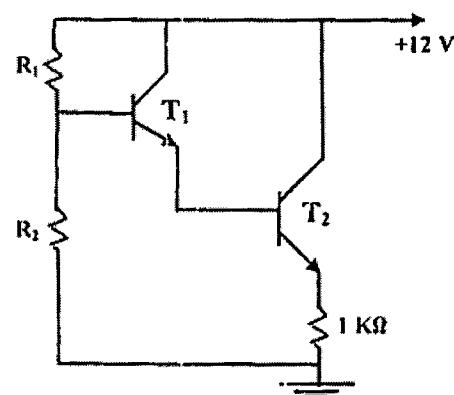


Fig.(4)

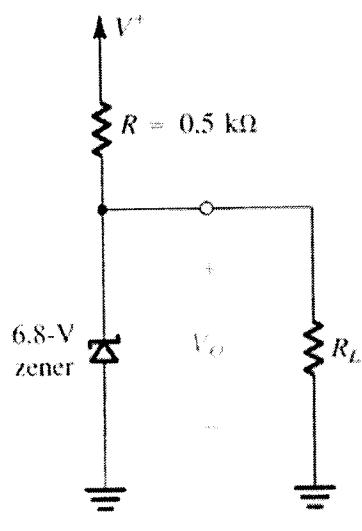


Fig.(5)

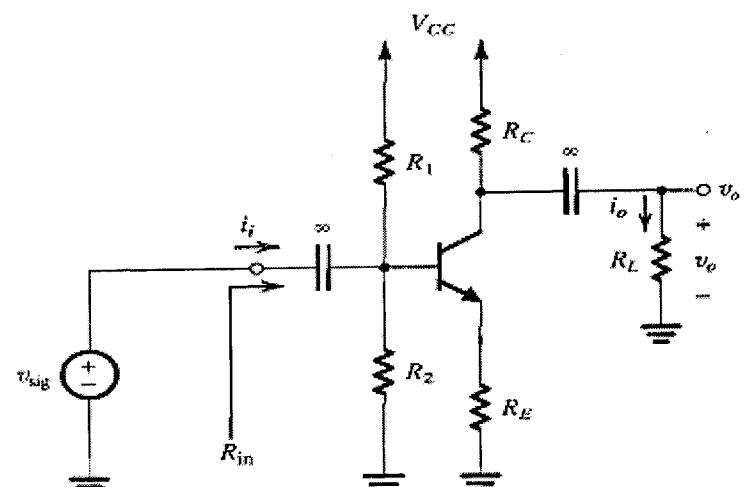


Fig.(6)

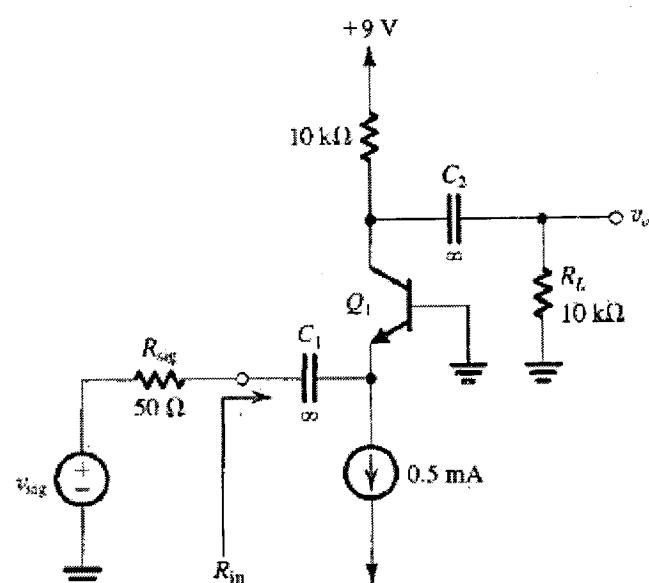



Fig.(7)

BEST WISHES
Hosam Labib

Model Answer

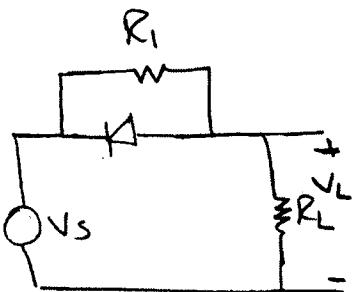
Q21: (a) (6 points)

In the circuit shown, if V_s is $20V_p$ square wave of period T , $R_L = R_1 = 10\Omega$, and the diode is ideal, find the average value of V_L .



Solution

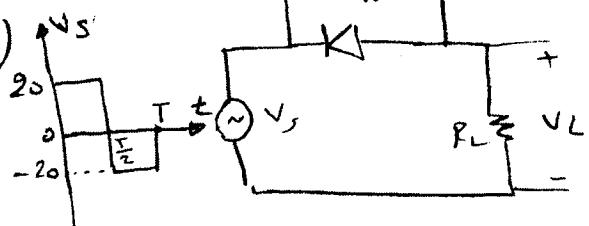- From $t=0 : \frac{T}{2}$ (i.e. +ve half cycle)
The diode is off and the circuit becomes:-





$$\therefore V_L = V_s \frac{R_L}{R_L + R_1} = 20 \frac{10}{10 + 10} = 10V$$

- For $t = \frac{T}{2} : T$ (i.e. -ve half cycle)

The diode is on and the circuit becomes:-

$$V_L = V_s = -20V$$

$\therefore V_L$ is

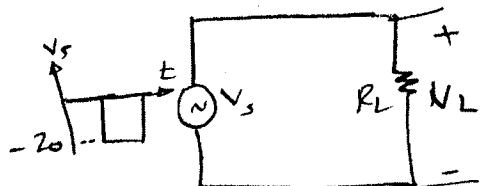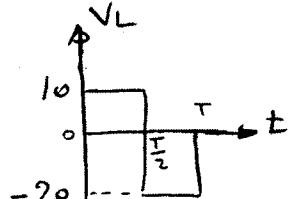

$$\begin{aligned} V_{L\text{ave}} &= \frac{1}{T} \int_0^T V_L(t) dt = \frac{1}{T} \left[\int_0^{\frac{T}{2}} 10 dt + \int_{\frac{T}{2}}^T -20 dt \right] \\ &= \frac{1}{T} \left[10t \Big|_0^{\frac{T}{2}} - 20t \Big|_{\frac{T}{2}}^T \right] \\ &= \frac{1}{T} \left[(10 \frac{T}{2} - 0) - (20T - 20 \frac{T}{2}) \right] \\ &= \frac{1}{T} [5T - 20T + 10T] \\ &= \frac{1}{T} [-5T] = -5V \end{aligned}$$

$$\therefore V_{L\text{ave}} = -5V$$

①

Q2: (b) (6 points)

Analyze the circuit of Fig. (2), to determine the voltages at all nodes and the currents through all branches. Assume that the transistor β is specified to be at least 50.


Solution

Let Transistor In Active Region

Loop (I)

$$-6 + V_{BE} + 3.3k \times I_E = 0$$
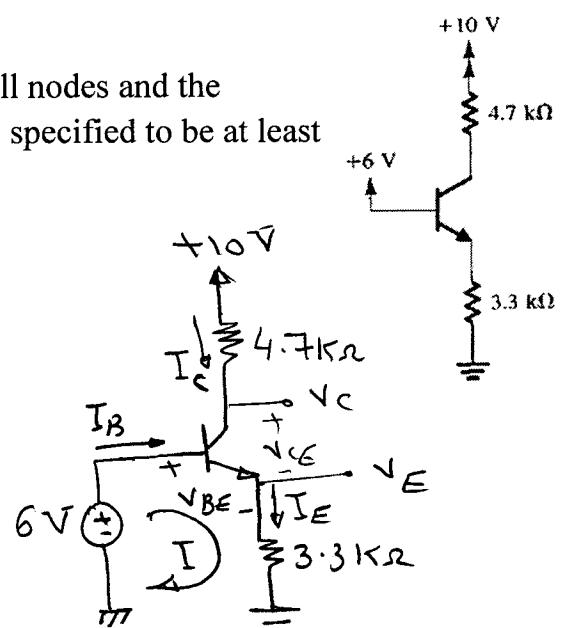
$$\therefore I_E = \frac{6 - V_{BE}}{3.3k} = \frac{6 - 0.7}{3.3k} = 1.6 \text{ mA}$$



$$\text{let } I_E = I_C \Rightarrow V_C = 10 - I_C \times 4.7k$$

$$V_C = 10 - 1.6 \times 4.7 = 2.48 \text{ V}$$

$$\therefore V_B = 6 \text{ V} \quad ; \quad V_E = V_B - V_{BE} = 6 - 0.7 = 5.3 \text{ V}$$

$\therefore V_B > V_E \Rightarrow EBJ \text{ Forward.}$

$\therefore V_B > V_C \Rightarrow CBJ \text{ Forward}$

\therefore Transistor In saturation Region not active Region

\therefore assumption not True

For saturation region $\Rightarrow |V_{CE}|_{sat} \approx 0.2 \text{ V}$

$$\therefore V_C = |V_{CE}|_{sat} + V_E = 0.2 + 5.3 = 5.5 \text{ V}$$

$$\therefore I_C = \frac{10 - V_C}{4.7k} = \frac{10 - 5.5}{4.7k} = 0.96 \text{ mA}$$

$$\therefore EBJ \text{ Forward.} \Rightarrow I_E = 1.6 \text{ mA} \quad ; \quad V_{BE} = 0.7 \quad ; \quad V_E = 5.3 \text{ V}$$


$$\therefore I_B = I_E - I_C = 1.6 \text{ mA} - 0.96 \text{ mA} = 0.64 \text{ mA}$$

$$\beta_{\text{forced}} = \frac{|I_C|_{sat}}{|I_B|_{sat}} = \frac{0.96 \text{ mA}}{0.64 \text{ mA}} = 1.5$$

- Since β_{forced} is less than min. value of β , Then The Transistor is in fact saturated

Q2: (12 points)

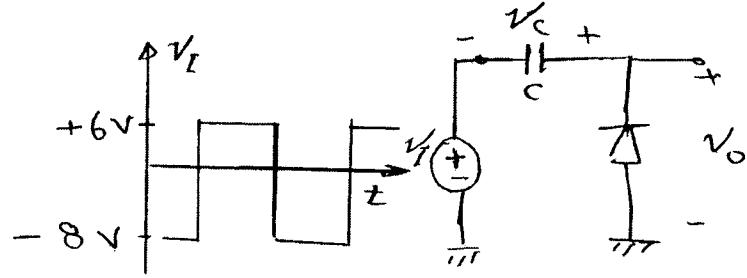
Q2:(a) Determine and sketch the output waveform for the network shown



$$V_c = 8 \text{ V}$$

$$V_o = V_i + V_c \quad \text{i.e } V_o = V_i + \text{shifted by -ve half cycle}$$

$$= V_i + 8$$

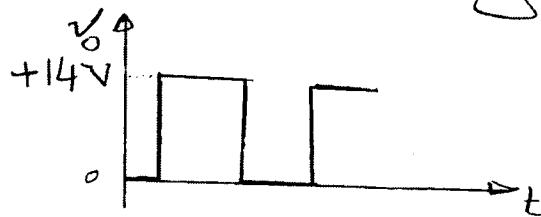

Q2: (b)

The Si Darlington Transistor pair shown has $B_1 = B_2 = 50$. Let $R_2 \rightarrow \infty$.

Find the values of R_1 , and V_{CE_1} needed to bias the circuit so that $V_{CE_2} = 6 \text{ V}$

Solution

For $R_2 \rightarrow \infty \Rightarrow I_2 = 0$

$$\therefore I_1 = I_{B_1}$$

$$\therefore I_{E_1} = I_{B_2}$$

$$\therefore V_{CE_2} = 6 = V_{C_2} - V_{E_2}$$

$$\therefore V_{E_2} = V_{C_2} - 6$$



$$V_{C_2} = V_{C_1} = V_{CC} = 12 \text{ V}$$

$$\therefore V_{E_2} = 12 - 6 = 6 \text{ V}$$

$$\therefore I_{E_2} = \frac{V_{E_2}}{R_E} = \frac{6}{1K} = 6 \text{ mA}$$

$$\therefore I_{B_2} = I_{E_1} = \frac{I_{E_2}}{1+B_2} = \frac{6 \text{ mA}}{1+50} = 0.118 \text{ mA}$$

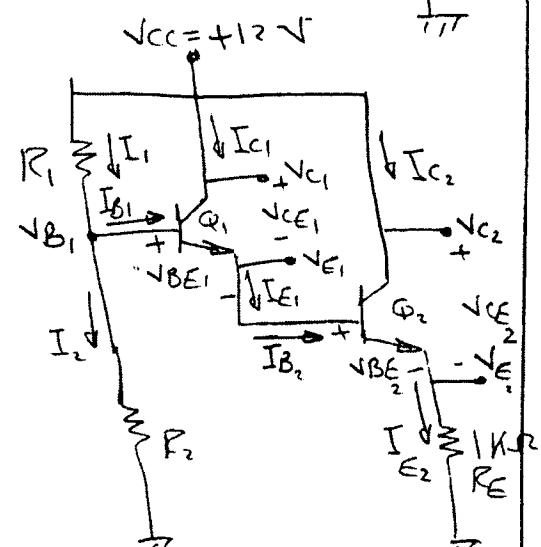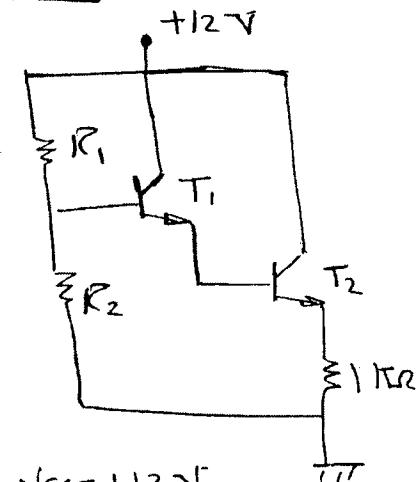
$$I_{B_1} = \frac{I_{E_1}}{1+B_1} = \frac{0.118 \text{ mA}}{1+50} = 2.314 \text{ mA}$$



(3)

Q2: (12 points)

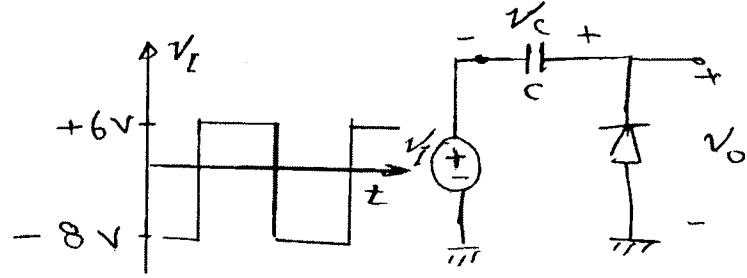
Q2: (a) Determine and sketch the output waveform for the network shown



$$V_c = 8 \text{ V}$$

$$V_o = V_i + V_c \quad \text{i.e. } V_o = V_i + \text{shifted by -ve half cycle}$$

$$= V_i + 8$$

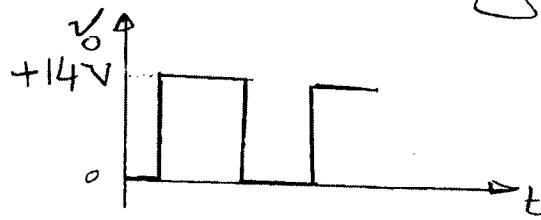

Q2: (b)

The Si Darlington Transistor pair shown has $B_1 = B_2 = 50$. Let $R_2 \rightarrow \infty$.

Find the values of R_1 , and V_{CE_1} needed to bias the circuit so that $V_{CE_2} = 6 \text{ V}$

Solution

For $R_2 \rightarrow \infty \Rightarrow I_2 = 0$

$$\therefore I_1 = I_{B_1}$$

$$\therefore I_{E_1} = I_{B_2}$$

$$\therefore V_{CE_2} = 6 = V_{C_2} - V_{E_2}$$

$$\therefore V_{E_2} = V_{C_2} - 6$$



$$V_{C_2} = V_{C_1} = V_{CC} = 12 \text{ V}$$

$$\therefore V_{E_2} = 12 - 6 = 6 \text{ V}$$

$$\therefore I_{E_2} = \frac{V_{E_2}}{R_E} = \frac{6}{1\text{K}} = 6 \text{ mA}$$

$$\therefore I_{B_2} = I_{E_1} = \frac{I_{E_2}}{1+B_2} = \frac{6 \text{ mA}}{1+50} = 0.118 \text{ mA}$$
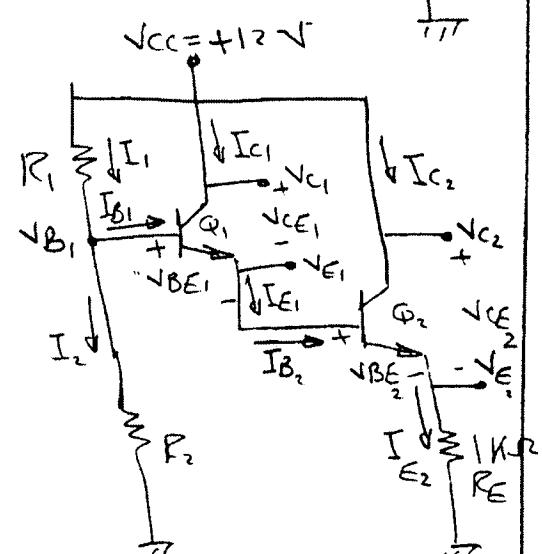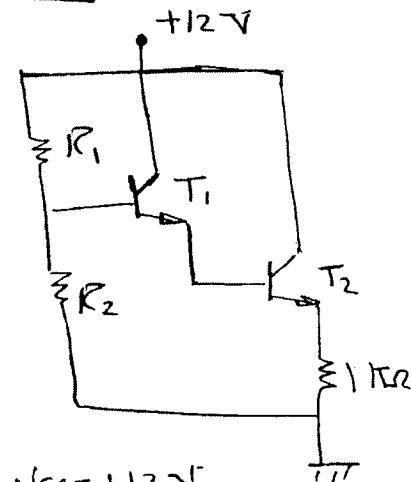
$$I_{R_1} = \frac{I_{E_1}}{1+B_1} = \frac{0.118 \text{ mA}}{1+50} = 2.314 \text{ mA}$$



(3)

Q2: (b) (cont.)

$$R_1 = \frac{V_{CC} - V_{B1}}{I_1}$$

$$\begin{aligned} V_{B1} &= V_{BE1} + V_{BE2} + V_{E1} \\ &= 0.7 + 0.7 + 6 = 7.4 \text{ V} \end{aligned}$$

$$\therefore R_1 = \frac{12 - 7.4}{2.314 \mu A} = 1.99 \text{ k}\Omega$$

$$\begin{aligned} \therefore V_{E1} &= V_{BE2} + V_{E2} \\ &= 0.7 + 6 = 6.7 \text{ V} \end{aligned}$$

$$\begin{aligned} \therefore V_{CE1} &= V_C - V_{E1} \\ &= 12 - 6.7 = 5.3 \text{ V} \end{aligned}$$

Q3:- (12 points)

The 6.8V Zener diode in the circuit shown is specified to have $V_Z = 6.8V$ at $I_Z = 5mA$, $r_Z = 20\Omega$, and $I_{ZK} = 0.1mA$. The supply voltage V^+ is nominally 10V but can vary by $\pm 1V$.

(a) Find V_o with no load and with V^+ at its nominal value.

$$\therefore V_Z = V_{Z0} + V_Z I_Z$$

$$6.8 = V_{Z0} + 20 * 5 * 10^{-3}$$

$$\therefore V_{Z0} = 6.8 - 0.1 = 6.7V$$

With no load i.e. $R_L = \infty$

$$I = I_Z = \frac{V^+ - V_{Z0}}{R + r_Z}$$

$$= \frac{10 - 6.7}{0.5K + 20} = 6.35mA$$

$$\therefore V_o = V_{Z0} + I_Z r_Z$$

$$= 6.7 + 6.35 * 20 = 6.83V$$

(b) Find the change in V_o resulting from the $\pm 1V$ change in V^+ .

The change in V_o can be found from

$$\Delta V_o = \Delta V^+ \frac{r_Z}{R + r_Z}$$

$$= \pm 1 * \frac{20}{0.5K + 20} = \pm 38.5mV$$

(c) Find the change in V_o when $R_L = 2K\Omega$




If $R_L = 2K\Omega$ is connected

$$\therefore I_L \leq \frac{V_Z}{R_L} = \frac{6.8}{2K} = 3.4mA$$

$$I = \frac{10 - 6.8}{0.5K} = 6.4mA$$

$$\therefore I = I_Z + I_L \Rightarrow I_Z|_{\text{loaded}} = I - I_L =$$

$$I_Z|_{\text{loaded}} = 6.4mA - 3.4mA = 3mA$$

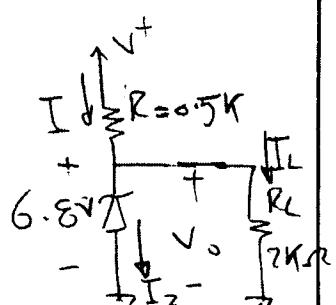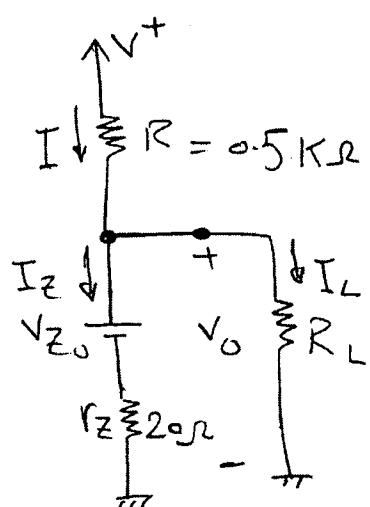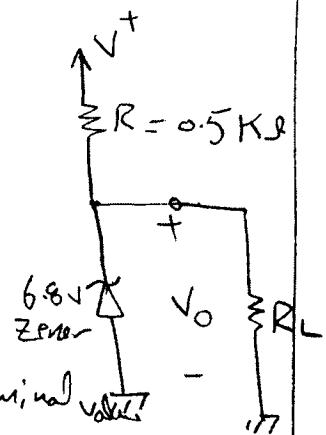

Q3: (cont.)

$$\text{Change in Zener current } \Delta I_Z = I_Z|_{\text{Load}} - I_Z|_{\text{No-Load}}$$

$$\Delta I_Z = 3 - 6.35 = -3.4 \text{ mA}$$

$\therefore \text{change in } V_o \Rightarrow \Delta V_o = \Delta I_Z V_Z$

$$\Delta V_o = -3.4 \text{ m} \times 20 = -68 \text{ mV}$$

(d) What is the min. value of R_L for which the diode still operates in the breakdown region?

For the Zener at edge of the breakdown region then
 $I_Z = I_{ZK} = 0.2 \text{ mA}$ and $V_{Zo} \approx V_{ZK} \approx 6.7 \text{ V}$

\therefore AT This point the lowest current supplied through R is

$$I = \frac{V^+ - V_{ZK}}{R}$$

$$= \frac{9 - 6.7}{0.5 \text{ n}} = 4.6 \text{ mA}$$

$$\therefore I_L = I - I_Z = 4.6 - 0.2 = 4.4 \text{ mA}$$

$$R_L|_{\min} = \frac{V_o}{I_L} \approx \frac{V_Z}{I_L}$$

$$= \frac{6.7}{4.4 \text{ mA}} = 1.5 \text{ k}\Omega$$


Q4: (12 Points)

In the circuit of Fig. (4), V_{sig} is a small sine-wave signal with zero average value. For $V_{CC} = 15 \text{ V}$, $R_1 = R_2 = 100 \text{ k}\Omega$, $R_E = 200 \text{ }\mu\Omega$

$$R_C = R_L = 20 \text{ k}\Omega, \text{ and } B = 100.$$

Using Hybrid- π model find the values of R_{in} , R_o , the voltage gain ($\frac{V_o}{V_{sig}}$), and the current gain ($\frac{I_o}{I_i}$).

Solution

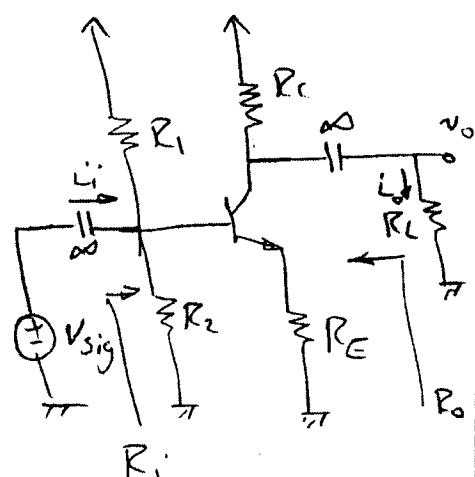

DC Analysis


- All cap. o.c

- Reduce AC sources

$$R_{Th} = R_1 // R_2$$

$$= 100 \text{ k} // 100 \text{ k} = 50 \text{ k}\Omega.$$
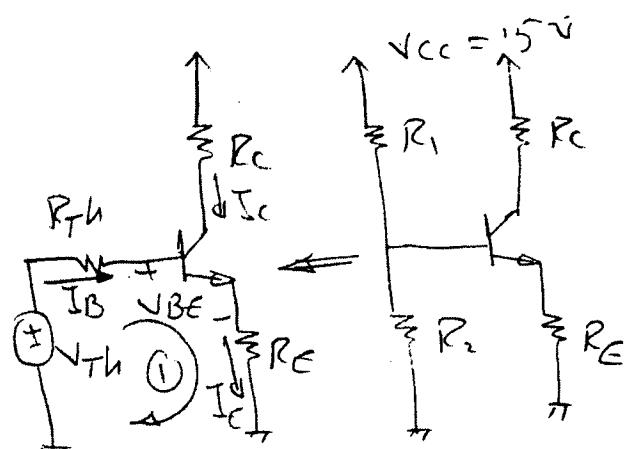
$$V_{Th} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{15 * 100 \text{ k}}{100 \text{ k} + 100 \text{ k}} = 7.5 \text{ V}$$



Loop (1)

$$-V_{Th} + I_B R_{Th} + V_{BE} + I_E R_E = 0$$

$$\therefore I_E = (1+B) I_B$$

$$-V_{Th} + I_B R_{Th} + V_{BE} + (1+B) I_B R_E = 0$$

$$I_B (R_{Th} + (1+B) R_E) = V_{Th} - V_{BE}$$

$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (1+B) R_E} = \frac{7.5 - 0.7}{50 \text{ k} + 101 * 200} = 96.87 \text{ mA}$$

$$I_C = B I_B = 100 * 96.87 \text{ mA} = 9.687 \text{ mA}$$




$$g_m = \frac{I_C}{V_T} = \frac{9.687 \text{ mA}}{25 \text{ m}} = 0.388 \text{ A/V}$$

$$r_{\pi} = \frac{B}{g_m} = \frac{100}{0.388} = 258 \text{ }\Omega$$

AC Analysis

- ALL cap. sc & reduce DC-sources

Q4: (cont.)

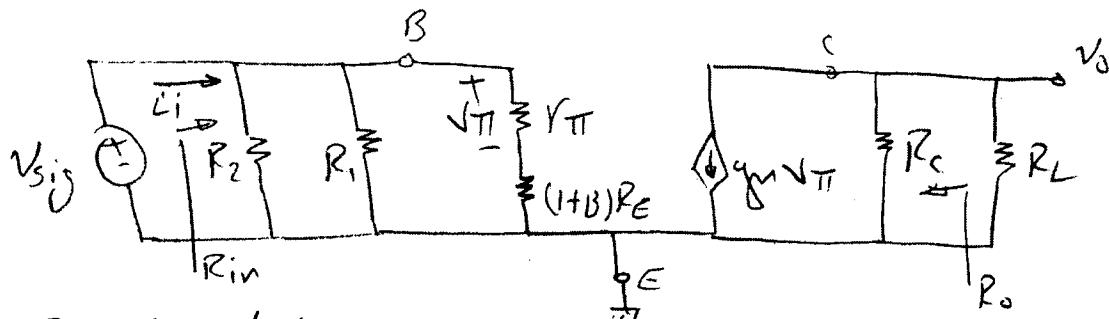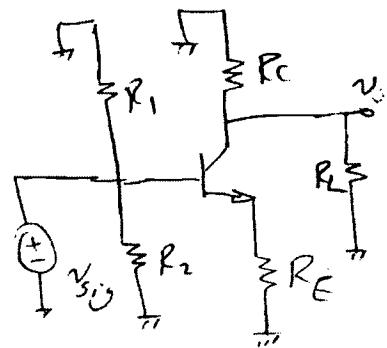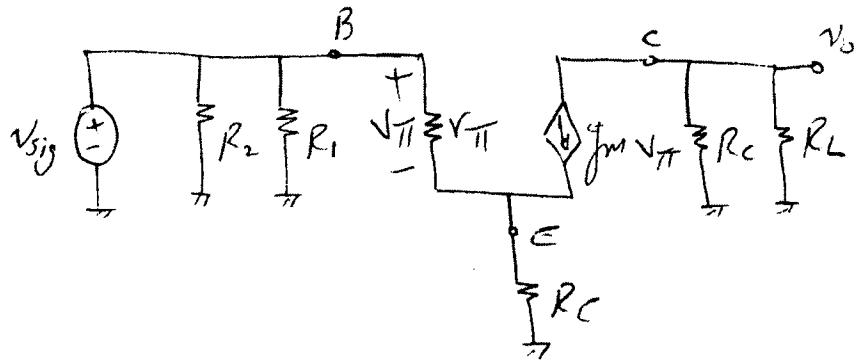

$$R_{in} = R_1 \parallel R_2 \parallel (r_{pi} + (1+B)R_E)$$

$$= 100K \parallel 100K \parallel (258 + 101 \times 200)$$

$$= 50K \parallel 20 \cdot 458K = 14.5K\Omega$$

$$R_o = R_c = 20K\Omega$$

$$V_{sig} = 0$$

$$V_0 = -g_m \sqrt{r_{pi}} (R_c \parallel R_L)$$

$$\sqrt{r_{pi}} = V_{sig} \frac{r_{pi}}{r_{pi} + (1+B)R_E}$$

$$V_0 = -g_m V_{sig} \frac{r_{pi} (R_c \parallel R_L)}{r_{pi} + (1+B)R_E}$$

$$A_v = \frac{V_0}{V_{sig}} = -g_m r_{pi} \frac{R_c \parallel R_L}{r_{pi} + (1+B)R_E} = -g_m \frac{B}{g_m} \frac{R_c \parallel R_L}{r_{pi} + (1+B)R_E}$$

$$= -100 \frac{(20K \parallel 20K)}{258 + 101 \times 200} = -48.88 \text{ V/V}$$

$$I_0 = -g_m \sqrt{r_{pi}} \frac{R_c}{R_c + R_L}$$

$$\therefore V_{sig} = I_i R_{in} \quad ; \quad \sqrt{r_{pi}} = V_{sig} \frac{r_{pi}}{r_{pi} + (1+B)R_E}$$

$$\therefore \sqrt{r_{pi}} = I_i R_{in} \frac{r_{pi}}{r_{pi} + (1+B)R_E}$$

$$I_0 = -g_m \left(I_i R_{in} \frac{r_{pi}}{r_{pi} + (1+B)R_E} \right) \frac{R_c}{R_c + R_L}$$

$$A_i = \frac{I_0}{I_i} = -g_m R_i \left(\frac{r_{pi}}{r_{pi} + (1+B)R_E} \right) \frac{R_c}{R_c + R_L} = -0.388 \times 14.5K \frac{258}{258 + 101 \times 200} \times \frac{20K}{40K}$$

$$= -35.5 \text{ A/A}$$

Q5: (12 points)

The Transistor in the circuit shown is biased to operate in the Active mode. Replace the Transistor with small-signal equivalent circuit T-mode and then find R_{in} , the voltage gain (V_o/V_{sig}), the current gain (I_o/I_i) and the output resistance R_{out} . Assuming that $\beta = 100$.

Solution

DC Analysis

- Reduce AC sources
- ALL capacitors are o.c

$$I_E = I = 0.5 \text{ mA}$$



$$I_C = \alpha I_E = \frac{\beta}{1+\beta} I_E = \frac{10}{101} * 0.5 \text{ mA} \\ = 0.495 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.495 \text{ mA}}{25 \text{ m}} = 19.8 \text{ mA/V}$$

$$V_E = \frac{V_T}{I_E} = \frac{25 \text{ m}}{0.5 \text{ mA}} = 50 \Omega$$

AC Analysis

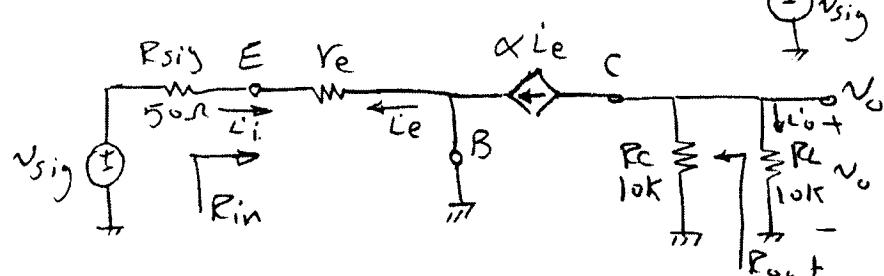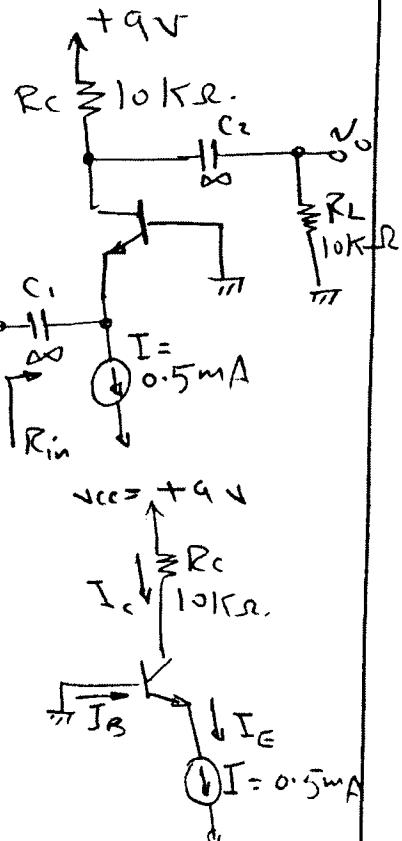- Reduce DC Sources
- ALL capacitors are s.c



$$R_{in} = V_E = 50 \Omega$$

$$\left. \frac{R_{out}}{V_{sig}=0} \right| = R_C = 10 \text{ k}\Omega$$

(9)

Q5: (Cont.)

To find $A_v = \frac{V_o}{V_{sig}}$

$$V_o = -\alpha i_e (R_C \parallel R_L)$$

$$i_e = -\frac{V_{sig}}{R_{sig} + r_e}$$

$$V_o = +\alpha \frac{V_{sig}}{R_{sig} + r_e} (R_C \parallel R_L)$$

$$\begin{aligned} \frac{V_o}{V_{sig}} &= \alpha \frac{(R_C \parallel R_L)}{R_{sig} + r_e} \\ &= (0.99) \frac{(10k \parallel 10k)}{50 + 50} \\ &= (0.99) \frac{5k}{100} = 49.5 \text{ V/V} \end{aligned}$$

To find $A_L = \frac{V_o}{i_i}$

$$i_o = -\alpha i_e \frac{R_C}{R_C + R_L}$$

$$i_e = -i_i$$

$$i_o = +\alpha i_i \frac{R_C}{R_C + R_L}$$

$$\begin{aligned} A_L &= \frac{i_o}{i_i} = \alpha \frac{R_C}{R_C + R_L} \\ &= (0.99) \frac{10k}{10k + 10k} = 0.495 \text{ A/A} \end{aligned}$$
