



Answer the following questions:

Q1: Complete the following sentences:

- i. is the maximum voltage appearing across the diode in reverse bias.
- ii. The output frequency of a full-wave rectifier with a 60 Hz sinusoidal input is.....Hz
- iii. Diode..... add a DC level to an AC voltage.
- iv. If the load resistance of a capacitor filtered full wave rectifier is reduced, the ripple voltages
- v. The DC value of a full wave rectifier voltage with a peak value of 200 is..... .
- vi. The PIV of the bridge rectifier is about.....the value for the center tapped transformer.
- vii. A transistor can be operated as an electronic switch in and.....region.
- viii. The bias methods for discrete BJT circuit are using , , and
- ix. In common base amplifier, the input and output voltages are..... phase.
- x. In common emitter amplifier the gainwith the emitter resistance.
- xi. The maximum current gain is one in the amplifier.
- xii. The maximum voltage gain is one in the amplifier.

Q2: (a) In fig.(1), what is the maximum positive and negative output voltages with $V_i = 20\sin(\omega t)$? Sketch the output waveform. Assume the diode is actual.
(b) The transistor parameters for the circuit in Figure (2) are $\beta_1 = 120$, $\beta_2 = 80$, $V_{BE1(on)} = V_{BE2(on)} = 0.7$ V. Determine the quiescent collector current in each transistor.

Q3: The parameters of the zener diode for the voltage regulator circuit of Fig.(3) are $V_Z=4.7$ V at test current $I_{ZT} = 53$ mA, $r_Z = 8\Omega$, and $I_{ZK} = 1$ mA. The supply voltage is $V_S = 12 \pm 2$ V, and $R_s=220\Omega$.

- a) Find the nominal value of the output voltage v_O under no-load condition R_L .
- b) Find the maximum and minimum values of the output voltage for a load resistance of $R_L=470\Omega$.
- c) Find the nominal value of the output voltage v_O for a load resistance of $R_L = 100\Omega$.
- d) Find the minimum value of R_L for which the zener diode operates in the breakdown region.

Q4: For the amplifier shown in Fig.(4) , $\beta = 80$ and $V_A = 150$ V. (a) Determine the dc voltages at the base and emitter terminals. (b) Using the small signal hybrid π -model calculate the values of R_{in} , R_o , the voltage gain (v_o/v_s) and the current gain $A_i = (i_o/i_s)$.

Q5: The parameters of the amplifier circuit shown in Figure (5) are $V_{cc} = 15V$, $R_{C1} = R_{C2} = 1k\Omega$, $R_1 = R_3 = 65k\Omega$, $R_2 = R_4 = 25k\Omega$, $R_{E1} = R_{E2} = 400\Omega$, $R_L = 20k\Omega$, and $C_1 = C_2 = C_3 = C_E \approx \infty$. Assume, identical transistors of $\beta=100$ and $V_A=100$ V. Calculate the input resistance R_i , the output resistance R_o , and the overall voltage gain $A_v = (v_o/v_s)$.

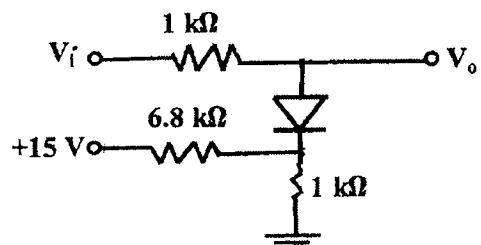


Fig.(1)

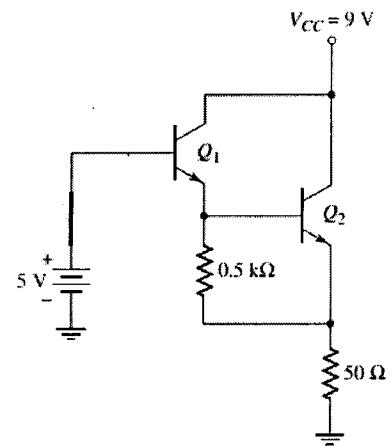


Fig.(2)

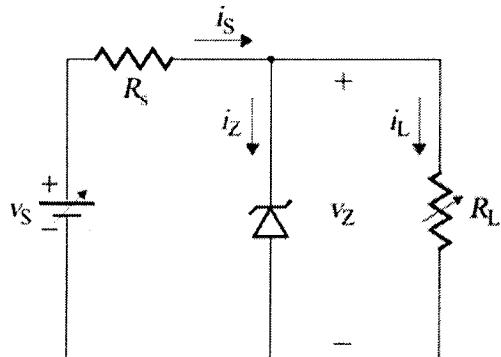


Fig.(3)

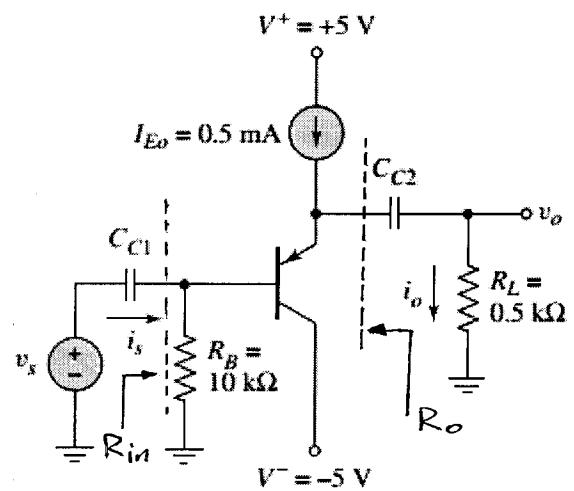


Fig.(4)

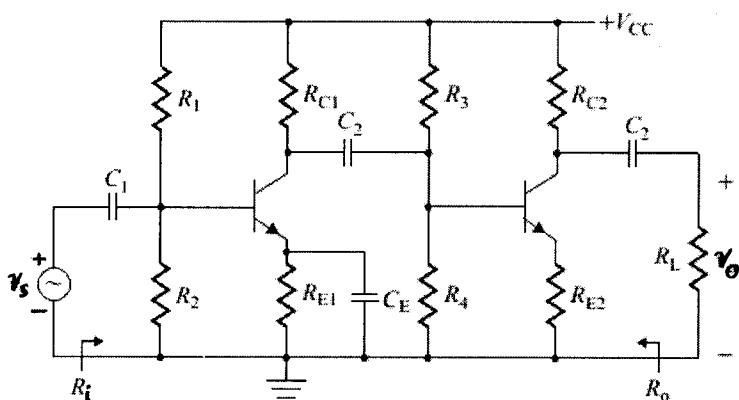


Fig.(5)

BEST WISHES

Hossam Labib




Answer the following questions:

Q1: Complete the following sentences:

- i. PIV is the maximum voltage appearing across the diode in reverse bias.
- ii. The output frequency of a full-wave rectifier with a 60 Hz sinusoidal input is 120 Hz
- iii. Diode clampers add a DC level to an AC voltage.
- iv. If the load resistance of a capacitor filtered full wave rectifier is reduced, the ripple voltages increase.
- v. The DC value of a full wave rectifier voltage with a peak value of 200 is ($V_{dc}=2*V_m/\pi=400/\pi=127.324V$).
- vi. The PIV of the bridge rectifier is about half the value for the center tapped transformer.
- vii. A transistor can be operated as an electronic switch in cut off and saturation region.
- viii. The bias methods for discrete BJT circuit are using single power supply (voltage divider bias), using two power supplies ,and using a collector-to- base feedback resistor, OR using constant current source.
- ix. In common base amplifier, the input and output voltages are in phase.
- x. In common emitter amplifier the gain decreases with the emitter resistance.
- xi. The maximum current gain is one in the common base amplifier.
- xii. The maximum voltage gain is one in the common collector amplifier.

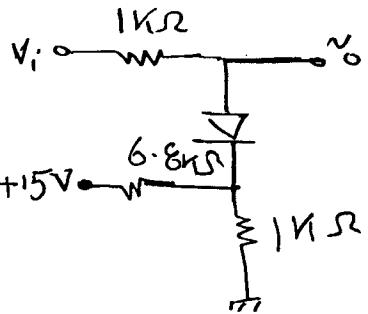Q2:



① In Fig. shown what is the maximum positive and negative o/p voltages with $v_i = 20 \sin(\omega t)$? Sketch the o/p waveform. Assume the diode is actual.



Solution

$$V_{bias} = \frac{15 \times 1k}{(6.8 + 1)k} = 1.9V \rightarrow ②$$

Then the circuit is +ve biased clipper

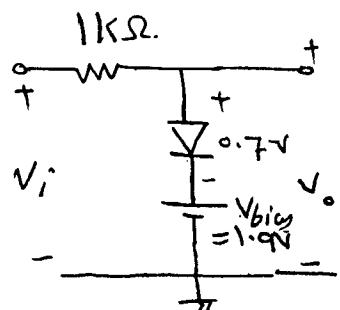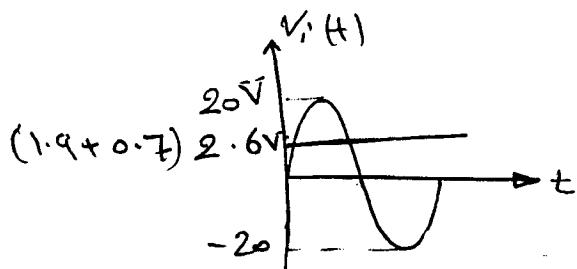


for $v_i < 2.6V \Rightarrow$ Diode is off $\Rightarrow v_o = v_i$

for $v_i > 2.6V \Rightarrow$ Diode is on $\Rightarrow v_o = 2.6V$

$$v_o|_{\substack{\text{max} \\ \text{+ve}}} = 2.6V \rightarrow ①.5$$

$$v_o|_{\substack{\text{max} \\ \text{-ve}}} = -20V \rightarrow ①.5$$

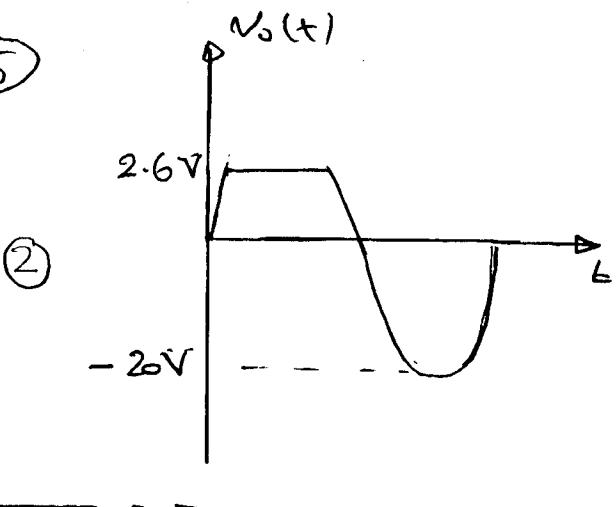

Q2:

- (b) The transistor parameters for the circuit in Figure (2) are $\beta_1 = 120$, $\beta_2 = 80$, $V_{BE1}(\text{on}) = V_{BE2}(\text{on}) = 0.7 \text{ V}$. Determine the quiescent collector current in each transistor.

Solution

Loop (I)

$$-5 + \sqrt{V_{BE1}} + \sqrt{V_{BE2}} + 50 \cdot I_2 = 0$$

$$I_2 = \frac{-5 - \sqrt{V_{BE1}} - \sqrt{V_{BE2}}}{50}$$

$$= \frac{-5 - 0.7 - 0.7}{50} = \frac{3.6}{50} = 72 \text{ mA}$$

$$I_1 = \frac{\sqrt{V_{BE2}}}{0.5 \text{ k}\Omega} = \frac{0.7}{0.5 \text{ k}\Omega} = 1.4 \text{ mA}$$

at node (1)

$$I_1 + I_{E2} = I_2 \Rightarrow I_{E2} = I_2 - I_1$$

$$I_{E2} = (72 - 1.4) \text{ mA} = 70.6 \text{ mA}$$

$$I_{B2} = \frac{I_{E2}}{1 + \beta_2} = \frac{70.6 \text{ mA}}{81} = 871.605 \text{ mA}$$


$$I_{C2} = \beta_2 I_{B2} = 871.605 \text{ mA} \times 80 = 69.728 \text{ mA}$$

at node (2)

$$I_{E1} = I_{B2} + I_1 = 871.605 \text{ mA} + 1.4 \text{ mA} = 2.272 \text{ mA}$$

$$I_{C1} = \alpha_1 I_{E1} = \frac{\beta_1}{1 + \beta_1} I_{E1}$$
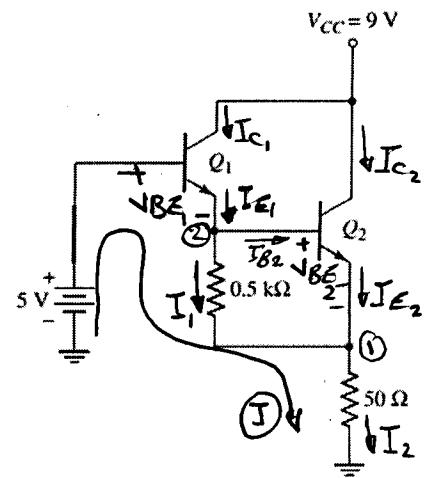
$$= \frac{120}{121} \times 2.272 \text{ mA} = 2.253 \text{ mA}$$



Q3:


The parameters of the zener diode for the voltage regulator circuit of Fig. () are $V_Z = 4.7 \text{ V}$ at test current $I_{ZT} = 53 \text{ mA}$, $r_Z = 8\Omega$, and $I_{ZK} = 1 \text{ mA}$. The supply voltage is $V_S = 12 \pm 2 \text{ V}$, and $R_s = 220\Omega$.

(a) Find the nominal value of the output voltage v_O under no-load condition R_L .

(b) Find the maximum and minimum values of the output voltage for a load resistance of $R_L = 470\Omega$.

(c) Find the nominal value of the output voltage v_O for a load resistance of $R_L = 100\Omega$.

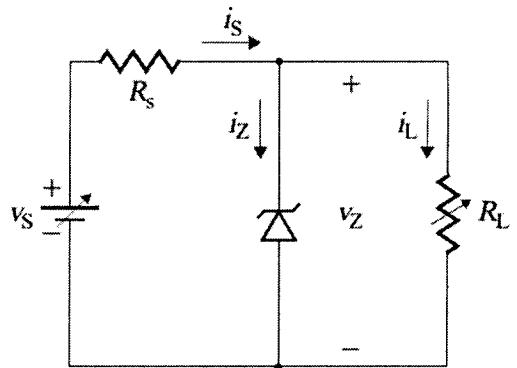(d) Find the minimum value of R_L for which the zener diode operates in the breakdown region.



Solution

$$\sqrt{Z} = 4.7 \text{ @ } I_{ZT} = 53 \text{ mA} ; r_Z = 8\Omega$$

$$r_{ZK} = 500\Omega \text{ at } I_{ZK} = 1 \text{ mA}$$

$$V_S = 12 \pm 2 \text{ V}, \text{ and } R_s = 220\Omega$$

1st find $\sqrt{Z_0}$

$$\therefore \sqrt{Z_0} = \sqrt{Z} + L_Z r_Z \Rightarrow \sqrt{Z_0} = \sqrt{Z} - L_Z r_Z$$

$$\sqrt{Z_0} = 4.7 - 53 \text{ mA} * 8 = 4.28 \text{ V}$$

(a) For No Load i.e. $R_L = \infty$ find v_O at nominal value of $V_S = 12 \text{ V}$

$$i_s = i_Z = \frac{V_S - \sqrt{Z_0}}{R_s + r_Z} = \frac{12 - 4.28}{220 + 8} = 33.86 \text{ mA}$$

$$\therefore v_O = \sqrt{Z_0} + L_Z r_Z = 4.28 + 33.86 \text{ mA} * 8 = 4.55 \text{ V}$$

(b) find The max. and min. values of The o/p voltage for $R_L = 470\Omega$

The max. value v_O occurs at V_S max



$$\therefore V_S \text{ max} = V_S + 2 \text{ V} = 12 + 2 = 14 \text{ V}$$

- At $V_S = 12 \text{ V}$ (Nominal value) and

$R_L = 470\Omega$ is connected

$$i_L = \frac{\sqrt{Z}}{R_L} = \frac{4.7}{470} = 10 \text{ mA}$$
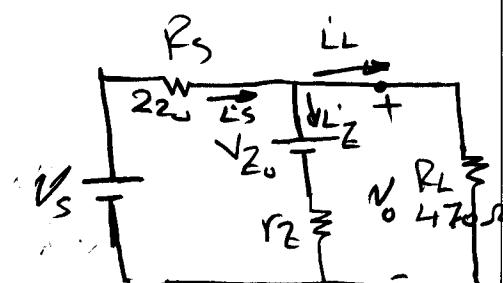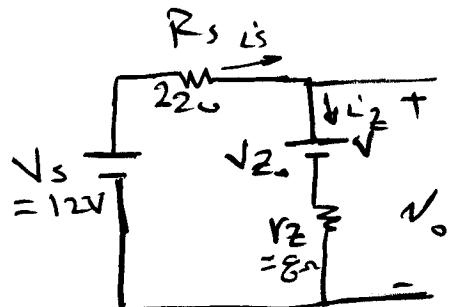
$$i_s = \frac{V_S - \sqrt{Z}}{R_s} = \frac{12 - 4.7}{220} = 33.2 \text{ mA}$$



$$\therefore \dot{I}_Z|_{\text{loaded}} = \dot{I}_S - \dot{I}_L = 33.2 \text{ mA} - 10 \text{ mA} = 23.2 \text{ mA}$$

$$\therefore V_o = V_{Z_0} + \dot{I}_Z|_L R_Z$$

$$= 4.28 + 23.2 \times 10^{-3} \times 8 = 4.47 \text{ V}$$

For $V_S|_{\max} = 14 \text{ V}$ and $R_L = 470 \Omega$ connected.

$$\dot{I}_S = \frac{V_S - V_o}{220} = \frac{14 - 4.47}{220} = 43.32 \text{ mA}$$

$$\dot{I}_L = \frac{V_o}{R_L} = \frac{4.47}{470} = 9.51 \text{ mA}$$

$$\therefore \dot{I}_Z|_{\max} = \dot{I}_S - \dot{I}_L = 43.32 - 9.51 = 33.81 \text{ mA}$$

$$\therefore V_o|_{\max} = V_{Z_0} + \dot{I}_Z|_{\max} R_Z$$

$$= 4.28 + 33.81 \text{ mA} \times 8 = 4.55 \text{ V}$$

For $V_S|_{\min} = 12 - 2 = 10 \text{ V}$

$$\dot{I}_S = \frac{V_S - V_o}{R_S} = \frac{10 - 4.47}{220} = 25.14 \text{ mA}$$

$$\dot{I}_L = \frac{V_o}{R_L} = \frac{4.47}{470} = 9.51 \text{ mA}$$

$$\dot{I}_Z|_{\min} = \dot{I}_S - \dot{I}_L = 25.14 - 9.51 = 15.63 \text{ mA}$$

$$\therefore V_o|_{\min} = V_{Z_0} + \dot{I}_Z|_{\min} R_Z = 4.28 + 15.63 \text{ mA} \times 8 = 4.41 \text{ V}$$

(c) For $R_L = 100 \Omega$ at nominal value of V_S find V_o

$$\text{for } V_S = 12 \text{ V} \Rightarrow \dot{I}_L = \frac{V_o}{R_L} = \frac{4.47}{100} = 47 \text{ mA}$$

$$\therefore \dot{I}_S = 33.2 \text{ mA} \Rightarrow \dot{I}_L > \dot{I}_S \quad (\dot{I}_S = \dot{I}_L + \dot{I}_Z)$$

\therefore Zener must be off

$$\therefore V_o = \frac{V_S R_L}{R_L + R_S} = \frac{12 \times 100}{100 + 220} = 3.75 \text{ V}$$



(d) Find the min. value of R_L for which the Zener operate in breakdown region

To operate in break down region \Rightarrow Zener current = I_{ZK}
 $= 1\text{mA} = I_Z = \frac{I_Z}{R_s} \mid_{\min} \sqrt{Z_K} \approx \sqrt{Z_0} = \sqrt{Z} = 4.28\text{V}$

$$\therefore I_S \mid_{\min} = \frac{\sqrt{V_{\min}} - \sqrt{Z_0}}{R_s} = \frac{10 - 4.28}{220} = 26\text{mA}$$

$$\therefore I_L = I_S \mid_{\min} - I_Z \mid_{\min} = 26\text{mA} - 1\text{mA} = 25\text{mA}$$

$\therefore R_L \mid_{\min}$ To operate in breakdown region is given by

$$R_L > \frac{V_Z}{I_L}$$

$$R_L \mid_{\min} > \frac{4.28}{25\text{mA}} = 171.2\Omega$$

CQ4:

For the amplifier shown in Fig.(4), $\beta = 80$ and $V_A = 150$ V. (a) Determine the dc voltages at the base and emitter terminals. (b) Using the small signal hybrid π -model calculate the values of R_{in} , R_o , the voltage gain (v_o/v_s), and the current gain (i_o/i_s).

Solution

DC Analysis

$$I_E = I = 0.5 \text{ mA}$$

$$I_B = \frac{I_E}{1+\beta} = \frac{0.5 \text{ mA}}{1+80} = 6.173 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{1+\beta} I_E$$

$$= \frac{80}{81} \times 0.5 \text{ mA} = 0.494 \text{ mA}$$




$$\gamma_T = \frac{I_C}{V_T} = \frac{0.494 \text{ mA}}{25 \text{ m}} = 19.76 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta}{\gamma_T} = \frac{80}{19.76 \text{ m}} = 4.049 \text{ k}\Omega$$


$$R_o = \frac{V_A}{I_C} = \frac{150}{0.494 \text{ mA}} = 303.644 \text{ k}\Omega$$

AC Analysis

Using π -model

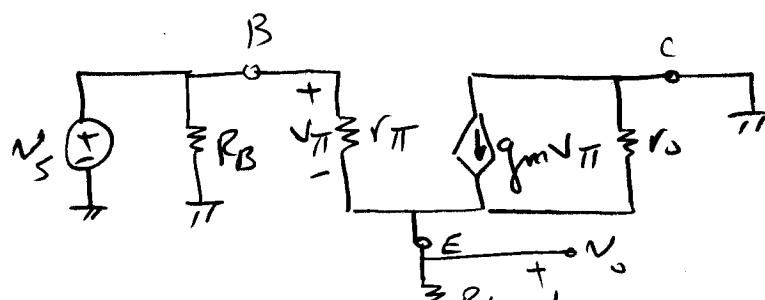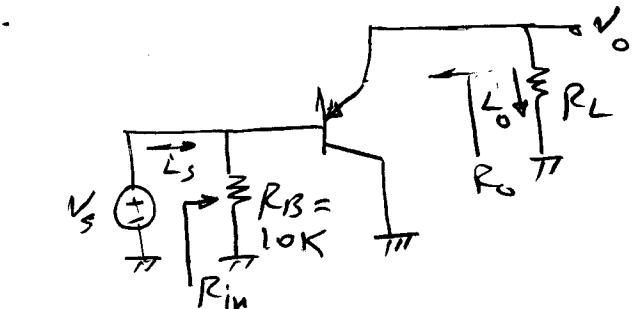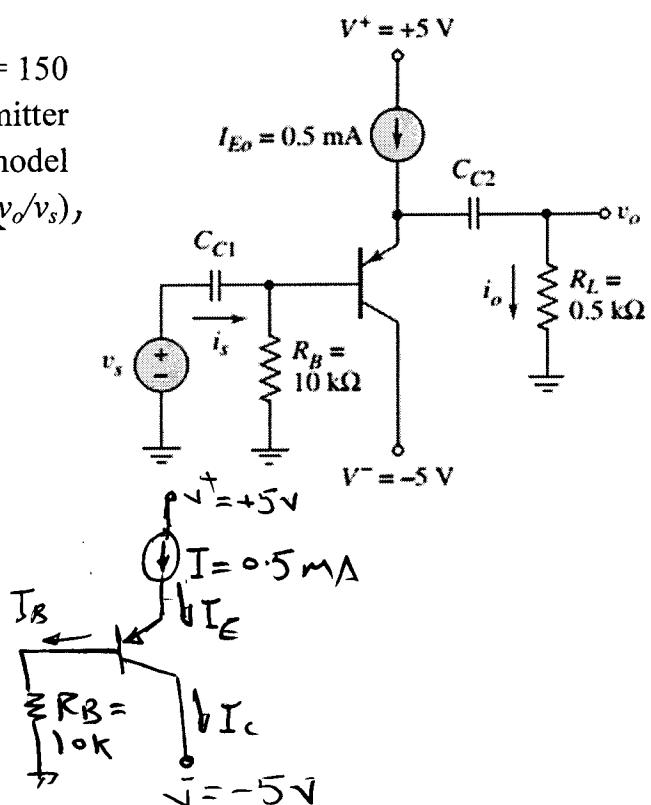


Roll R_L Then The model become -

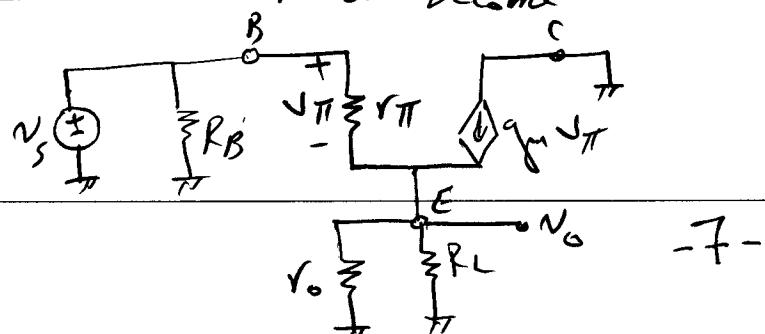

To find R_i

$$R_L \parallel r_o = 0.5K \parallel 303.644K = 499.178\Omega$$
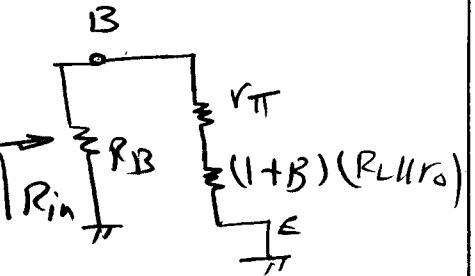
$$R_{in} = R_B \parallel [r_\pi + (1+B)(R_L \parallel r_o)]$$




$$= 10K \parallel [4.049K\Omega + (1+80)(499.178)]$$

$$= 10K \parallel 44.482K = 8.165 K\Omega$$

To find R_o

$$R_o |_{N_s=0} \Rightarrow R_B \parallel S.C. = 0$$

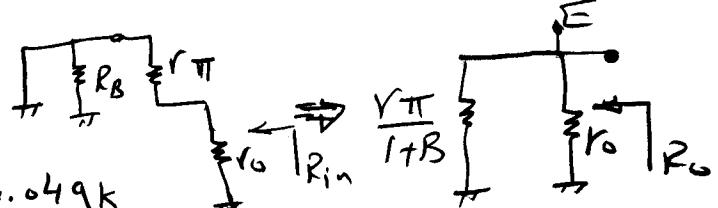


$$R_o = r_o \parallel \frac{r_\pi}{1+B} = 303.644K \parallel \frac{4.049K}{81}$$

$$= 303.644K \parallel 50 \approx 50\Omega$$

To find $A_v = \frac{V_o}{V_s}$
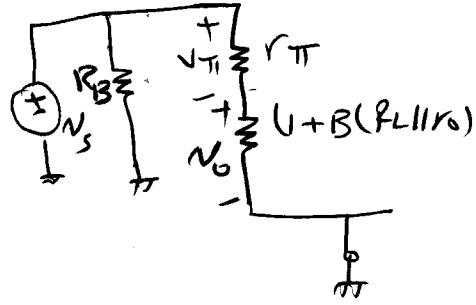
$$V_o = \frac{V_s(1+B)(R_L \parallel r_o)}{r_\pi + (1+B)(R_L \parallel r_o)}$$



$$\therefore A_v = \frac{V_o}{V_s} = \frac{(1+B)(R_L \parallel r_o)}{r_\pi + (1+B)(R_L \parallel r_o)}$$

$$= \frac{81(499.178)}{4.049K + 81(499.178)}$$

$$= \frac{40.433K}{4.049K + 40.433K} = 0.91 \text{ V/V}$$

To find $A_L = \frac{I_o}{I_s}$


$$I_o = I_s \frac{r_o}{r_o + R_L} = (1+B) I_b \frac{r_o}{r_o + R_L}$$

$$I_b = I_s \frac{R_B}{R_B + r_\pi + (1+B)(R_L \parallel r_o)}$$

$$A_L = \frac{I_o}{I_s} = (1+B) \left(\frac{r_o}{r_o + R_L} \right) \left(\frac{R_B}{R_B + r_\pi + (1+B)(R_L \parallel r_o)} \right)$$

$$= 81 \left(\frac{303.644K}{303.644K + 0.5K} \right) \left(\frac{10K}{10K + 4.049K + 81 \times 499.178} \right)$$

$$= 14.84 \text{ V/V}$$

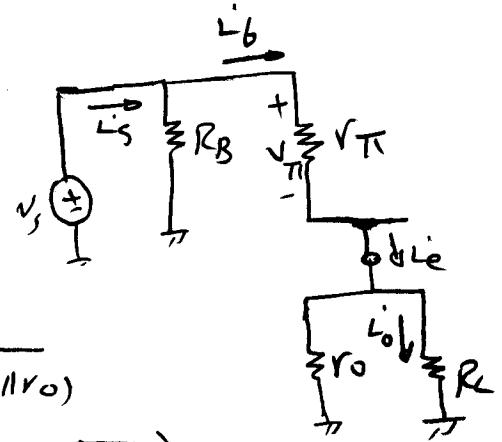

Q5:

The parameters of the circuit shown are

$$V_{CC} = 15 \text{ V}, R_{C1} = R_{C2} = 1 \text{ k}\Omega, \\ R_1 = R_3 = 65 \text{ k}\Omega, R_2 = R_4 = 25 \text{ k}\Omega,$$

$$R_E_1 = R_E_2 = 400 \text{ }\Omega; R_L = 20 \text{ k}\Omega, \\ \text{and } C_1 = C_2 = C_3 = C_E \approx \infty$$



Assume, identical Transistors of
 $B = 100$ and $V_A = 100 \text{ V}$.

calculate R_i , R_o , and $A_v = \frac{V_o}{V_s}$

Solution

DC Analysis

ALL cap. o.c
for Q₁ and Q₂

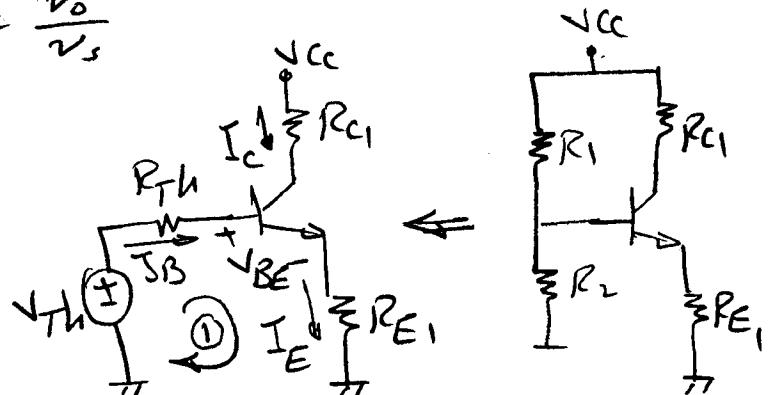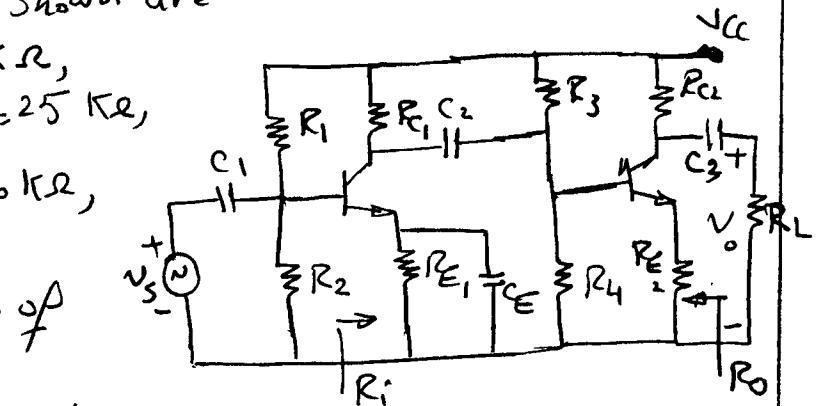

$$R_{Th} = R_1 // R_2 = 65 \text{ k} // 25 \text{ k} = 18.1 \text{ k}\Omega$$

$$V_{Th} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{15 \times 25 \text{ k}}{25 \text{ k} + 65 \text{ k}} = 4.17 \text{ V}$$

Loop ①

$$-V_{Th} + I_B R_{Th} + V_{BE} + I_E R_{E1} = 0 \quad \rightarrow ①$$

$$\therefore I_E = (1 + \beta) I_B$$

$$I_B (R_{Th} + (1 + \beta) R_{E1}) = V_{Th} - V_{BE}$$

$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (1 + \beta) R_{E1}} = \frac{4.17 - 0.7}{18.1 \text{ k} + 101 \times 400} = 59.32 \text{ mA} \quad \rightarrow ②$$


$$I_C = \beta I_B = 5.932 \text{ mA} \quad \rightarrow ③$$

$$\therefore g_m = g_{f2} = g_f = \frac{I_C}{V_T} = \frac{5.932 \text{ mA}}{25 \text{ m}} = 237.28 \text{ mA/V} \quad \rightarrow ④$$

$$r_{\pi 1} = r_{\pi 2} = r_{\pi} = \frac{\beta}{g_m} = \frac{100}{237.28 \times 10^{-3}} = 421.52 \quad \rightarrow ⑤$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{5.932 \text{ mA}} = 16.86 \text{ k}\Omega \quad \rightarrow ⑥$$

AC Analysis

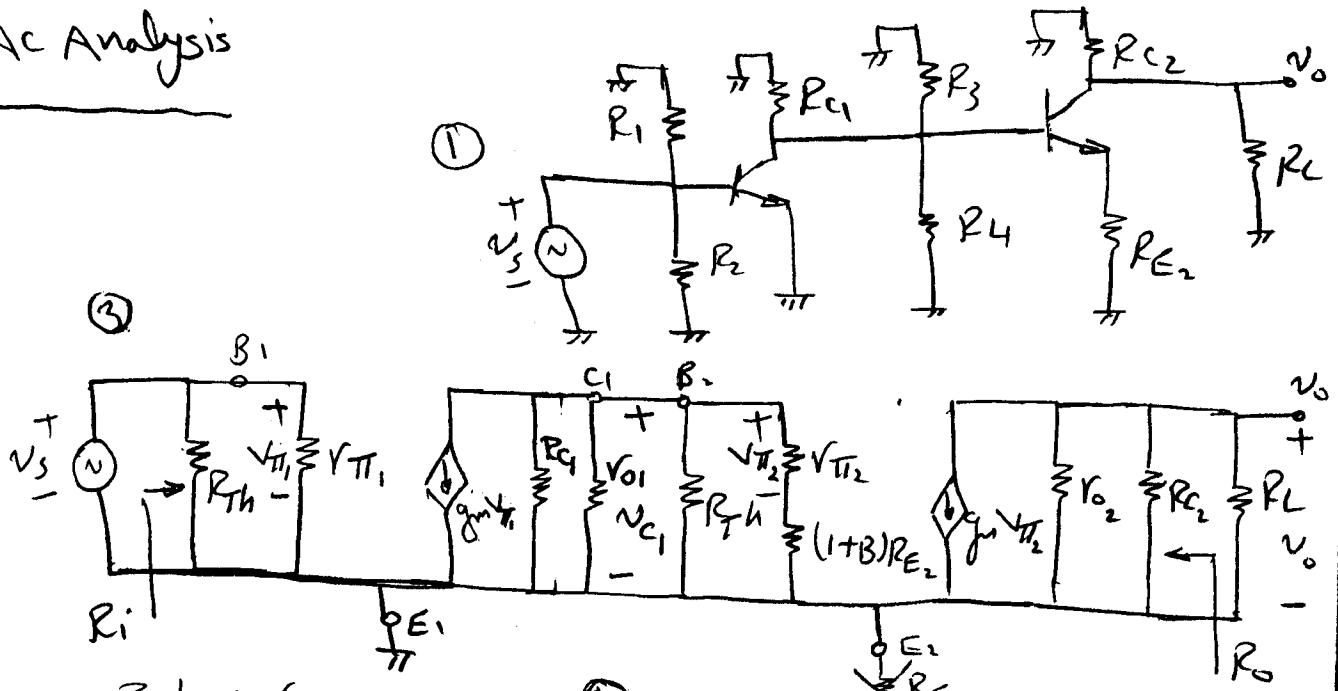

$$R_i = R_{Th} \parallel r_{\pi 1} \quad \text{--- } ①$$

$$= 18.1 \text{ K} \parallel 421 = 411 \Omega \quad \text{--- } ①$$

$$R_o = r_{o2} \parallel R_{C2} \quad \text{--- } ①$$

$$N_s = 16.86 \text{ K} \parallel 1 \text{ K} \Omega = 944 \Omega \quad \text{--- } ①$$

$$R_{Ley} = r_{o2} \parallel R_{C2} \parallel R_L = 16.86 \text{ K} \parallel 1 \text{ K} \parallel 20 \text{ K} = 901.5 \Omega$$

$$\begin{aligned} R_{eq} &= R_{C1} \parallel r_{o1} \parallel R_{Th} \parallel [r_{\pi 2} + (1+B)R_{E2}] \\ &= 1 \text{ K} \parallel 16.86 \text{ K} \parallel 18.1 \text{ K} \parallel [421 + 101 \times 400] \\ &= 1 \text{ K} \parallel 16.86 \text{ K} \parallel 18.1 \text{ K} \parallel 40.82 \text{ K} \Omega = 878 \Omega. \end{aligned}$$

$$V_o = -g_m r_{\pi 2} R_{Ley} \quad \text{--- } ①$$

$$V_{C1} = -g_m r_{\pi 1} R_{eq} \quad \text{--- } ①$$

$$r_{\pi 2} = V_{C1} \frac{r_{\pi 2}}{r_{\pi 2} + (1+B)R_{E2}}$$

$$r_{\pi 2} = -g_m r_{\pi 1} R_{eq} \frac{r_{\pi 2}}{r_{\pi 2} + (1+B)R_{E2}} \quad \text{--- } ①$$

$$\therefore r_{\pi 1} = V_s \frac{r_{\pi 2}}{r_{\pi 2} + (1+B)R_{E2}} \quad \text{--- } ①$$

$$r_{\pi 2} = -g_m V_s R_{eq} \frac{r_{\pi 2}}{r_{\pi 2} + (1+B)R_{E2}}$$

$$V_o = +g_m g_m V_s R_{eq} \frac{r_{\pi 2}}{r_{\pi 2} + (1+B)R_{E2}} R_{Ley}$$

$$\begin{aligned}
 A_v &= \frac{V_o}{V_s} = \alpha_m \alpha_f \cdot \frac{R_E r_{T2} R_C \beta}{r_{T2} + (1+\beta) R_E^2 E_2} \\
 &= (237 \cdot 28 \cdot 1.5)^2 \cdot \frac{878 * 421 * 901.5}{421 + 101 * 400} \\
 &= \underline{\underline{459.6 \text{ V/V}}} \quad \rightarrow \textcircled{1}
 \end{aligned}$$