
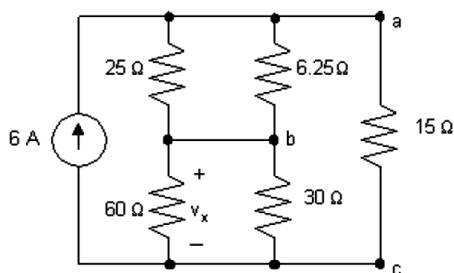



## Exam With Model Answer

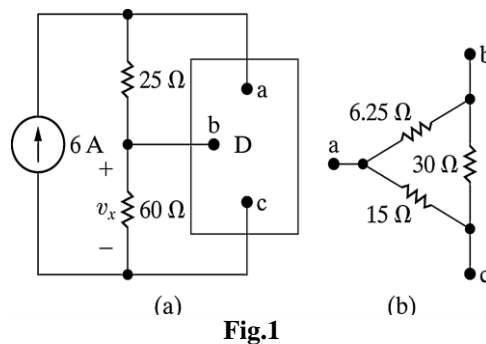**Question 1 (15 marks)**

In the circuit in Fig.1(a) the device labeled D represents a component that has the equivalent circuit shown in Fig.1(b). The labels on the terminals of D show how the device is connected to the circuit. Find  $v_x$  and the power absorbed by the device.


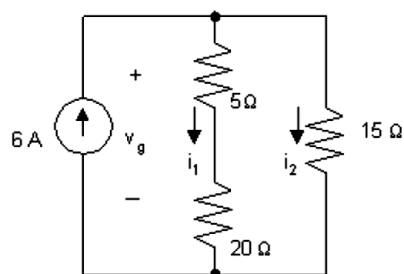
$$25 \parallel 6.25 = 5 \Omega \quad 60 \parallel 30 = 20 \Omega$$



$$i_1 = \frac{(6)(15)}{(40)} = 2.25 \text{ A}; \quad v_x = 20i_1 = 45 \text{ V}$$

$$v_g = 25i_1 = 56.25 \text{ V}$$


$$v_{6.25} = v_g - v_x = 11.25 \text{ V}$$

$$P_{\text{device}} = \frac{11.25^2}{6.25} + \frac{45^2}{30} + \frac{56.25^2}{15} = 298.6875 \text{ W}$$

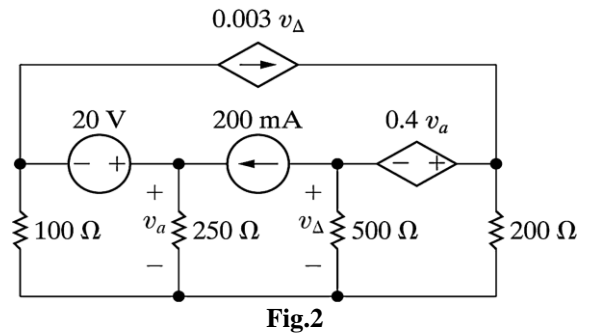
**Question 2 (15 marks)**

For the circuit shown in Fig.2,

- Write the node voltage equations needed to find the voltages  $v_a$  and  $v_\Delta$ . (*Write both the main equations and the auxiliary equations*).
- Write the mesh current equations needed to find the voltages  $v_a$  and  $v_\Delta$ . (*Write both the main equations and the auxiliary equations*).



a)

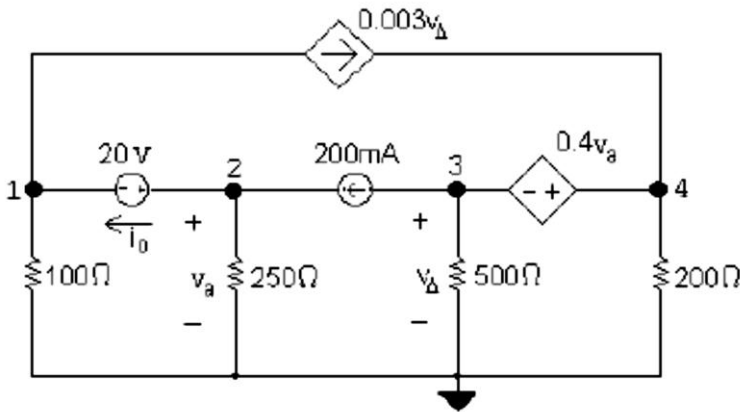

Node voltage equations:


$$\frac{v_1}{100} + 0.003v_\Delta + \frac{v_2}{250} - 0.2 = 0$$

$$0.2 + \frac{v_3}{100} + \frac{v_4}{200} - 0.003v_\Delta = 0$$

b) Write the mesh equations by yourself.


**Question 3 (15 marks)**

- Find the Norton equivalent circuit with respect to the terminals a,b for the circuit seen in Fig.3.
- Find the maximum power that could be transferred to the load connected across the terminals a,b.

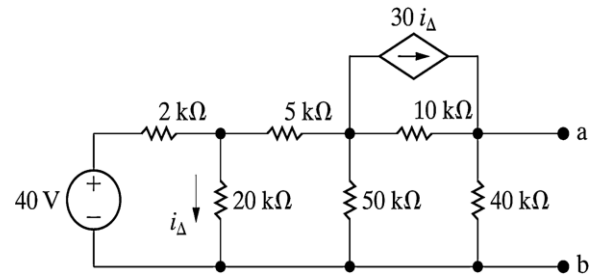

**Fig.3**

- Norton equivalent circuit

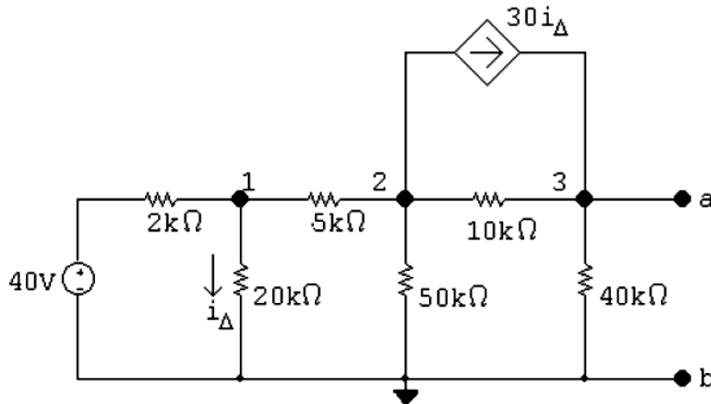

The node voltage equations are:

$$\frac{v_1 - 40}{2000} + \frac{v_1}{20,000} + \frac{v_1 - v_2}{5000} = 0$$

$$\frac{v_2 - v_1}{5000} + \frac{v_2}{50,000} + \frac{v_2 - v_3}{10,000} + 30 \frac{v_1}{20,000} = 0$$

$$\frac{v_3 - v_2}{10,000} + \frac{v_3}{40,000} - 30 \frac{v_1}{20,000} = 0$$

In standard form:


$$v_1 \left( \frac{1}{2000} + \frac{1}{20,000} + \frac{1}{5000} \right) + v_2 \left( -\frac{1}{5000} \right) + v_3(0) = \frac{40}{2000}$$

$$v_1 \left( -\frac{1}{5000} + \frac{30}{20,000} \right) + v_2 \left( \frac{1}{5000} + \frac{1}{50,000} + \frac{1}{10,000} \right) + v_3 \left( -\frac{1}{10,000} \right) = 0$$

$$v_1 \left( -\frac{30}{20,000} \right) + v_2 \left( -\frac{1}{10,000} \right) + v_3 \left( \frac{1}{10,000} + \frac{1}{40,000} \right) = 0$$

Solving,  $v_1 = 24 \text{ V}$ ;  $v_2 = -10 \text{ V}$ ;  $v_3 = 280 \text{ V}$

$V_{Th} = v_3 = 280 \text{ V}$

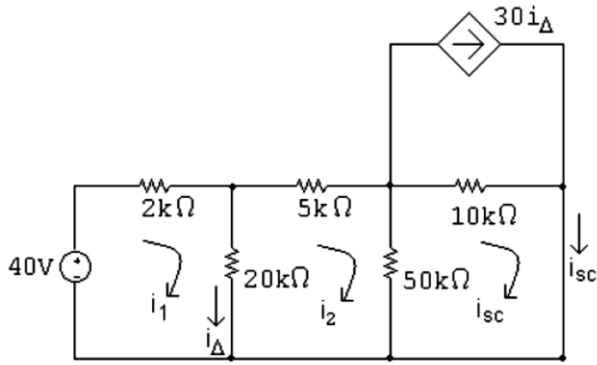

The mesh current equations are:

$$-40 + 2000i_1 + 20,000(i_1 - i_2) = 0$$

$$5000i_2 + 50,000(i_2 - i_{sc}) + 20,000(i_2 - i_1) = 0$$

$$50,000(i_{sc} - i_2) + 10,000(i_{sc} - 30i_{\Delta}) = 0$$

The constraint equation is:

$$i_{\Delta} = i_1 - i_2$$

Put these equations in standard form:

$$i_1(22,000) + i_2(-20,000) + i_{sc}(0) + i_{\Delta}(0) = 40$$


$$i_1(-20,000) + i_2(75,000) + i_{sc}(-50,000) + i_{\Delta}(0) = 0$$

$$i_1(0) + i_2(-50,000) + i_{sc}(60,000) + i_{\Delta}(-300,000) = 0$$

$$i_1(-1) + i_2(1) + i_{sc}(0) + i_{\Delta}(1) = 0$$

Solving,  $i_1 = 13.6 \text{ mA}$ ;  $i_2 = 12.96 \text{ mA}$ ;  $i_{sc} = 14 \text{ mA}$ ;  $i_{\Delta} = 640 \mu\text{A}$
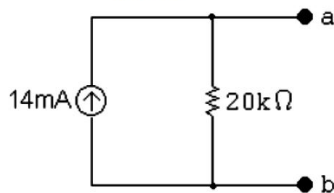
$$R_{Th} = \frac{280}{0.014} = 20 \text{ k}\Omega$$



b) The maximum power transferred to the load =  $(V_{th})^2/4R_{th} = 0.98 \text{ Watt}$

**Question 4 (15 marks)**

The op amp in the circuit in Fig.4 is ideal. Using  $V_{cc} = \pm 10V$ , Find the value of  $\sigma$  in which the op amp does not saturate.


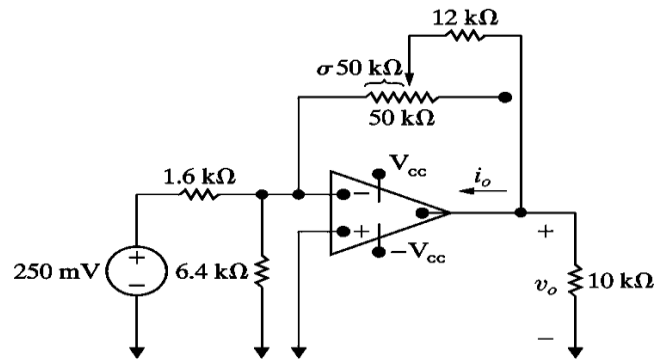


Fig.4

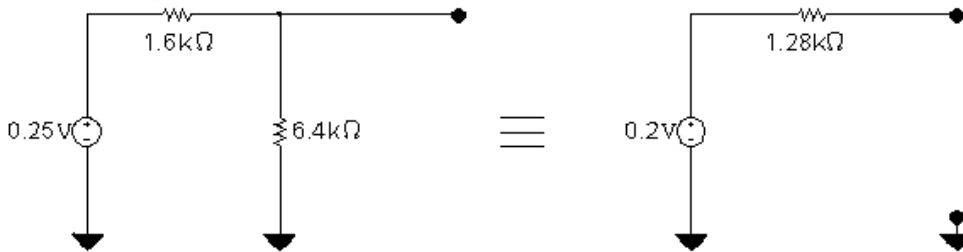Replace the combination of  $v_g$ ,  $1.6 k\Omega$ , and the  $6.4 k\Omega$  resistors with its Thévenin equivalent.



$$\text{Then } v_o = \frac{-[12 + \sigma 50]}{1.28}(0.20)$$

At saturation  $v_o = -10V$ ; therefore

$$-\left(\frac{12 + \sigma 50}{1.28}\right)(0.2) = -10 \quad \text{or} \quad \sigma = 1.04$$

The max value for  $\sigma$  is 1, so any value of  $\sigma$  will not saturate the amplifier.

*Good Luck,*