



جامعة بنها - كلية الهندسة بنها - قسم الهندسة الكهربائية

الإجابة النموذجية لمادة نظم التحريك الكهربائية ك1439 الفرقة الرابعة كهرباء قوى وتحكم

يوم الاربعاء الموافق 11/1/2017 د شوقي حامد عرفه ابراهيم

Benha University	Time: 3 hours	 
Benha Faculty of Engineering	Forth Year : 11/1/2017	
Subject: Electrical drive systems (E1439)	Elect.Eng.Dept.	

Solve & draw as much as you can (questions in two pages)

Question (1)

[10] Points

a- Explain in details: Electrical drives- Speed control of a DC motor?

b- A three phase- Y- induction motor [380V, 60Hz, 1700rpm, pf=0.8, $\eta_m=0.85$, 4 poles]. Find ω_{syn} , S, I_s , P_m , T_{dev} when used to:

i-Drive a load of 80Nm, 1440 rpm across gear box of $\eta_{gear}=0.9$.

ii-Drive an elevator of $\eta_{elev}=0.75$ and loaded by 8000Kg to 100m in one minute (design to half load).

iii-Drive a water pump of 20m³/hour, height =25m across gear box of $\eta_{gear}=0.8$.

Question (2)

[15] Points

a- The closed loop control system is used for speed control of a separately excited DC motor. Draw the steady state block diagram and prove that

$$\frac{\omega_r}{V_r} = \frac{K_1 K \phi}{BR_a + K \phi (K_1 K_2 + K \phi)} \quad \frac{\omega_r}{-T_w} = \frac{R_a}{BR_a + K \phi (K_1 K_2 + K \phi)}$$

b- A [80Hp, 200V, 1200 rpm] separately excited DC motor is used in a speed control system. The field current is held constant at a value for which $R_a = 0.1\Omega$, $B = 0.03 N.m.s/rad$, $K\Phi = 1.3 V.S/rad$, $K_1 = 200$, $K_2 = 0.1 V s/rad$.

i- Find V_r required to drive the motor at rated speed with no load?

ii- Find the motor speed if V_r is not changed and the motor supplied rated torque?

iii- Find the motor speed if V_r is decreased by 15%?

Question (3)**[30] Points**

A separately excited DC motor has

11hp, 240V, 1500rpm, $R_a = 0.125\Omega$, $R_f = 120\Omega$, $K\Phi = 1.5Nm/A$, $T_{losses} = \text{constant} = 2.24Nm$, load torque is 50Nm.

- a- Find the motor speed if the armature voltage is 190 V?
- b- Find the motor speed and (pf) if its armature is supplied by fully controlled single phase rectifier [firing angle = 25 degrees, 240 V, 60Hz AC supply] and assume constant armature current and field current?
- c- Find the motor speed and (pf) if its armature is supplied by a semi-controlled single phase rectifier [firing angle = 20 degrees, 240 V, 60Hz AC supply] and assume constant armature current and field current?
- d- Find the motor speed if its armature is supplied by fully controlled single phase rectifier [firing angle = 25 degrees, 240 V, 60Hz AC supply]. Assume constant field current but the armature current discontinuous for 10 degrees every half cycle?
- e- Draw the wave forms of voltages and currents and the power circuit for b, c, and d?

Question (4)**[10] Points**

A separately excited DC motor has [$K\Phi = 0.5 \frac{Nm}{A}$, $R_a = 0.3\Omega$, $L_a = 0.06H$]

a- If the load is [5Nm at 859 rpm] and the motor armature supplied from class A chopper and 72V dc source. The chopping frequency is 1 KHz. The field current is held constant.

- i-Find the minimum duty cycle?
- ii-Find the armature current equations during the on and off periods?
- iii- Draw the power circuit and current and voltage waveforms?

Question (5)**[25] Points**

- a- Explain how to control the speed of the 3-phase induction motor?
- b- A three phase 460V, 60Hz, 4 poles, 1750 rpm, wye-connected induction motor has the following equivalent circuit parameters referred to the stator side:

$R_s = 1.01\Omega$, $R_r = 0.69\Omega$, $X_m = 43.5\Omega$, $X_1 = 1.3\Omega$, $X_2 = 1.94\Omega$, $T_L = K\omega_r^2 = 41Nm$ at 1740rpm

- i- Draw the equivalent circuit and find ω_{syn} , ω_r , S , I_s , I_r , P_{gap} , P_{copper} , T_{dev} ?
- ii- If the motor is connected to a 3-phase full wave AC/AC converter. Find the firing angle required to run the motor with speed range of 1000 rpm to 1750 rpm.
- iii- If the motor is connected to a 3-phase six step inverter. Find the required DC supply to run the motor with speed of 1000 rpm?
- iv- Draw the power circuit and current and voltage waveforms for case ii and case iii?

Answer

Question (1)

[20] Points


a- Explain in details: Electrical drives- Speed control of a DC motor?

The study of electric drive systems involves controlling electric motors in the steady state and in dynamic operations, taking into account the characteristics of mechanical loads and the behaviors of power electronic converters.

The electrical Drive is a system converts the electrical Energy to the mechanical energy with electrical control.

Drive types are: 1-line shaft drive 2-single motor single load drive 3-multimotor drives.

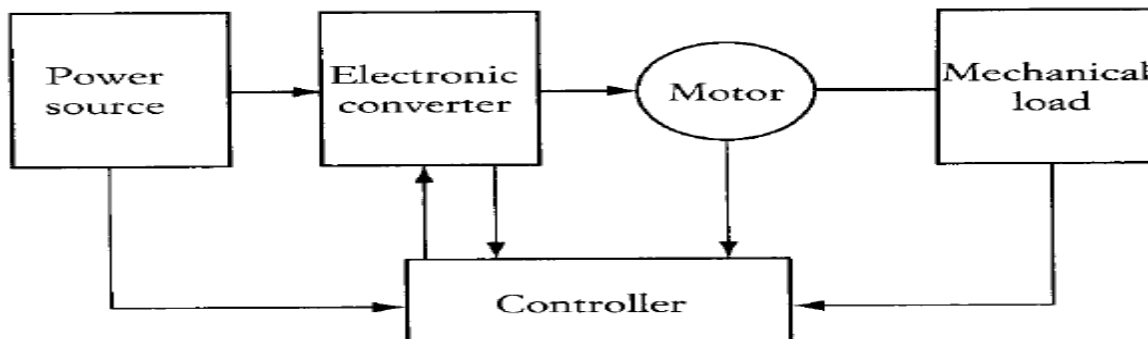Functional blocks of an electric drive system






1. *Separately excited machines.* The field winding is composed of a large number of turns with small cross-section wire. This type of field winding is designed to withstand the rated voltage of the motor. The field and armature circuits are excited by separate sources.


Speed control of DC drive: Common dc drives are 1-rectifier drives 2-dc chopper drives 3-dual converter drives

$$\omega = \frac{V_t}{K\Phi} - \frac{R_a}{(K\Phi)^2} T_d \quad \omega = \frac{V_t}{K\Phi} - \frac{R_a I_a}{K\Phi}$$

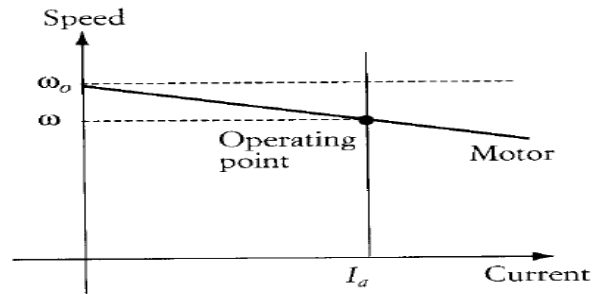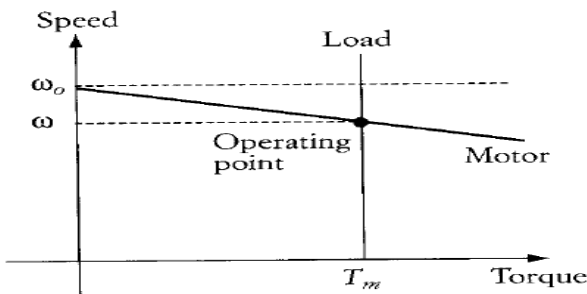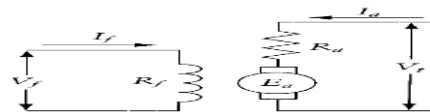
Equivalent circuit of a dc motor in steady-state operation



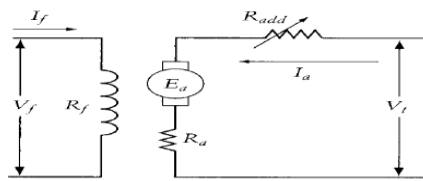
A setup for speed change by adding an armature resistance



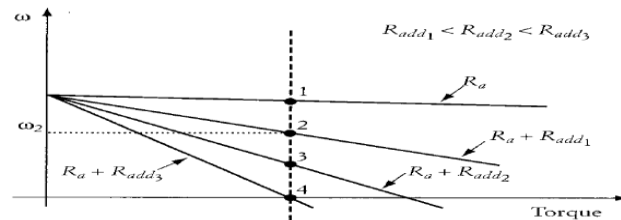
Effect of adding an armature resistance on speed



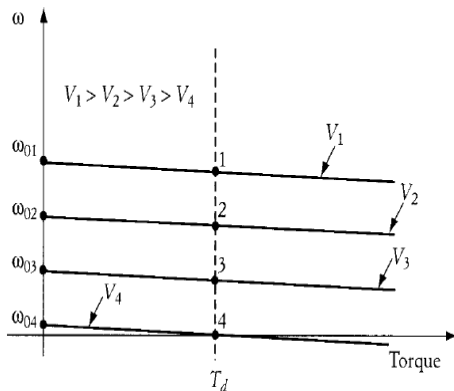Motor characteristics when armature voltage changes



Effect of field voltage on motor speed

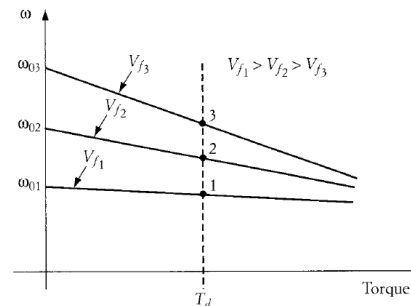

$$T_{\text{mech}} = K_a \Phi_d i_a, \quad e_a = K_a \Phi_d \omega_m$$

In a motor the relation between the emf E_a generated in the armature and the armature terminal voltage V_a is

$$V_a = E_a + I_a R_a \quad (7.11)$$

$$I_a = \frac{V_a - E_a}{R_a} \quad (7.12)$$

Torque and power:

The electromagnetic torque T_{mech}

$$T_{\text{mech}} = K_a \Phi_d I_a$$

The generated voltage E_a

$$E_a = K_a \Phi_d \omega_m$$

$$K_a = \frac{\text{poles} C_a}{2\pi m}$$

$E_a I_a$: electromagnetic power

$$T_{\text{mech}} = \frac{E_a I_a}{\omega_m} = K_a \Phi_d I_a$$

b-A three phase- Y- induction motor [380V, 60Hz, 1700rpm, pf=0.8, $\eta_m=0.85$, 4 poles]. Find ω_{syn} , S, I_s , P_m , T_{dev} when used to:

i-Drive a load of 80Nm, 1440 rpm across gear box of $\eta_{\text{gear}}=0.9$.

ii-Drive an elevator of $\eta_{\text{elev}}=0.75$ and loaded by 8000Kg to 100m in one minute (design to half load).

iii-Drive a water pump of 20m³/hour, height =25m across gear box of $\eta_{\text{gear}}=0.8$.

i---- $n_s=120*60/4=1800\text{rpm}$, $\omega_s=1800*\pi/30=188.5\text{rad/s}$, $S=(n_s-n_r)/n_s=(1800-1700)/1800=0.056$

$P_L=T_L*\omega_L=80*1440*\pi/30=12.06\text{KW}$, $P_{\text{inp gear}}=P_L/\eta_{\text{gear}}=12.06/0.9=13.4\text{KW}$

$P_{\text{inp m}}=P_{\text{outm}}/\eta_m=13.4/0.85=15.8\text{KW}=\sqrt{3} V_L I_L \cos\Phi$, $I_L=15800/(\sqrt{3}*380*0.8)=29.95\text{A}$

ii----- $P_L=F*V=m*g*V=8000*9.81*100/60=130.8\text{KW}$, $P_{\text{inp ele}}=P_L/\eta_{\text{ele}}=130.8/0.75=174.4\text{KW}$

$P_{\text{inp m}}=P_{\text{outm}}/\eta_m=174.4*0.5/0.85=102.6\text{KW}=\sqrt{3} V_L I_L \cos\Phi$, $I_L=102600/(\sqrt{3}*380*0.8)=124.7\text{A}$

iii---- $P_L=F*V=Q*g*h*\rho/t=20*9.81*25*1000/3600=1.3625\text{KW}$, $P_{\text{inp pump}}=P_L/\eta_{\text{gear}}=1.3625/0.8=1.703\text{KW}$, $P_{\text{inp m}}=P_{\text{outm}}/\eta_m=1.703/0.85=2.004\text{KW}=\sqrt{3} V_L I_L \cos\Phi$, $I_L=2004/(\sqrt{3}*380*0.8)=3.81\text{A}$


Question (2)

[15] Points

a- The closed loop control system is used for speed control of a separately excited DC motor. Draw the steady state block diagram and prove that

$$\frac{\omega_r}{V_r} = \frac{K_1 K \phi}{BR_a + K \phi (K_1 K_2 + K \phi)}$$
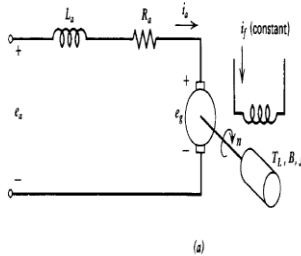
$$\frac{\omega_r}{-T_w} = \frac{R_a}{BR_a + K \phi (K_1 K_2 + K \phi)}$$



In the Laplace domain, equations 6.1 through 6.4 can be written as

$$E_a(s) = E_g(s) + R_a I_a(s) + L_a s I_a(s) \quad (6.5)$$

$$E_g(s) = K_a \Phi N(s) \quad (6.6)$$

$$T(s) = T_L(s) + B N(s) + J s N(s) \quad (6.7)$$

$$T(s) = K_t \Phi I_a(s) \quad (6.8)$$

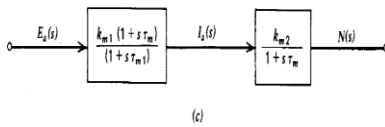
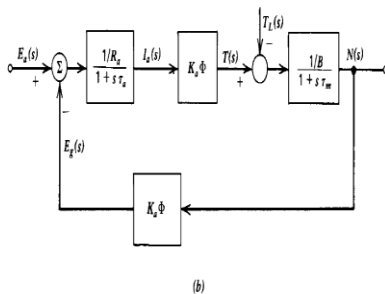


Fig. 6.1 Development of motor transfer function. (a) Separately excited dc motor model. (b) Functional block diagram. (c) Simplified functional block diagram.

$$I_a(s) = \frac{E_a(s) - E_g(s)}{R_a + sL_a} = \frac{[E_a(s) - E_g(s)] 1/R_a}{1 + \tau_a s}$$

where $\tau_a = L_a/R_a =$ electrical time constant of the motor armature

$$N(s) = \frac{T(s) - T_L(s)}{B + Js} = \frac{[T(s) - T_L(s)] 1/B}{1 + \tau_m s}$$

where $\tau_m = J/B =$ mechanical time constant of the motor.

$$\frac{N(s)}{E_r(s)} = \frac{k_s k_{IC} k_{m2}}{1 + k_s k_{IC} k_{m2} k_t} \frac{(1 + s\tau_t)}{1 + s \frac{(\tau_m + \tau_t)}{k^1} + \frac{s^2 \tau_m \tau_t}{k^1}}$$

$$\frac{N(s)}{E_a(s)} = \frac{K_a \Phi}{(K_a \Phi)^2 + R_a B + s R_a B \tau_m} = \frac{k_m}{1 + s \tau_{m1}}$$

$$\frac{N(s)}{E_a(s)} = \frac{K_a \Phi}{(K_a \Phi)^2 + R_a B(1 + s \tau_a)(1 + s \tau_m)}$$

$$\tau_{m1} = \frac{R_a B}{(K_a \Phi)^2 + R_a B} \tau_m$$

$$k_m = \frac{K_a \Phi}{(K_a \Phi)^2 + R_a B}$$

$$\tau_{m1} < \tau_m$$

2b

$$\frac{N(s)}{I_a(s)} = \frac{K_a \Phi / B}{1 + s \tau_m} = \frac{k_{m2}}{1 + s \tau_m}$$

From equations 6.12a and 6.13

$$\begin{aligned} \frac{I_a(s)}{E_a(s)} &= \frac{N(s)}{E_a(s)} \times \frac{I_a(s)}{N(s)} \\ &= \frac{k_m B(1 + s \tau_m)}{K_a \Phi(1 + s \tau_{m1})} = \frac{k_{m1}(1 + s \tau_m)}{1 + s \tau_{m1}} \end{aligned}$$

$$k_{m1} = \frac{B}{(K_a \Phi)^2 + R_a B} = \frac{k_m}{K_a \Phi / B}$$

$$k_{m2} = \frac{K_a \Phi}{B}$$

$$k_m = k_{m1} k_{m2}$$

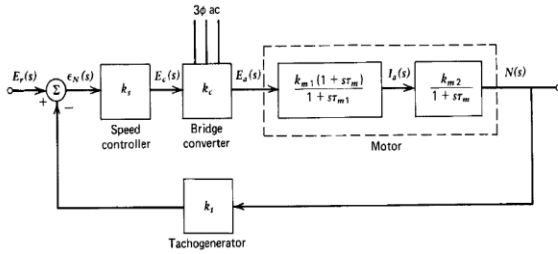


Fig. 6.3 Speed-control loop.

Proportional (P) Controller

Several types of speed controllers² are possible. Two of the more common ones are proportional (P) and proportional-integral (PI). First, a P controller is considered.

From Fig. 6.3

$$\frac{N(s)}{E_r(s)} = \frac{G(s)}{1 + G(s)H(s)}$$

E_c and the armature voltage E_a can be obtained. If the small time delay associated with the converter is neglected then

$$\frac{E_a(s)}{E_c(s)} = k_c = \frac{3\sqrt{2} V_{LL}}{\pi \hat{E}_c}$$

where \hat{E}_c corresponds to 0° firing angle and V_{LL} is the ac line to line rms voltage.

where

$$G(s) = \frac{k_c k_t k_{m1} k_{m2}}{1 + s \tau_{m1}}$$

$$H(s) = k_t$$

From equations 6.15, 6.15a, and 6.15b

$$\frac{N(s)}{E_r(s)} = \frac{k_1}{1 + s \tau_1}$$

$$V_r = 125.7/9.39 = 13.39V$$

$$\frac{\Delta\omega_r}{-\Delta T_w} = \frac{R_a}{BR_a + K\phi(K_1K_2 + K\phi)} = \frac{0.1}{27.7} = \frac{0.089}{41.9} = 0.00361,$$

$$\Delta\omega_r = -0.00361 * 474.8 = -\frac{1.714\text{rad}}{s}, \Delta\omega_r = -0.00361 * 476.2 = -\frac{1.72\text{rad}}{s}$$

$$\omega_r = 125.7 - 1.72 = \frac{124.\text{rad}}{s} = 1184\text{rpm}$$

iii-As V_r decreased to $=0.85*13.39=11.38V$, $w_r=11.38*9.39=106.87\text{rad/s}$

As motor loaded then $w_r=106.87-1.74=105.\text{rad/s}=1004\text{rpm}$

Question (3)

[30] Points

A separately excited DC motor has

11hp , $240V$, 1500rpm , $R_a = 0.125\Omega$, $R_f = 120\Omega$, $K\Phi = 1.5\text{Nm/A}$, $T_{\text{losses}} = \text{constant} = 2.24\text{Nm}$, load torque is 50Nm .

- Find the motor speed if the armature voltage is $190V$?
- Find the motor speed and (pf) if its armature is supplied by fully controlled single phase rectifier [firing angle = 25 degrees, $240V$, 60Hz AC supply] and assume constant armature current and field current?
- Find the motor speed and (pf) if its armature is supplied by a semi-controlled single phase rectifier [firing angle = 20 degrees, $240V$, 60Hz AC supply] and assume constant armature current and field current?
- Find the motor speed if its armature is supplied by fully controlled single phase rectifier [firing angle = 25 degrees, $240V$, 60Hz AC supply]. Assume constant field current but the armature current discontinuous for 10 degrees every half cycle?
- Draw the wave forms of voltages and currents and the power circuit for b, c, and d?

$$a-I_a = [50 + 2.24]/1.5 = 34.83A, E_a = 190 - 34.83 * 0.125 = 185.65V, w = 185.65/1.5 = 123.76\text{rad/s}, n = 1182\text{rpm}, V_a = E_a + I_a R_a$$

b-For a single phase rectifier with continuous armature current $V_a > E_a$

$\alpha=25$ degrees , $V_a=[2V_{max}\cos\alpha]/\pi=(2*240*1.414\cos25)/\pi=195.83V$, $w=[195.83-34.83*0.125]/1.5=127.65\text{rad/s}$, $n=1219\text{rpm}$, $V_a=E_a+I_aR_a$,

$\text{pf}=\cos\alpha=0.9\cos25=0.82$, $\text{pf}_1(\text{fundamental})=\cos\alpha=\cos25=0.91$

c-For a single phase semi-cont. rectifier with continuous armature current

$\alpha=20$ degrees , $V_a=[V_{max}(1+\cos\alpha)]/\pi=[240*1.414(1+\cos20)/\pi]=209.56V$, $w=[209.56-34.83*0.125]/1.5=136.8\text{rad/s}$, $n=1306.4\text{rpm}$

$\text{pf}_1(\text{fundamental})=\cos\alpha/2=\cos10=0.985$, $\text{pf}=(\sqrt{2}/(\pi(\pi-\alpha)))(1+\cos\alpha)=0.99$

d-For a single phase fully-cont. rectifier with discontinuous (10deg.) armature current

$\alpha=25$ degrees , $V_a=[V_{max}(\cos\alpha -\cos195)]/\pi=[240*1.414(0.966+\cos25)/\pi]=202.3V$,

$w=[202.3-34.83*0.125]/1.5=131.95\text{rad/s}$, $n=1260\text{rpm}$

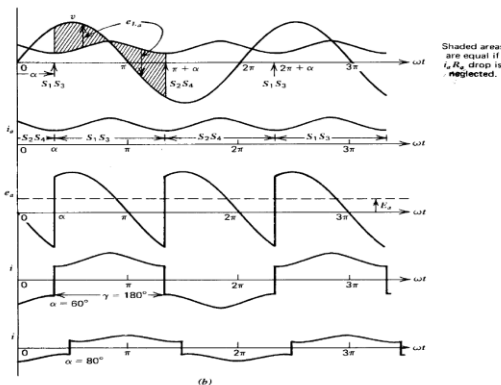
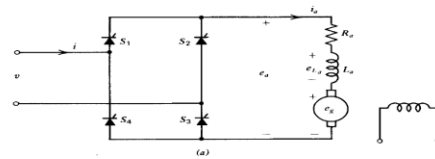
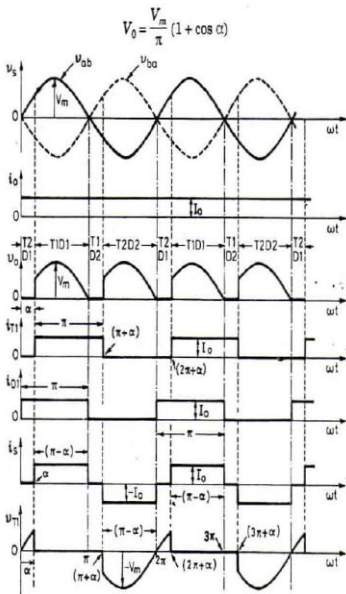
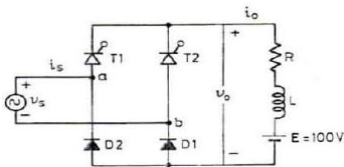


Fig. 2.3 Speed control of a separately excited dc motor by a single-phase full-converter. (a) Power circuit. (b) Voltage and current waveforms for continuous motor current (motor operation). (c) Waveforms for inversion operation.

Question (4)**[10] Points**

A separately excited DC motor has [$K\Phi = 0.5 \frac{Nm}{A}$, $R_a = 0.3\Omega$, $L_a = 0.06H$]

a- If the load is [5Nm at 859 rpm] and the motor armature is supplied from class A chopper and 72V dc source. The chopping frequency is 1 KHz. The field current is held constant.

i-Find the minimum duty cycle?

ii-Find the armature current equations during the on and off periods?

iii- Draw the power circuit and current and voltage waveforms?

$I_a = 5/0.5 = 10A$, $E = (2\pi/60) * 859 * 0.5 = 45V$, $E/V_{dc} = 45/72 = 0.625$,

$T_a = L_a/R_a = 0.06/0.3 = 0.2S$, $T_p = 1/1000 = 1mS$, $T_p/T_a = 0.005$,

$$t_{on\ critical} = \tau \ln \left[1 + \frac{E}{V_{dc}} \left(e^{T_p/\tau} - 1 \right) \right] = 0.626msec.$$

$$K_{critical} = \frac{\tau}{T_p} \ln \left[1 + \frac{E}{V_{dc}} \left(e^{T_p/\tau} - 1 \right) \right] = 0.626, V_a = E_a + I_a R_a = 45 + 10 * 0.3 = 48V,$$

$K = t_{on}/T_p = V_{av}/V_{dc} = 48/72 = 0.67 > K_c$ then continuous current mode

$$I_{max} = \frac{V_{dc}(1 - e^{-t_{on}/\tau})}{R_a(1 - e^{-T_p/\tau})} - \frac{E}{R_a} = 10.2A, \quad I_{min} = \frac{V_{dc}(e^{t_{on}/\tau} - 1)}{R_a(e^{T_p/\tau} - 1)} - \frac{E}{R_a} = 9.9A$$

$$i_{on\ period} = \frac{V_{dc} - E}{R_a} - \left(\frac{V_{dc} - E}{R_a} - I_{min} \right) e^{-t/\tau} = 90 - 80 \exp(-5t)$$

$$i_{off\ period} = \frac{-E}{R_a} + \left(\frac{E}{R_a} + I_{max} \right) e^{-t/\tau} = -150 + 160 \exp(-5t)$$

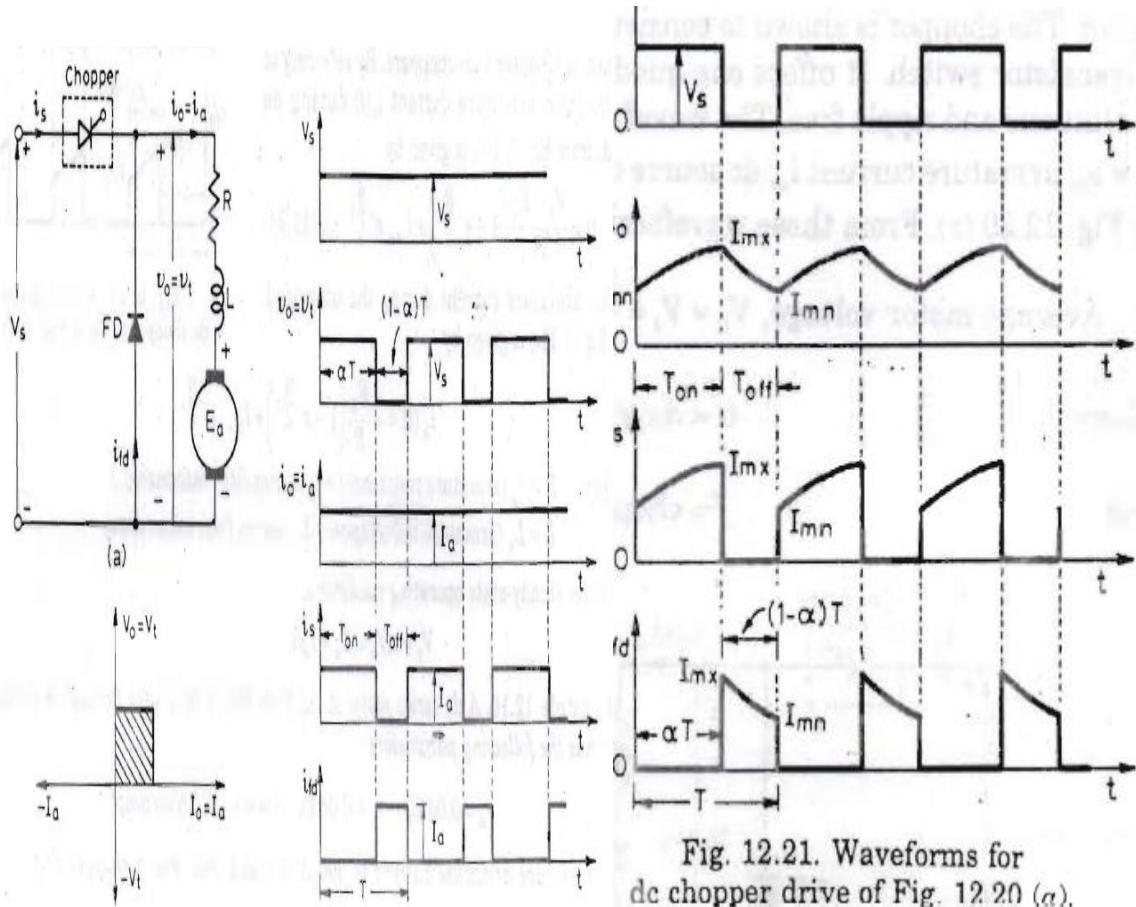


Fig. 12.21. Waveforms for dc chopper drive of Fig. 12.20 (a).

Question (5)

[25] Points

a- Explain how to control the speed of the 3-phase induction motor?

The speed control of an induction motor requires more elaborate techniques than the speed control of dc machines. First, however, let us analyze the basic relationship for the speed-torque characteristics of an induction motor given in Equation (5.57).

$$T_d = \frac{P_d}{\omega} = \frac{V^2 R'_2}{s \omega_s \left[\left(R_1 + \frac{R'_2}{s} \right)^2 + X_{eq}^2 \right]} \quad (7.1)$$

By examining this equation, one can conclude that the speed ω (or slip s) can be controlled if at least one of the following variables or parameters is altered:

1. armature or rotor resistance
2. armature or rotor inductance
3. magnitude of terminal voltage
4. frequency of terminal voltage

Using three tools are 1-inverter 2-AC/AC converter 3-cycloconverter

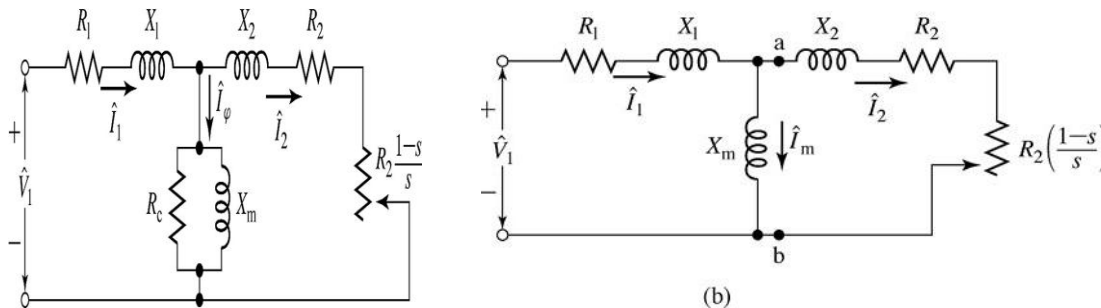


Figure 6.9 Single-phase equivalent circuit for a three-phase induction motor.

Equivalent circuits with the core-loss and iron losses are neglected

b-A three phase 460V, 60Hz, 4 poles, 1750 rpm, wye-connected induction motor has the following equivalent circuit parameters referred to the stator side:

$$R_s = 1.01\Omega, R_r = 0.69\Omega, X_m = 43.5\Omega, X_1 = 1.3\Omega, X_2 = 1.94\Omega, T_L = K\omega_r^2 = 41Nm \text{ at } 1740rpm$$

i- Draw the equivalent circuit and find ω_{syn} , ω_r , S , I_s , I_r , P_{gap} , P_{copper} , T_{dev} ?

ii- If the motor is connected to a 3-phase full wave AC/AC converter. Find the firing angle required to run the motor with speed range of 1000 rpm to 1750 rpm.

iii- If the motor is connected to a 3-phase six step inverter. Find the required DC supply to run the motor with speed of 1000 rpm?

iv- Draw the power circuit and current and voltage waveforms for case ii and case iii?

$$n_s = 120 \cdot 60 / 4 = 1800 \text{ rpm}, \omega_s = 1800 \cdot \pi / 30 = 188.5 \text{ rad/sec.}, \omega_r = 1740 \cdot \pi / 30 = 182.2 \text{ rad/sec.}$$

$$S1=(n_s-n_r)/n_s = (1800-1750)/1800= 0.028, \omega_{r1}=1750*\pi/30=183.3\text{rad/sec.}$$

$$S2=(n_s-n_r)/n_s = (1800-1000)/1800= 0.444, \omega_{r2}=1000*\pi/30=104.72\text{rad/sec.}$$

$$\text{motor torque} = \frac{3I_2^2 R_2}{S\omega_s} = \text{load torque} = K\omega_r^2 = k(182.2)^2 = 41\text{Nm}, K = 0.001235$$

$$\text{load torque1} = K\omega_{r1}^2 \text{ Nm} = 0.001235(183.3)^2 = 41.5\text{Nm} = \frac{3 * 0.69 * I_2^2}{0.028 * 188.5} = I_2 = 10.3\text{A},$$

$$V_{ph} = I_2 * Z = I_2 * \sqrt{\left[\left(R_1 + \frac{R_2}{S}\right)^2 + (X_1 + X_2)^2\right]}$$

$$V_{ph} = 10.3 * \sqrt{\left[\left(1.01 + \frac{0.69}{0.028}\right)^2 + (1.3 + 1.94)^2\right]} = 266.32\text{V}$$

$$\text{load torque2} = K\omega_{r2}^2 \text{ Nm} = 0.001235(104.72)^2 = 13.54\text{Nm} = \frac{3I_2^2 R_2}{S\omega_s}$$

$$I_2 = (0.444 * 188.5 * 13.54)/(3 * 0.69) = 23.4\text{A},$$

$$V_{ph} = 23.4 * \sqrt{\left[\left(1.01 + \frac{0.69}{0.444}\right)^2 + (1.3 + 1.94)^2\right]} = 96.7\text{V}$$

As 1750rpm,

$$\frac{R'_2}{S} = \frac{0.69}{0.028} = 24.64, \quad Z'_2 = 1.01 + 24.64 + j(1.3 + 1.94) = 25.86\angle 7.2^\circ \Omega$$

$$V_{ph} = \frac{460\angle 0}{\sqrt{3}} = 265.6\angle 0\text{V}, I'_2 = \frac{265.6\angle 0}{25.86\angle 7.2} = 10.3\angle -7.2\text{A then } \alpha = 7\text{deg.}$$

As 1000rpm

$$\frac{R'_2}{S} = \frac{0.69}{0.444} = 1.55, \quad Z'_2 = 1.01 + 1.55 + j(1.3 + 1.94) = 4.13\angle 51.7^\circ \Omega$$

$$V_{ph} = \frac{460\angle 0}{\sqrt{3}} = 265.6\angle 0\text{V}, I'_2 = \frac{265.6\angle 0}{4.13\angle 51.7} = 64.3\angle -51.7\text{A}$$

$$\frac{T_{cont.}}{T_{rate}} = \left[\frac{(1 - S_{cont.})}{1 - S_{rate}}\right]^2 = \frac{S_{rate}}{S_{cont.}} \left(\frac{I_{cont.}}{I_{rate}}\right)^2$$

$$I_{cont.} = 10.3 \frac{0.444}{0.028} * \left[\frac{1 - 0.444}{1 - 0.028}\right]^2 = 53.44\text{A}$$

then α, β from table or curves as $I_{aN} = \frac{53.44}{64.3} = 0.83\text{A}, \text{angle} = 51.7\text{deg.}$


The AC/AC converter used to control the speed of the 3-phase induction motor

for six-step inverter $V_{ph} = \sum_{n=6k \pm 1}^{\infty} \frac{2 * V_{dc}}{n * \pi} \sin n \omega t$,

$$V_{1-ph-rms} = \frac{\sqrt{2} * V_{dc}}{\pi} = 96.7, V_{dc} = 215V = 600K, K = 0.36$$

$$V_{1-ph-rms} = \frac{\sqrt{2} * V_{dc}}{\pi} = 266.3, V_{dc} = 266.3V = 600K, K = 0.99$$

Phase control of induction motor

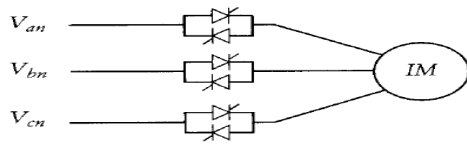

Impact of voltage on motor speed

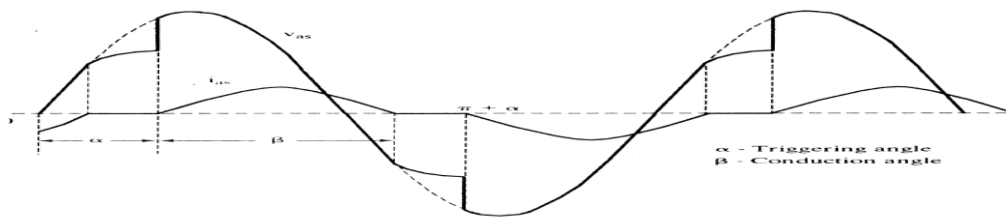
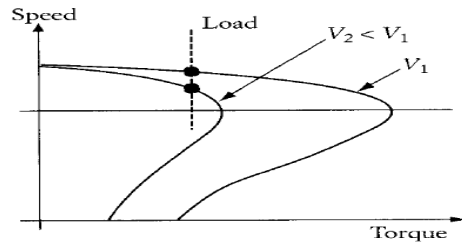


Figure 6.4 Phase voltage and current waveforms

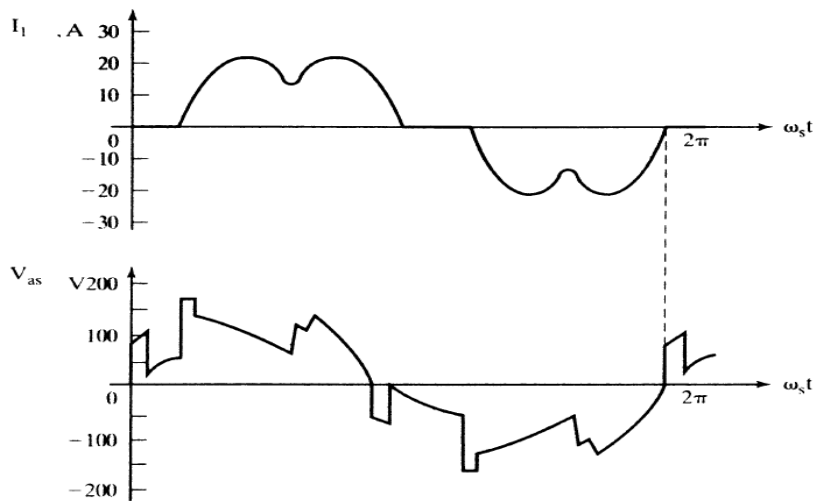


Figure 6.10 Typical line-current and phase-voltage waveforms of a phase-controlled induction motor drive

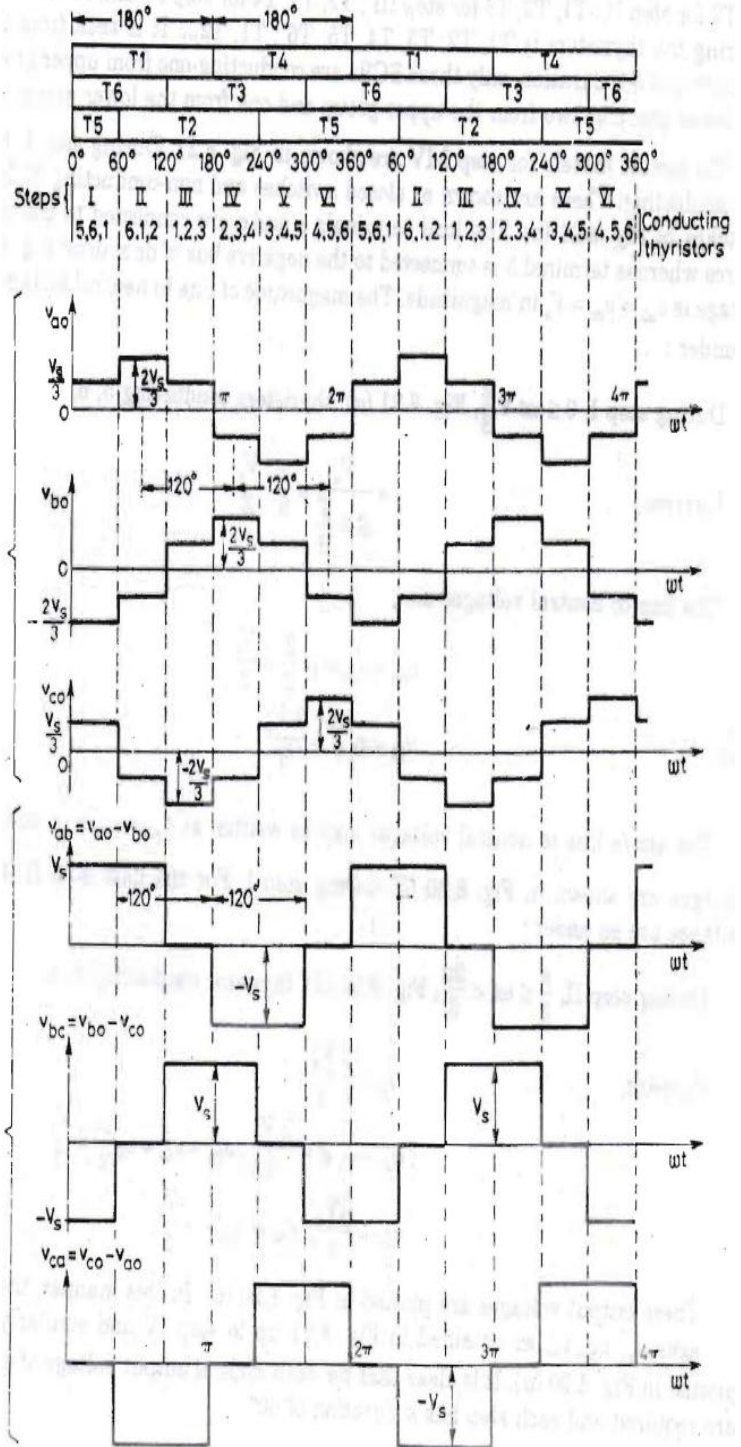
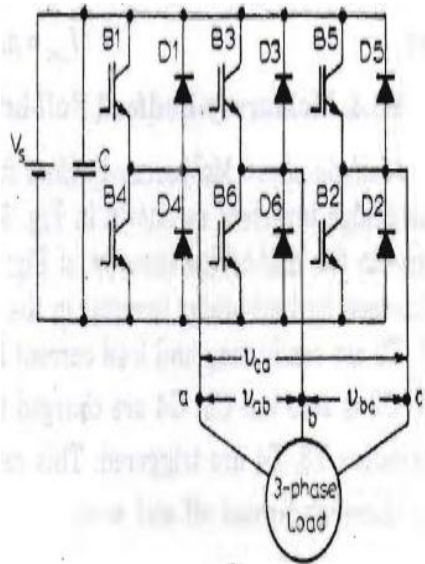


Fig. 8.20. Voltage waveforms for 180° mode 3-phase VSI.

Fourier series expansion of line to neutral voltage v_{ao} in Fig. 8.20 is given by

$$v_{ao} = \sum_{n=6k \pm 1}^{\infty} \frac{2 V_s}{n\pi} \sin n\omega t$$

$k = 0, 1, 2, \dots$

here

and line currents can be obtained from Eqs. (8.44) to (8.46). From Eq. (8.44), rms value of n th component of line voltage is

$$V_{Ln} = \frac{4 V_s}{\sqrt{2} n\pi} \cos \frac{n\pi}{6} \quad \dots(8.48)$$

Rms value of fundamental line voltage,

$$V_{L1} = \frac{4 V_s}{\sqrt{2} \cdot \pi} \cos \frac{\pi}{6} = 0.7797 V_s \quad \dots(8.49)$$

$$V_L = \left[\frac{1}{\pi} \int_0^{2\pi/3} V_s^2 d(\omega t) \right]^{1/2} = \sqrt{\frac{2}{3}} V_s = 0.8165 V_s$$

Rms value of phase voltage V_p is

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{\sqrt{2}}{3} V_s = 0.4714 V_s$$

Rms value of fundamental phase voltage, from Eq. (8.47), is

$$V_{p1} = \frac{2V_s}{\sqrt{2}\pi} = 0.4502 V_s = \frac{V_{L1}}{\sqrt{3}}$$

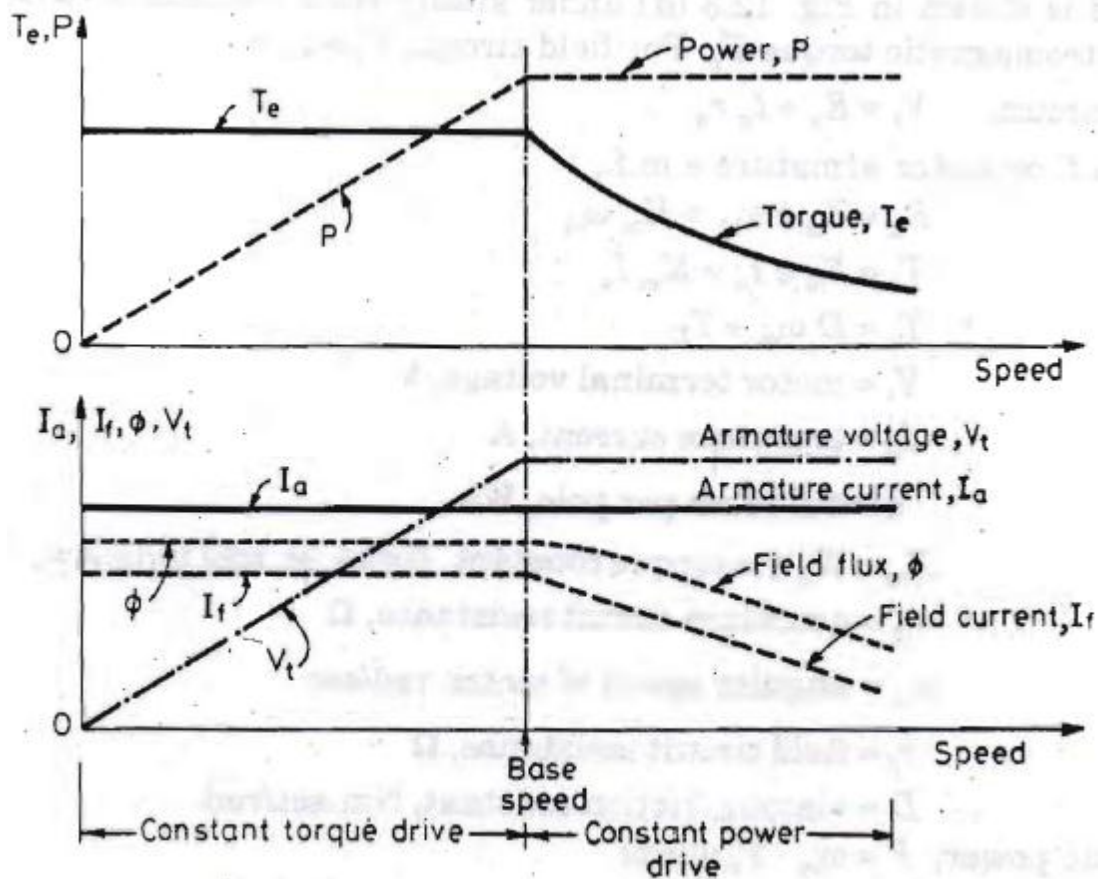


Fig. 12.4. Characteristics of a separately-excited dc motor.

12.19. A separately-excited dc motor is fed from 220 V dc source through a chopper operating at 400 Hz. The load torque is 30 Nm at a speed of 1000 rpm. The motor has $R_a = 0.02 \Omega$ and $K_m = 1.5 \text{ V-sec/rad}$. Neglecting all motor and chopper losses, calculate minimum and maximum values of armature current and the armature current

expressions during on and off periods.

As the armature resistance is neglected, armature current varies linearly between minimum and maximum values.

average armature current, $I_a = \frac{T_e}{K_m} = \frac{30}{1.5} = 20 \text{ A}$

back emf, $E_a = K_m \cdot \omega_m = 1.5 \times \frac{2\pi \times 1000}{60} = 157.08 \text{ V}$

applied voltage, $\alpha V_s = V_t = E_a + I_a r_s = 157.08 + 0$

$$\alpha = \frac{157.08}{220} = 0.714$$

chopper period, $T = \frac{1}{f} = \frac{1}{400} = 2.5 \text{ ms}$

$$T_{on} = \alpha T = 0.714 \times 2.5 = 1.785 \text{ ms}$$

$$T_{off} = (1 - \alpha) T = 0.715 \text{ ms}$$

During on-period T_{on} , armature current will rise which is governed by the equation,

$$0 + L \frac{di_a}{dt} + E_a = V_s$$

$$\frac{di_a}{dt} = \frac{V_s - E_a}{L} = \frac{220 - 157.08}{0.02} = 3146 \text{ A/s}$$

During off-period, $\frac{di_a}{dt} = -\frac{E_a}{L} = \frac{-157.08}{0.02} = -7854 \text{ A/s}$

Since current is rising linearly, it is seen from Fig. 12.21 that

$$I_{mx} = I_{mn} + \left(\frac{di_a}{dt} \text{ during } T_{on} \right) \times T_{on}$$

$$= I_{mn} + 3146 \times 1.785 \times 10^{-3}$$

$$I_{mx} = I_{mn} + 5.616 \quad \dots(i)$$

From the variation between I_{mn} and I_{mx} , average value of armature current

$$I_a = \frac{I_{mx} + I_{mn}}{2} = 20 \text{ A}$$

$$I_{mx} = 40 - I_{mn} \quad \dots(ii)$$

From eqs. (i) and (ii), we get $I_{mx} = 22.808 \text{ A}$

re current expression during turn-off,

$$i_a(t) = I_{mx} + \left(\frac{di_a}{dt} \text{ during } T_{off} \right) \times t$$

$$= 22.808 - 7854 t \quad \text{for } 0 \leq t \leq T_{off}$$

le 12.20. Repeat Example 12.19, in case motor has a resistance of 0.2Ω for its circuit.

a. (a) From Example 12.19, armature current, $I_a = 20 \text{ A}$ and motor emf, $E_a = 157.08 \text{ V}$; re, $V_s = 220 \text{ V}$.

ature circuit, $\alpha V_s = V_0 = V_t = E_a + I_a r_a = 157.08 + 20 \times 0.2 = 161.08 \text{ V}$

$$\alpha = \frac{161.08}{220} = 0.7322$$

$$T_{on} = \alpha T = 0.7322 \times 2.5 = 1.831 \text{ ms}$$

$$T_{off} = T - T_{on} = 0.669 \text{ ms}, \quad \frac{R}{L} = \frac{0.2}{0.02} = 10$$

T_{on} , from Eq. (12.34), armature current is

$$i_a(t) = \frac{220 - 157.08}{0.2} (1 - e^{-10t}) + I_{mn} \cdot e^{-10t}$$

$$= 314.6 (1 - e^{-10t}) + I_{mn} \cdot e^{-10t}$$

$T_{on} = 1.831 \text{ ms}$, current become I_{mx} . This gives

$$i_a(t) = I_{mx} = 5.7079 + 0.98187 I_{mn} \quad \dots(i)$$

T_{off} , from Eq. (12.35), armature current is

$$i_a(t) = \frac{-157.08}{0.2} (1 - e^{-10t}) + I_{mx} \cdot e^{-10t}$$

$$= -785.4 (1 - e^{-10t}) + I_{mx} \cdot e^{-10t}$$

0.669 ms , $i_a(t) = I_{mn}$. This gives

$$i_a(t) = I_{mn} = -5.237 + 0.9933 I_{mx} \quad \dots(ii)$$

Eqs. (i) and (ii), we get

$$I_{mx} = 5.7079 + 0.98187 (-5.237 + 0.9933 I_{mx})$$

$$= 0.5658 + 0.9753 I_{mx}$$

$$I_{mx} = \frac{0.5658}{0.0247} = 22.907 \text{ A}$$

$$I_{mn} = -5.237 + 0.9933 \times 22.907 = 17.516 \text{ A}$$

ature current excursion

$$= I_{mx} - I_{mn} = 22.907 - 17.516 = 5.39 \text{ A}$$

Constant-torque region. As explained before, this region of constant torque can be controlled by volts/hertz control as shown in Fig. 12.29. In the low-frequency range of speed, stator resistance is compensated by a boost in the stator voltage as shown in Fig. 12.29. In this region, stator current is kept constant at its rated value. Power, equal to the constant torque and speed, varies linearly with speed as shown. Slip frequency is constant during this region.

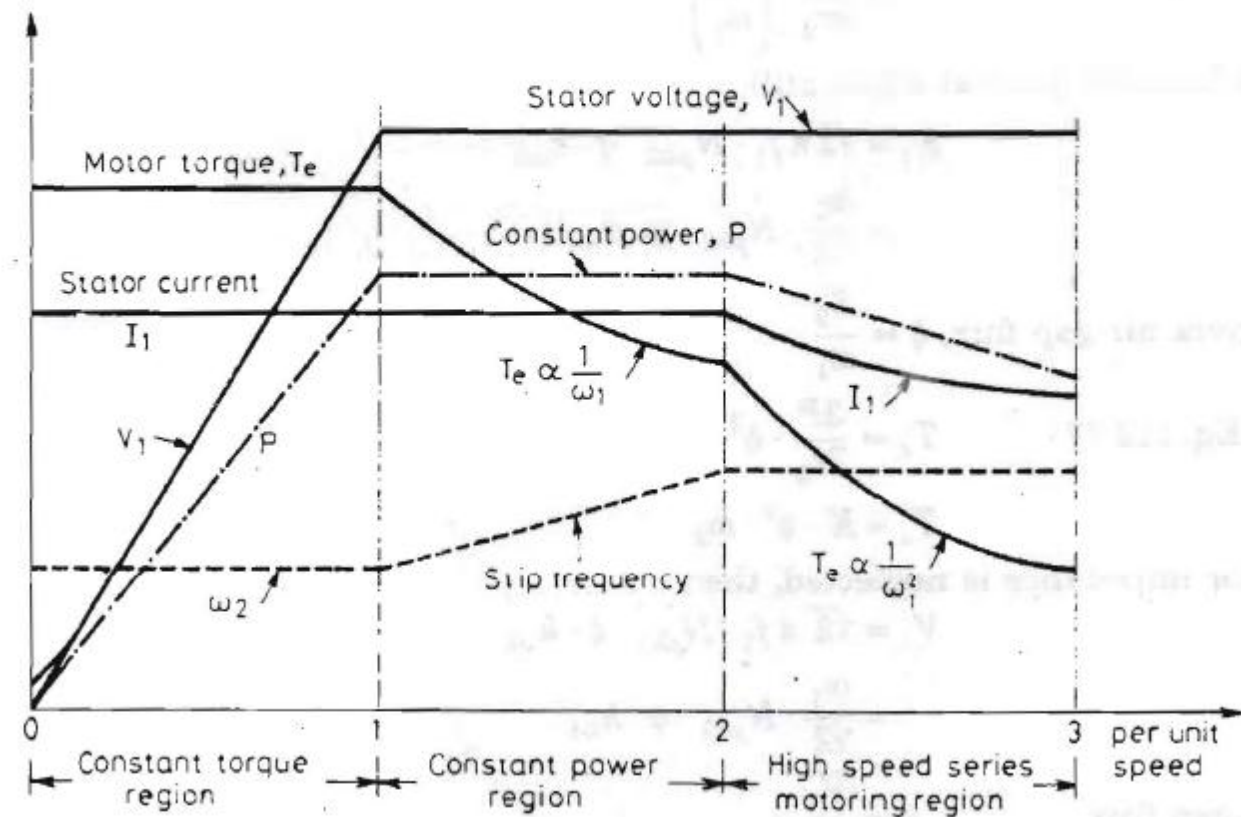


Fig. 12.35. Stator voltage, current, slip-frequency, torque and power variation with speed for speed-torque characteristics of Fig. 12.34.

power region. When maximum speed, called base speed, is attained in the region, stator voltage reaches its rated value. Motor speeds beyond base (or are obtained by keeping stator voltage constant and lowering the stator frequency.

A 3-phase induction motor is given by

$$T_e = \frac{3}{\omega_s} \text{ (Power input to rotor)}$$

$$= \frac{3}{\omega_s} \cdot E_2 I_2 \cos \theta_2$$

For frequency, $\cos \theta_2 \left(= \frac{r_2}{\sqrt{r_2^2 + (2\pi f_2 l_2 s)^2}} \right)$ is almost nearer to unity.

$$T_e = \frac{3}{\omega_s} \cdot E_2 I_2 \quad \dots(12.76)$$

Current, $I_2 = \frac{E_2}{\frac{r_2}{s} + j x_2}$

Since, $\frac{r_2}{s} \gg x_2$. This gives $I_2 = \frac{sE_2}{r_2}$

The three line output voltages can be described by the Fourier series as follows :

$$v_{ab} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \cos \frac{n\pi}{6} \sin n(\omega t + \pi/6) \quad \dots(8.44)$$

$$v_{bc} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \cos \frac{n\pi}{6} \sin n(\omega t - \pi/2) \quad \dots(8.45)$$

$$v_{ca} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \cos \frac{n\pi}{6} \sin n\left(\omega t + \frac{5\pi}{6}\right) \quad \dots(8.46)$$

For $n = 3$, $\cos \frac{3\pi}{6} = 0$. Thus, all triplen harmonics are absent from the line voltages as given by Eqs. (8.44) to (8.46).