

Final Written Examination.

24/12/2013



Time all: 3 Hrs


Answer the following questions

Question (1):

Find the equivalent resistance R_{ab} for the circuit shown in fig.1.

[10 Marks]

Fig.1

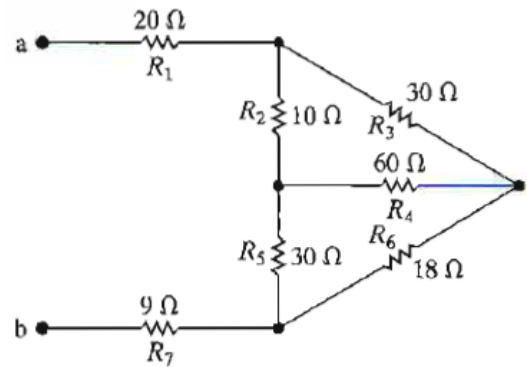

Question (2):

- Use Kirchoff's laws and Ohm's law to find the voltage v_o as shown in Fig. 2.
- Show that your solution is consistent with the constraint that the total power developed in the circuit equals the total power dissipated.

[10 Marks]

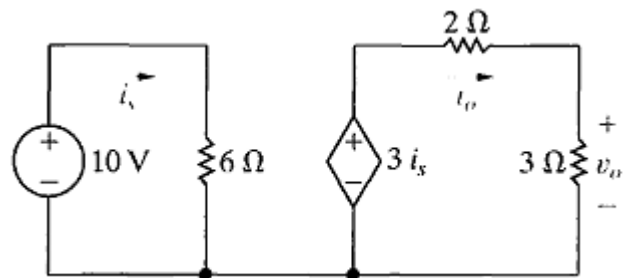


Fig.2

Question (3):

Use the mesh current method to find the total power dissipated in the circuit in Fig. 3

[10 Marks]

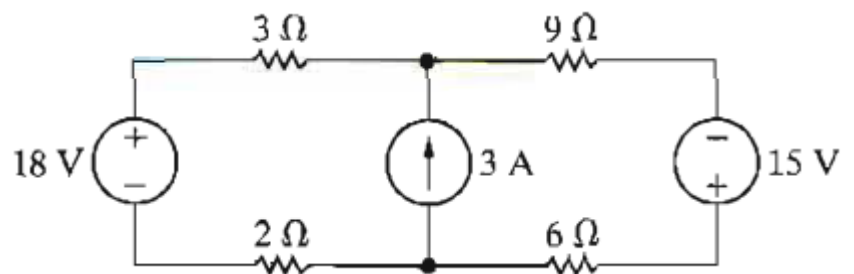


Fig.3

Question (4):

[10 Marks]

Determine the Thevenin equivalent with respect to the terminals a,b for the circuit shown in Fig. 4.

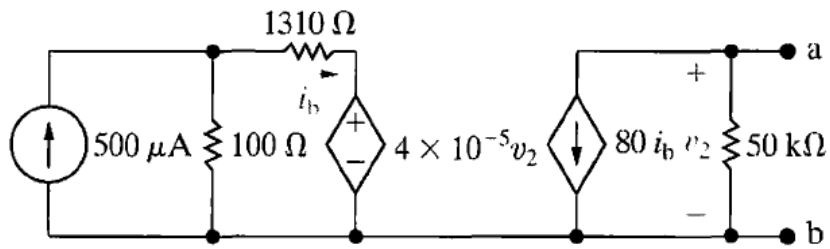


Fig.4

Question (5):

[10 Marks]

The switch in the circuit shown in Fig. 5 has been in position x for a long time.

At $t = 0$, the switch moves instantaneously to position y. Find

- a) $v_c(t)$ for $t \geq 0$,
- b) $v_o(t)$ for $t \geq 0+$
- c) $i_o(t)$ for $t \geq 0+$, and
- d) The total energy dissipated in the 60 kΩ resistor.

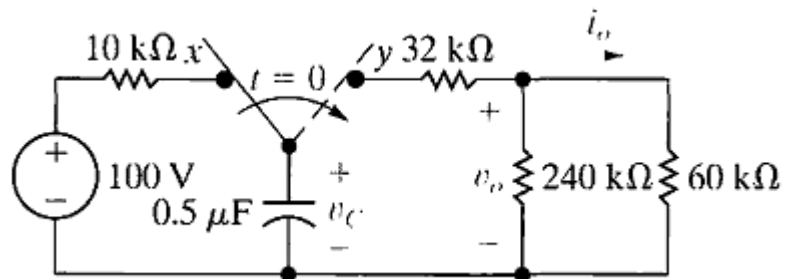


Fig.5

Question (6):

[10 Marks]

Use the concept of source transformation to find the phasor voltage V_0 in the circuit shown in Fig. 6.

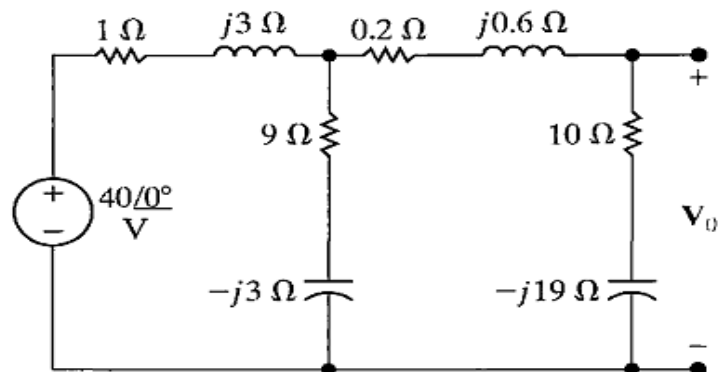


Fig.6

Fig. 6