



Model Answer

Question (1): [12 Marks]

$$40i_2 + \frac{5}{40} + \frac{5}{10} = 0; \quad i_2 = -15.625 \text{ mA}$$

$$v_1 = 80i_2 = -1.25 \text{ V}$$

$$25i_1 + \frac{(-1.25)}{20} + (-0.015625) = 0; \quad i_1 = 3.125 \text{ mA}$$

$$v_g = 60i_1 + 260i_1 = 320i_1$$

Therefore, $v_g = 1 \text{ V}$.

Question (2): [12 Marks]

Convert the upper delta to a wye.

$$R_1 = \frac{(50)(50)}{200} = 12.5 \Omega$$

$$R_2 = \frac{(50)(100)}{200} = 25 \Omega$$

$$R_3 = \frac{(100)(50)}{200} = 25 \Omega$$


Convert the lower delta to a wye.

$$R_4 = \frac{(60)(80)}{200} = 24 \Omega$$

$$R_5 = \frac{(60)(60)}{200} = 18 \Omega$$


$$R_6 = \frac{(80)(60)}{200} = 24 \Omega$$

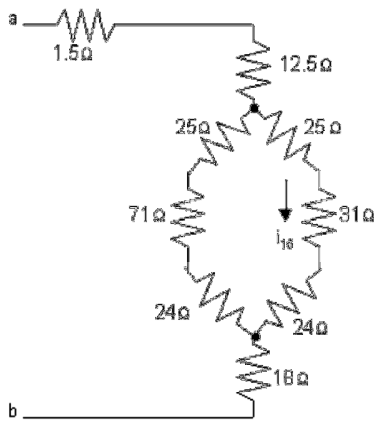Now redraw the circuit using the wye equivalents.



$$R_{ab} = 1.5 + 12.5 + \frac{(120)(80)}{200} + 18 = 14 + 48 + 18 = 80 \Omega$$

Question (3): [15 Marks]

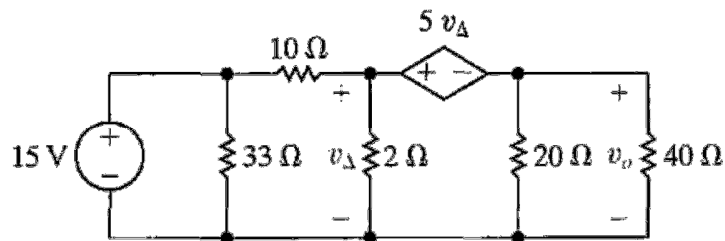


Place $5v_{\Delta}$ inside a supernode and use the lower node as a reference. Then

$$\frac{v_{\Delta} - 15}{10} + \frac{v_{\Delta}}{2} + \frac{v_{\Delta} - 5v_{\Delta}}{20} + \frac{v_{\Delta} - 5v_{\Delta}}{40} = 0$$

$$12v_{\Delta} = 60; \quad v_{\Delta} = 5 \text{ V}$$

$$v_o = v_{\Delta} - 5v_{\Delta} = -4(5) = -20 \text{ V}$$

Question (4): [15 Marks]

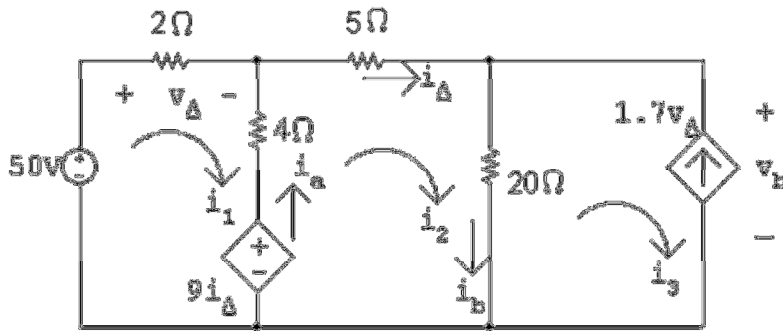

Mesh equations:

$$-50 + 6i_1 - 4i_2 + 9i_{\Delta} = 0$$

$$-9i_{\Delta} - 4i_1 + 29i_2 - 20i_3 = 0$$

Constraint equations:

$$i_{\Delta} = i_2; \quad i_3 = -1.7v_{\Delta}; \quad v_{\Delta} = 2i_1$$

Solving, $i_1 = -5 \text{ A}; \quad i_2 = 16 \text{ A}; \quad i_3 = 17 \text{ A}; \quad v_{\Delta} = -10 \text{ V}$

$$9i_{\Delta} = 9(16) = 144 \text{ V}$$

$$i_a = i_2 - i_1 = 21 \text{ A}$$

$$i_b = i_2 - i_3 = -1 \text{ A}$$

$$v_b = 20i_b = -20 \text{ V}$$

$$p_{50\text{V}} = -50i_1 = 250 \text{ W (absorbing)}$$


$$p_{9i_{\Delta}} = -i_a(9i_{\Delta}) = -(21)(144) = -3024 \text{ W (delivering)}$$

$$p_{1.7\text{V}} = -1.7v_{\Delta}v_b = i_3v_b = (17)(-20) = -340 \text{ W (delivering)}$$

$$\sum P_{\text{dev}} = 3024 + 340 = 3364 \text{ W}$$

$$\begin{aligned} \sum P_{\text{dis}} &= 250 + (-5)^2(2) + (21)^2(4) + (16)^2(5) + (-1)^2(20) \\ &= 3364 \text{ W} \end{aligned}$$

Question (5): [14 Marks]

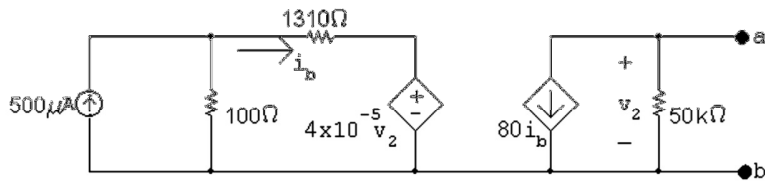

OPEN CIRCUIT

$$v_2 = -80i_b(50 \times 10^3) = -40 \times 10^5 i_b$$

$$4 \times 10^{-5} v_2 = -160i_b$$

$$1310i_b + 4 \times 10^{-5} v_2 = 1310i_b - 160i_b = 1150i_b$$

So $1150i_b$ is the voltage across the 100Ω resistor.

$$\text{From KCL at the top left node, } 500 \mu\text{A} = \frac{1150i_b}{100} + i_b = 12.5i_b$$

$$\therefore i_b = \frac{500 \times 10^{-6}}{12.5} = 40 \mu\text{A}$$

$$v_{\text{Th}} = -40 \times 10^5 (40 \times 10^{-6}) = -160 \text{ V}$$


SHORT CIRCUIT

$$v_2 = 0; \quad i_{\text{sc}} = -80i_b$$

$$i_b = \frac{100}{100 + 1310} (500 \times 10^{-6}) = 35.46 \mu\text{A}$$


$$i_{\text{sc}} = -80(35.46) = -2837 \mu\text{A}$$
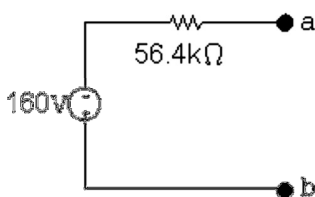
$$R_{\text{Th}} = \frac{-160}{-2837 \times 10^{-6}} = 56.4 \text{ k}\Omega$$



Question (6): [12 Marks]


6 A source:

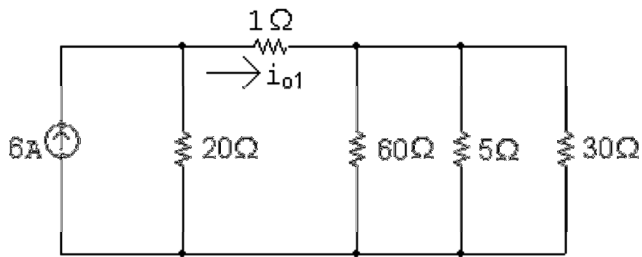

$$30\ \Omega \parallel 5\ \Omega \parallel 60\ \Omega = 4\ \Omega$$


$$\therefore i_{o1} = \frac{20}{20 + 5}(6) = 4.8\ \text{A}$$

10 A source:

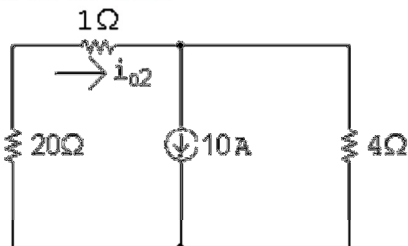

$$i_{o2} = \frac{4}{25}(10) = 1.6\ \text{A}$$

75 V source:

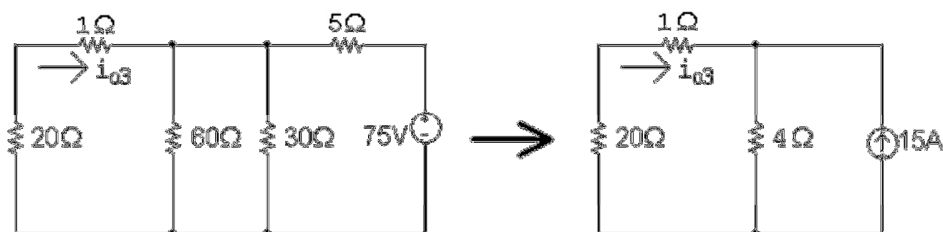

$$i_{o3} = -\frac{4}{25}(15) = -2.4\ \text{A}$$

$$i_o = i_{o1} + i_{o2} + i_{o3} = 4.8 + 1.6 - 2.4 = 4\ \text{A}$$

Question (7): [10 Marks]

In the difference amplifier shown in Fig.7, what range of values of R_x yields saturation in both directions?

Solve by yourself.



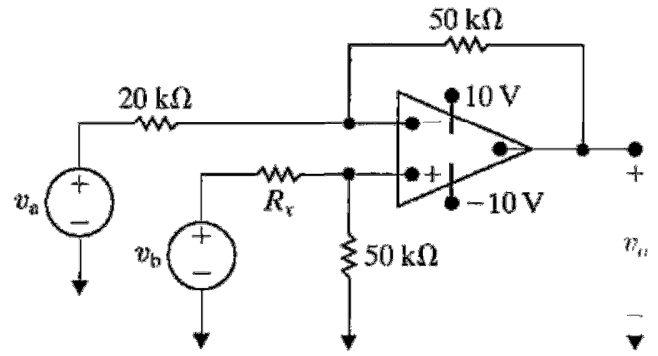


Fig.7


Question (8): [10 Marks]

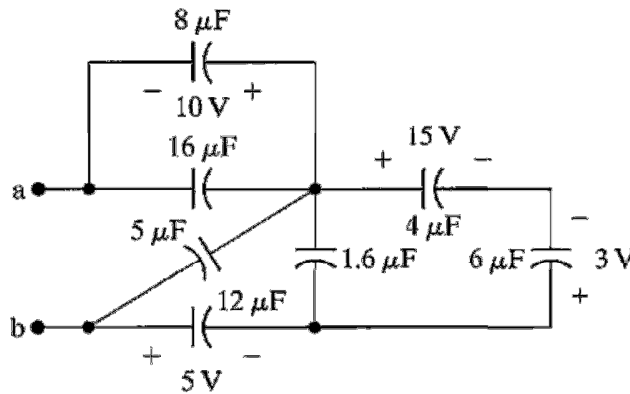

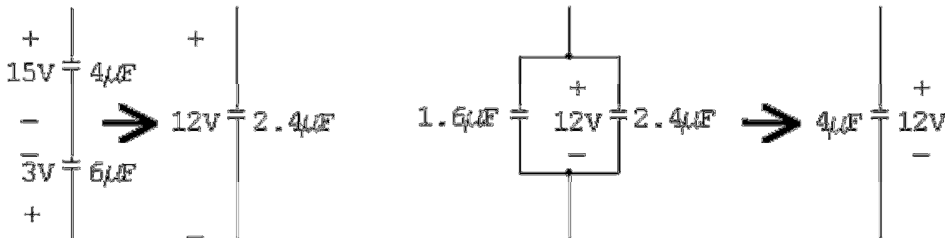
$$\frac{1}{4} + \frac{1}{6} = \frac{5}{12} \quad \therefore C_{eq} = 2.4 \mu\text{F}$$


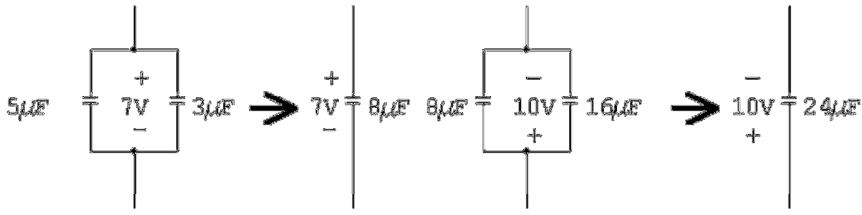
$$\frac{1}{4} + \frac{1}{12} = \frac{4}{12} \quad \therefore C_{eq} = 3 \mu\text{F}$$


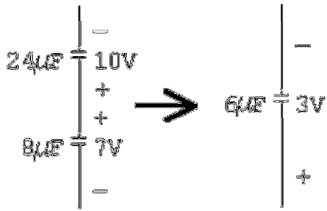
$$\frac{1}{24} + \frac{1}{8} = \frac{4}{24} \quad \therefore C_{eq} = 6 \mu\text{F}$$



Complete your solution using $Q = \frac{1}{2} CV^2$

With best wishes