

عناوين الابحاث تخلفات مادة دوائر كهربية-٢ —د/ شوقي حامد عرفة

EME208 Electric circuits II

- 1- Compare between step-response of series-RLC circuit and parallel-RLC circuits.
- 2- Compare between natural-response of series-RLC circuit and parallel-RLC circuit.
- 3-Voltage and power of balanced three-phase circuits